



EAST WEST UNIVERSITY

Course Title: CSE209

Section: 02

Semester: Fall 22

Assignment- 01

SUBMITTED TO

M. Saddam Hossain Khan

Senior Lecturer

Department of Computer Science & Engineering

East West University


SUBMITTED BY

Name: B M Shahria Alam

Student ID: 2021-3-60-016

Date of submission: 03 November 2022.

Assignment 1

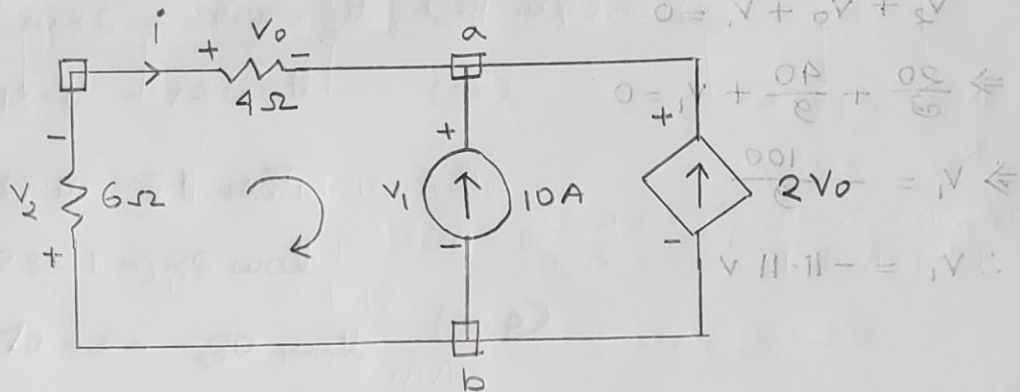

Let,

the current of V_0 , I and given resistance $R = 4\Omega$

$$\begin{aligned} \therefore \text{By Ohm's law, } V_0 &= IR \\ &= I \cdot 4 \\ &= 4I \end{aligned}$$

$$\left(\frac{0.01}{e} \times 2 \right) \times \frac{0.01}{e} =$$

$$1000 \times 2 \times 0.80 =$$

Now applying KCL in node a,

$$-I - 10 - 2V_0 = 0$$

$$\Rightarrow -I - 10 - 2(4I) = 0$$

$$\Rightarrow -I - 10 - 8I = 0$$

$$\Rightarrow I = -\frac{10}{9} \text{ A}$$

$$\begin{aligned} \text{So, } V_0 &= 4 \times \frac{10}{9} \\ &= 4.444 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{And, } V_2 &= 6 \times \frac{10}{9} \\ &= \frac{20}{3} \\ &= 6.67 \text{ V} \end{aligned}$$

Applying KVL in the loop, Assuming

$$V_2 + V_0 + V_1 = 0$$

$$\Rightarrow \frac{20}{3} + \frac{40}{9} + V_1 = 0$$

$$\Rightarrow V_1 = -\frac{100}{9}$$

$$\therefore V_1 = -11.11 \text{ V}$$

\therefore So, the power across the dependent source is,

$$\begin{aligned} P &= -V_1 \times (2V_0) \\ &= \frac{100}{9} \times \left(2 \times \frac{40}{9}\right) \\ &= 98.765 \text{ watt} \end{aligned}$$