


Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Term II Examination, Fall 2020 Semester

Course: CSE 345 Digital Logic Design, Section-2
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 40 (20 will be counted for final grading)
Time: 1 Hour and 30 Minutes (Including Submission)

Note: There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Consider that $ABCD$ is a 4-bit input and X is a 1-bit output of a combinational circuit. The output is $X = 1$ if the input contains even number of 0s; otherwise $X = 0$. **Design** the combinational circuit. [CO3,C3, Mark: 6]

 2. **Analyze** the following circuit by constructing truth table of the outputs. [CO2,C4, Mark: 8]



- | | | |
|----|--|-------------------|
| 3. | Design a full-adder using only AND, EXOR, and OR gates. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] | [CO3,C3, Mark: 6] |
| 4. | Design a 10×4 Encoder for active-LOW input. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] | [CO3,C6, Mark: 6] |

5. **Construct** a combinational circuit using an 8×1 MUX for implementing the following Boolean function. [Properly label all the inputs and outputs] [CO3,C6, Mark: 6]
- $$F(A, B, C, D) = \sum (1, 5, 6, 8, 10, 12, 14)$$
6. **Write** a Procedural Verilog description using case statement for implementing a 4 × 1 MUX with active-LOW Enable input. [CO3,C6, Mark: 8]