


# Chapter 8

## Encoders, Decoders, Multiplexers, and Demultiplexers


## 8.2 Encoders
 
### 8.2.1 Design of Encoders


An *encoder* is a combinational circuit that has  $2^n$  (or less) input lines and  $n$  output lines. Only one of the input lines is activated at a given time. The output lines generate the binary code corresponding to the activated input. The input lines can be activated in two ways – by setting the activated input to 0 and the other inputs to 1 (active-LOW input) or by setting the activated input to 1 and the other inputs to 0 (active-HIGH input). The block diagram and truth tables of an



(a) Block diagram for active-LOW input

 

(c) Block diagram for active-HIGH input

 

(a) Block diagram for active-LOW input

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$O_2$	$O_1$	$O_0$
1	1	1	1	1	1	1	0	0	0	0
1	1	1	1	1	1	0	1	0	0	1
1	1	1	1	1	0	1	1	0	1	0
1	1	1	1	0	1	1	1	0	1	1
1	1	1	0	1	1	1	1	1	0	0
1	1	0	1	1	1	1	1	1	0	1
1	0	1	1	1	1	1	1	1	1	0
0	1	1	1	1	1	1	1	1	1	1

(b) Truth table for active-LOW input

For active-LOW input

$$O_0 = D_1' + D_3' + D_5' + D_7' = (D_1 D_3 D_5 D_7)'$$

$$O_1 = D_2' + D_3' + D_6' + D_7' = (D_2 D_3 D_6 D_7)'$$


$$O_2 = D_4' + D_5' + D_6' + D_7' = (D_4 D_5 D_6 D_7)'$$

For active-LOW input


$$O_0 = D'_1 + D'_3 + D'_5 + D'_7 = (D_1 D_3 D_5 D_7)'$$

$$O_1 = D'_2 + D'_3 + D'_6 + D'_7 = (D_2 D_3 D_6 D_7)'$$
 
$$O_2 = D'_4 + D'_5 + D'_6 + D'_7 = (D_4 D_5 D_6 D_7)'$$



(a) Active-LOW input

 

(c) Block diagram for active-HIGH input

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

(d) Truth table for active-HIGH input

For active-HIGH input

$$O_0 = D_1 + D_3 + D_5 + D_7$$

$$O_1 = D_2 + D_3 + D_6 + D_7$$


$$O_2 = D_4 + D_5 + D_6 + D_7$$

For active-HIGH input

$$O_0 = D_1 + D_3 + D_5 + D_7$$

$$O_1 = D_2 + D_3 + D_6 + D_7$$

$$O_2 = D_4 + D_5 + D_6 + D_7$$

 


(b) Active-HIGH input


## 8.3 Decoders
 
### 8.3.1 Design of Decoders

A *decoder* is a combinational circuit that accepts  $n$  inputs that represent a binary code and activate only the output that corresponds to the input code. The number of output lines may be a maximum of  $2^n$ . If the  $n$ -bit decoded information has unused or don't care combinations, the decoder output will have less than  $2^n$  outputs. The output lines can be activated in two ways – by setting the activated output to 0 and the other outputs to 1 (active-LOW output) or by setting the activated output to 1 and the other outputs to 0 (active-HIGH output). If the number of output lines is less than  $2^n$ , the decoder is often designed such that all the outputs remain inactivated when an invalid input combination (unused code) is applied.




(a) Block diagram for active-LOW output

 

(c) Block diagram for active-HIGH output

# Binary-to-Octal Decoder

 

(a) Block diagram for active-LOW output

Inputs			Outputs							
$A_2$	$A_1$	$A_0$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	1	1	1	1	1	1	1	0
0	0	1	1	1	1	1	1	1	0	1
0	1	0	1	1	1	1	1	0	1	1
0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	1	1	0	1	1	1	1
1	0	1	1	1	0	1	1	1	1	1
1	1	0	1	0	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1

(b) Truth table for active-LOW output

For active-LOW output

$$O_0 = A_2 + A_1 + A_0 = (A_2' A_1' A_0')'$$

$$O_1 = A_2 + A_1 + A_0' = (A_2' A_1' A_0)'$$

$$O_2 = A_2 + A_1' + A_0 = (A_2' A_1 A_0')'$$

$$O_3 = A_2 + A_1' + A_0' = (A_2' A_1 A_0)'$$


$$O_4 = A_2' + A_1 + A_0 = (A_2 A_1' A_0')'$$

$$O_5 = A_2' + A_1 + A_0' = (A_2 A_1' A_0)'$$


$$O_6 = A_2' + A_1' + A_0 = (A_2 A_1 A_0')'$$
 
$$O_7 = A_2' + A_1' + A_0' = (A_2 A_1 A_0)'$$





(a) Active-LOW output

 

(c) Block diagram for active-HIGH output

Inputs			Outputs							
$A_2$	$A_1$	$A_0$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

(d) Truth table for active-HIGH output

For active-HIGH output

$$O_0 = A_2' A_1' A_0'$$

$$O_1 = A_2' A_1' A_0$$

$$O_2 = A_2' A_1 A_0'$$


$$O_3 = A_2' A_1 A_0$$

$$O_4 = A_2 A_1' A_0'$$

$$O_5 = A_2 A_1' A_0$$


$$O_6 = A_2 A_1 A_0'$$

$$O_7 = A_2 A_1 A_0$$

 

(a) Active-HIGH output
 
## BCD-to-Decimal Decoder with active-LOW output:



Inputs				Outputs									
$A_3$	$A_2$	$A_1$	$A_0$	$O_9$	$O_8$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	1	1	1	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	1	1	1	1	0	1
0	0	1	0	1	1	1	1	1	1	1	0	1	1
0	0	1	1	1	1	1	1	1	1	0	1	1	1
0	1	0	0	1	1	1	1	1	0	1	1	1	1
0	1	0	1	1	1	1	1	0	1	1	1	1	1
0	1	1	0	1	1	1	0	1	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1	1	1	1	1	1	1
1	0	0	1	0	1	1	1	1	1	1	1	1	1
1	0	1	0	1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1	1

(b) Truth table

$$O_0 = A_3 + A_2 + A_1 + A_0 = (A_3' A_2' A_1' A_0')'$$

$$O_1 = A_3 + A_2 + A_1 + A_0' = (A_3' A_2' A_1' A_0)'$$

$$O_2 = A_3 + A_2 + A_1' + A_0 = (A_3' A_2' A_1 A_0')'$$

$$O_3 = A_3 + A_2 + A_1' + A_0' = (A_3' A_2' A_1 A_0)'$$

$$O_4 = A_3 + A_2' + A_1 + A_0 = (A_3' A_2 A_1' A_0')'$$


$$O_5 = A_3 + A_2' + A_1 + A_0' = (A_3' A_2 A_1' A_0)'$$

$$O_6 = A_3 + A_2' + A_1' + A_0 = (A_3' A_2 A_1 A_0')'$$

$$O_7 = A_3 + A_2' + A_1' + A_0' = (A_3' A_2 A_1 A_0)'$$


$$O_8 = A_3' + A_2 + A_1 + A_0 = (A_3 A_2' A_1' A_0')'$$
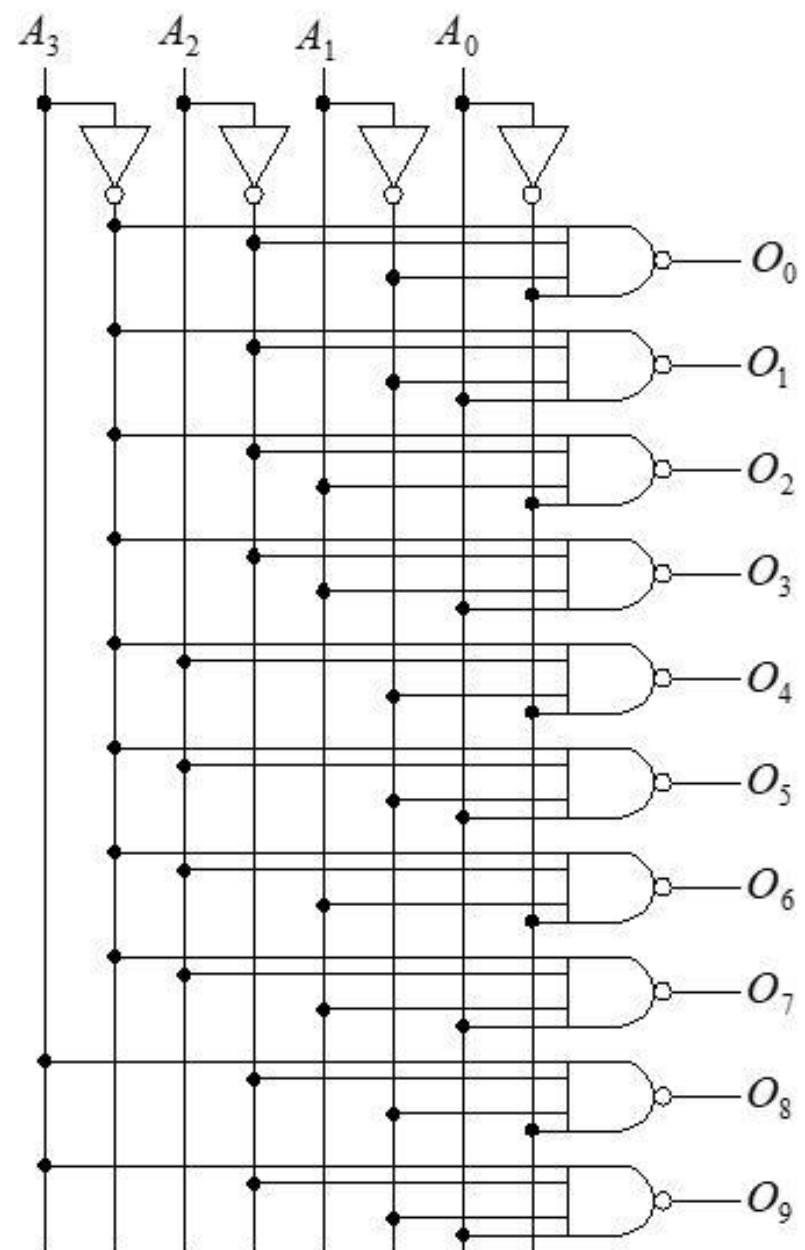
$$O_9 = A_3' + A_2 + A_1 + A_0' = (A_3 A_2' A_1' A_0)'$$


 
### 8.3.2 Decoders with Enable Input

Some decoders have enable input that is used to control the operation of the decoder. If the enable input is active, the output corresponding to the input is activated. If the enable input is not active, no output is activated. The block diagram and truth table of a 2-to-4-line decoder with



(a) Block diagram

Inputs			Outputs			
$E$	$A_1$	$A_0$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

(b) Truth table

$$O_0 = E + A_1 + A_0 = (E'A_1'A_0)'$$

$$O_1 = E + A_1 + A_0' = (E'A_1'A_0)'$$

$$O_2 = E + A_1' + A_0 = (E'A_1A_0)'$$

$$O_3 = E + A_1' + A_0' = (E'A_1A_0)'$$




$$O_0 = E + A_1 + A_0 = (E'A_1'A_0)'$$

$$O_1 = E + A_1 + A_0' = (E'A_1'A_0)'$$

$$O_2 = E + A_1' + A_0 = (E'A_1A_0')'$$

$$O_3 = E + A_1' + A_0' = (E'A_1A_0')'$$

 

- active-LOW Enable Input and active-HIGH Outputs
- active-HIGH Enable Input and active-HIGH Outputs
- active-HIGH Enable Input and active-LOW Outputs

## 8.3.3 Expansion of Decoder

Implementation of 4X16 Decoder





with 2X4 Decoders (active-LOW

Enable Input and active-LOW outputs)


	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	Active Outputs
<u>00</u>	0	0	0	0	O <sub>0</sub>
	0	0	0	1	O <sub>1</sub>
	0	0	1	0	O <sub>2</sub>
	0	0	1	1	O <sub>3</sub>
<u>01</u>	0	1	0	0	O <sub>4</sub>
	0	1	0	1	O <sub>5</sub>
	0	1	1	0	O <sub>6</sub>
	0	1	1	1	O <sub>7</sub>
<u>10</u>	1	0	0	0	O <sub>8</sub>
	1	0	0	1	O <sub>9</sub>
	1	0	1	0	O <sub>10</sub>
	1	0	1	1	O <sub>11</sub>
<u>11</u>	1	1	0	0	O <sub>12</sub>
	1	1	0	1	O <sub>13</sub>
	1	1	1	0	O <sub>14</sub>
	1	1	1	1	O <sub>15</sub>


    
## Implementation of 4X16 Decoder with 2X4 Decoders




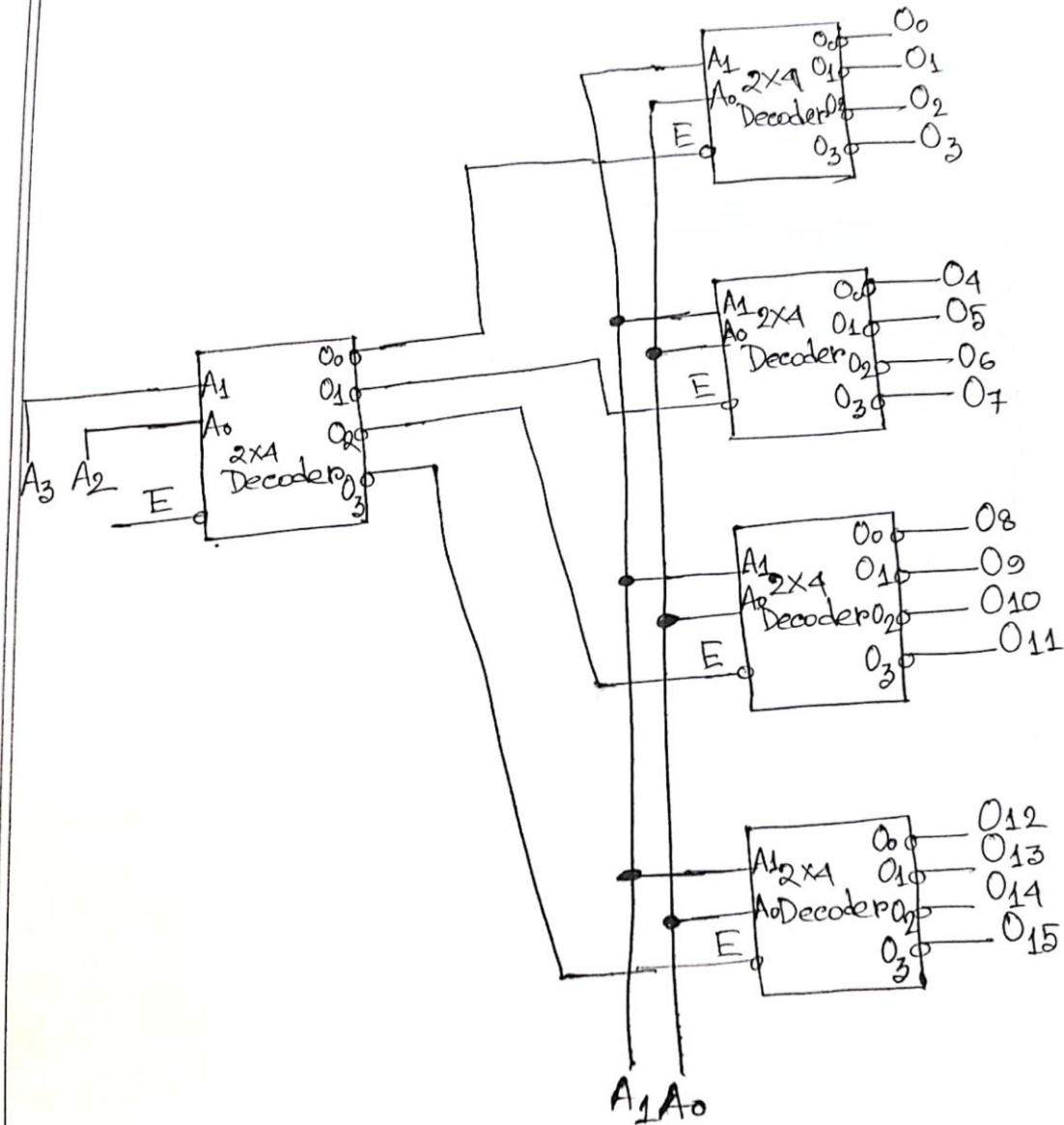
# Implementation of 4X16 Decoder with 2X4 Decoders



# Implementation of 4X16 Decoder with 2X4 Decoders


$A_3 A_2 A_1 A_0$   
1 1 0 1

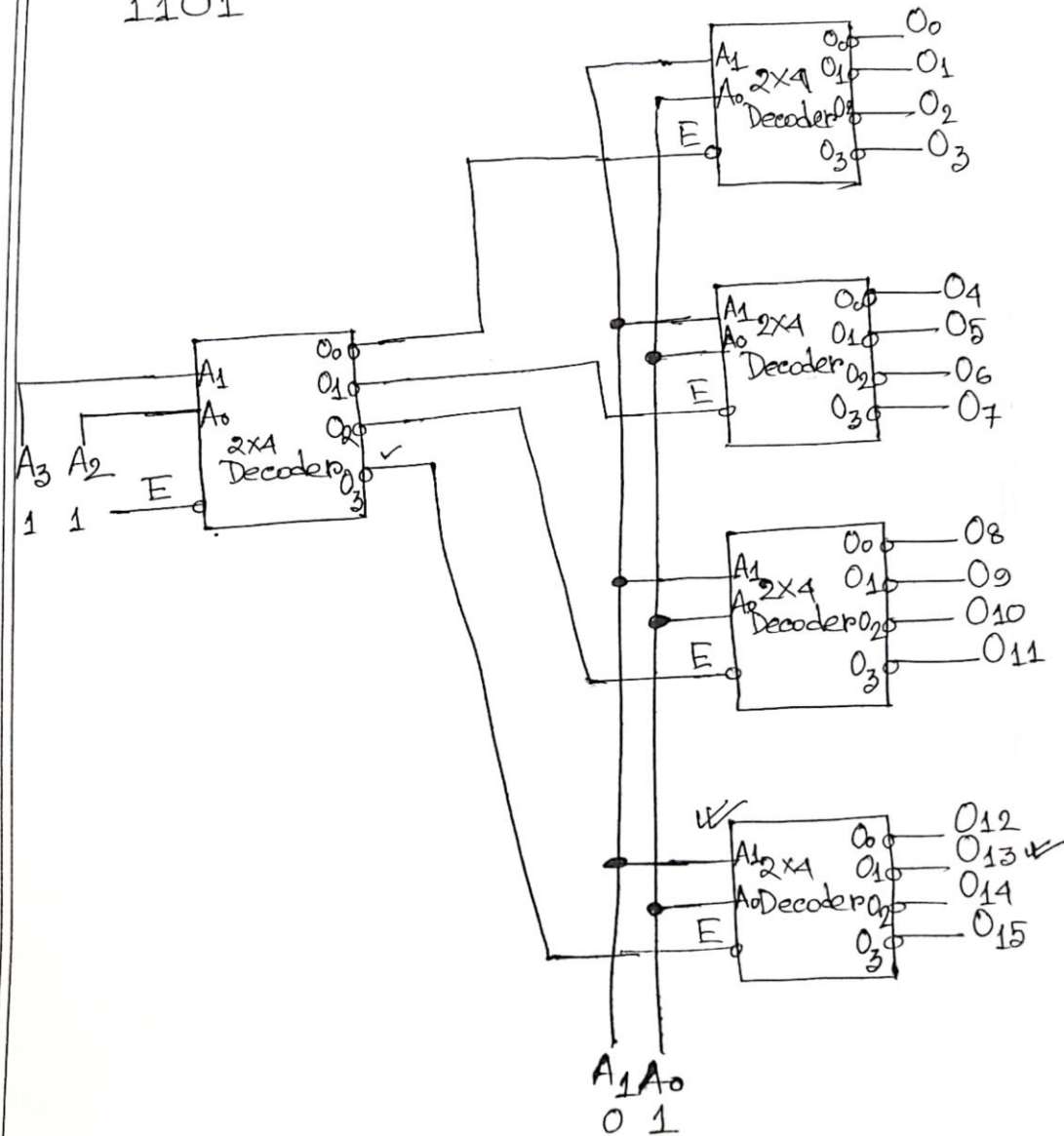


 

(b) Implementation of 4-to-16-line decoder with 2-to-4-line decoders
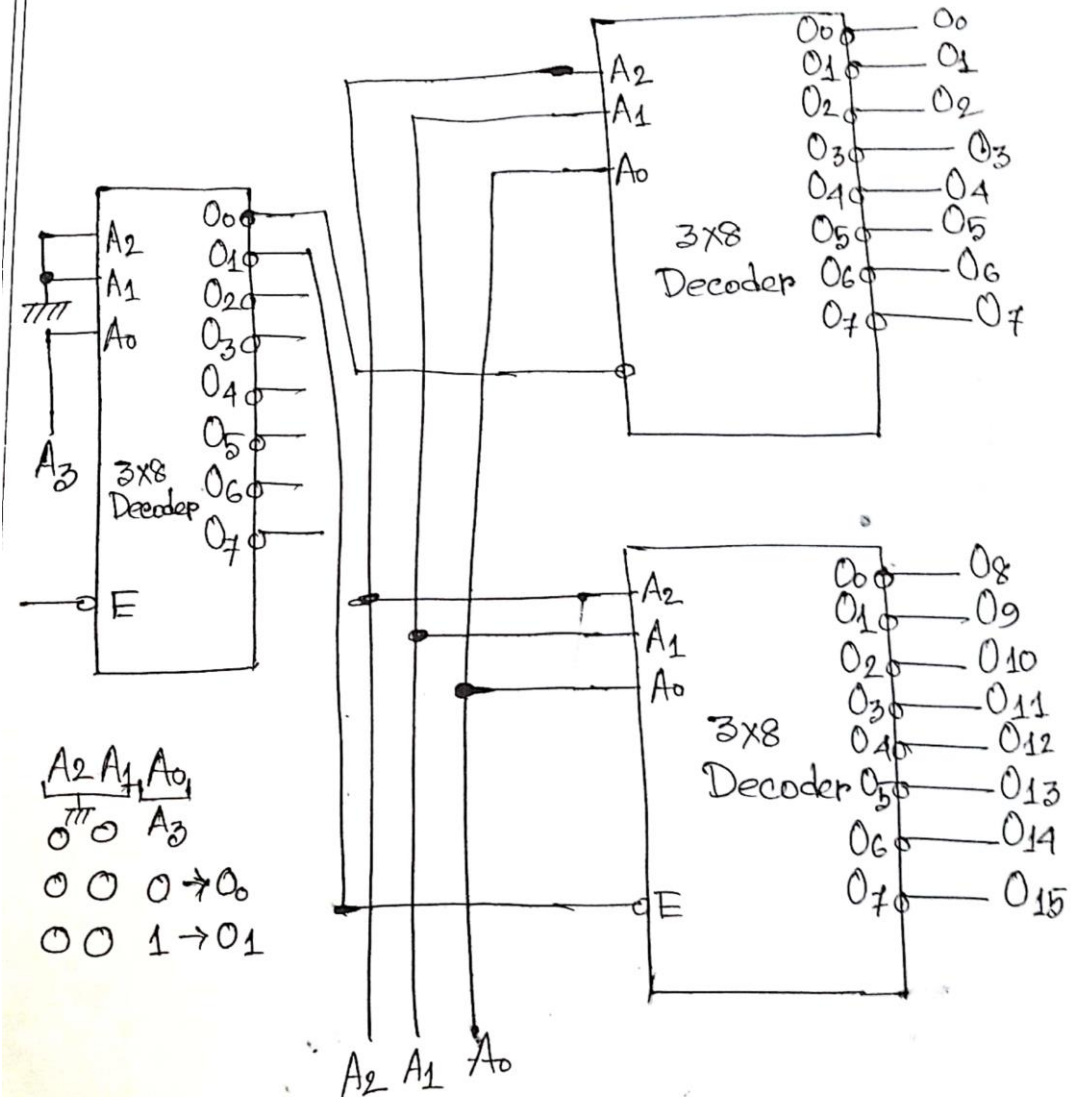
# Implementation of 4x16 Decoder with only 3x8 Decoders (active-LOW Enable Input and active-LOW Outputs)



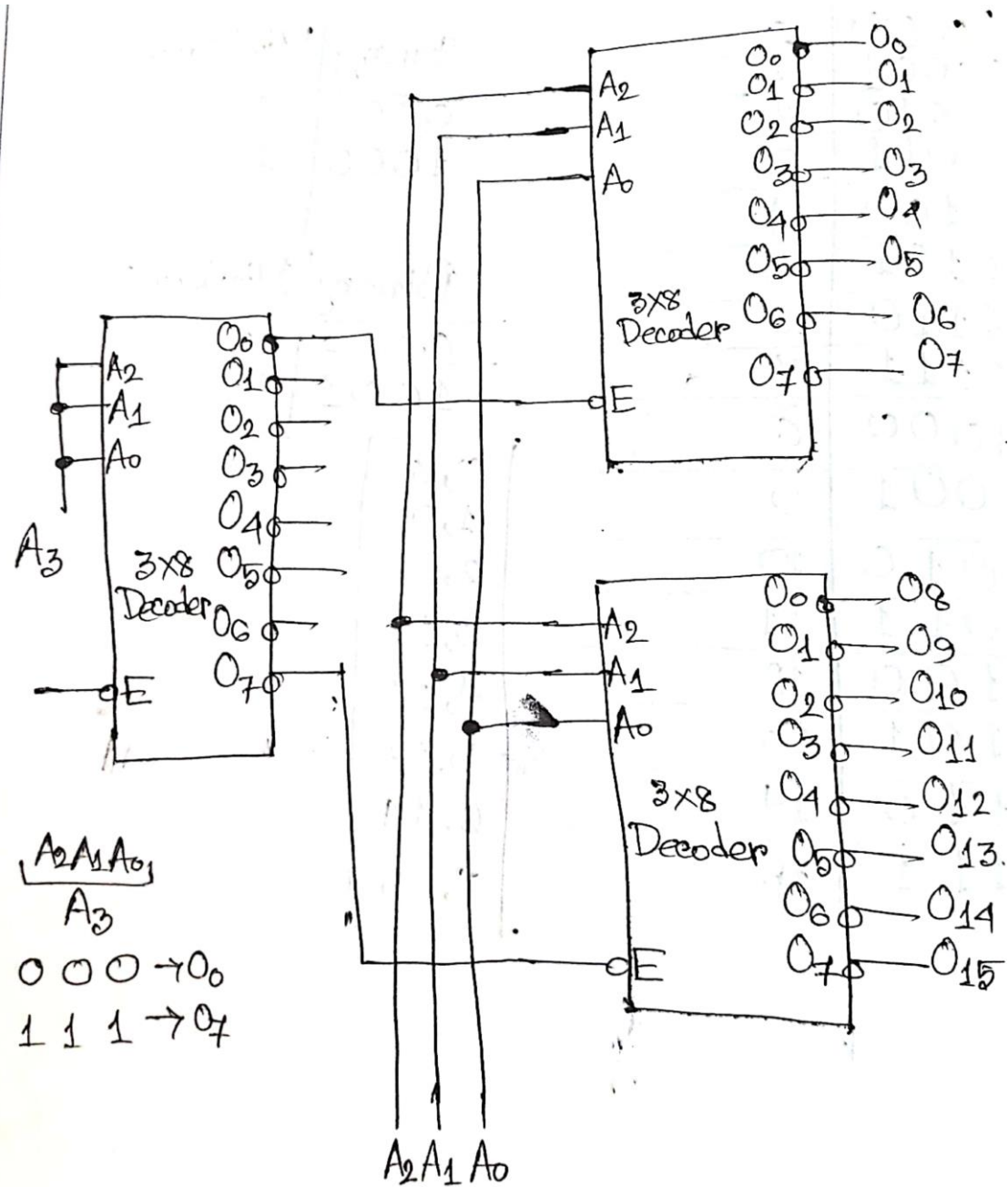


## 8.3.4 Combinational Logic Implementation with Decoder

Implementation of CSOP Function


$$F_1(A, B, C) = \sum (1, 2, 4, 7)$$

$$F_2(A, B, C) = \sum (0, 5, 6, 7)$$

 \* active-HIGH outputs generate Minterms (m)  $m' = M$   
\* active-LOW outputs generate Maxterms (M)  $M' = m$





 

$$F_1(A, B, C) = \sum (1, 2, 4, 7)$$

$$= m_1 + m_2 + m_4 + m_7$$

$$= (m_1 + m_2 + m_4 + m_7)'$$

$$= (m_1' \cdot m_2' \cdot m_4' \cdot m_7')$$


$$= (M_1 \cdot M_2 \cdot M_4 \cdot M_7)$$




## Implementation of CPOS Function

$$F_1(A, B, C) = \prod (0, 3, 5, 6)$$

$$F_2(A, B, C) = \prod (1, 2, 3, 4)$$

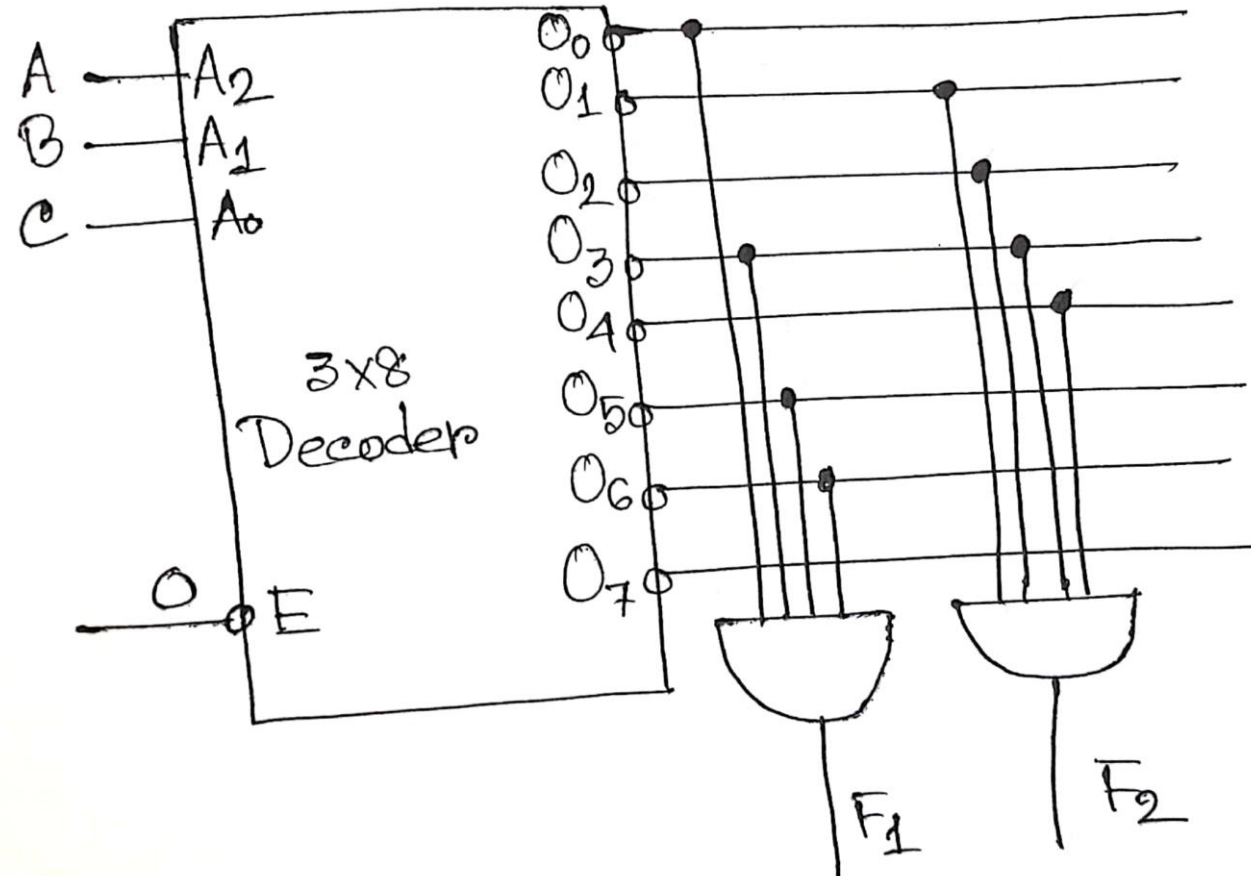

 


$$\begin{aligned}
 F_1(A, B, C) &= \pi(0, 3, 5, 6) \\
 &= M_0 \cdot M_3 \cdot M_5 \cdot M_6 \\
 &= ((M_0 \cdot M_3 \cdot M_5 \cdot M_6)')' \\
 &= (M_0' + M_3' + M_5' + M_6')' \\
 &= (m_0 + m_3 + m_5 + m_6)'
 \end{aligned}$$

# 8.7 Multiplexers (MUX)
 
## 8.7.1 Design of Multiplexers


A digital multiplexer (MUX in short) is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of address lines (also called selection lines). Normally, there are  $2^n$  input lines and  $n$  address lines whose bit combinations determine which input is selected.



(a) Block diagram


$A_1$	$A_0$	$O$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Truth table

 

$$O = I_0 A_1' A_0' + I_1 A_1' A_0 + I_2 A_1 A_0' + I_3 A_1 A_0$$


## 8.7.2 Multiplexer with Enable Input

 

(a) Block diagram

$E$	$A_1$	$A_0$	$O$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


(b) Truth table

 

$$O = I_0 E' A_1' A_0' + I_1 E' A_1' A_0 + I_2 E' A_1 A_0' + I_3 E' A_1 A_0$$


### 8.7.4 Expansion of Multiplexer

Implementation of 16X1 MUX with 4X1 MUX

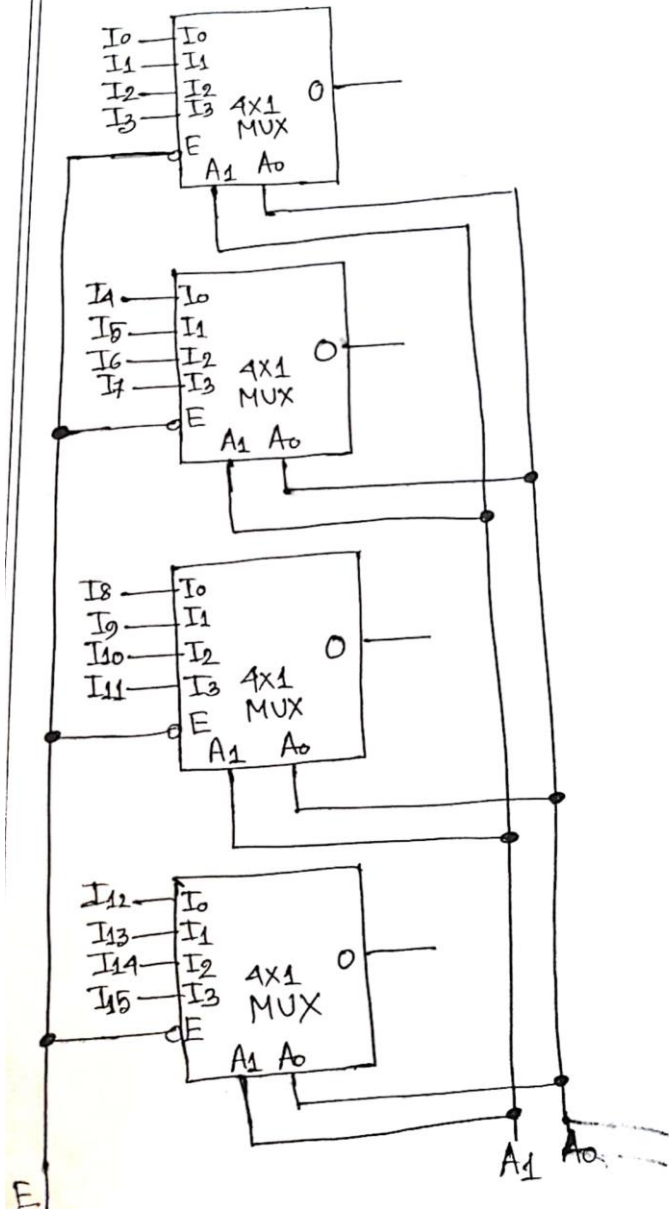


### 8.7.4 Expansion of Multiplexer


Implementation of 16X1 MUX with 4X1 MUX

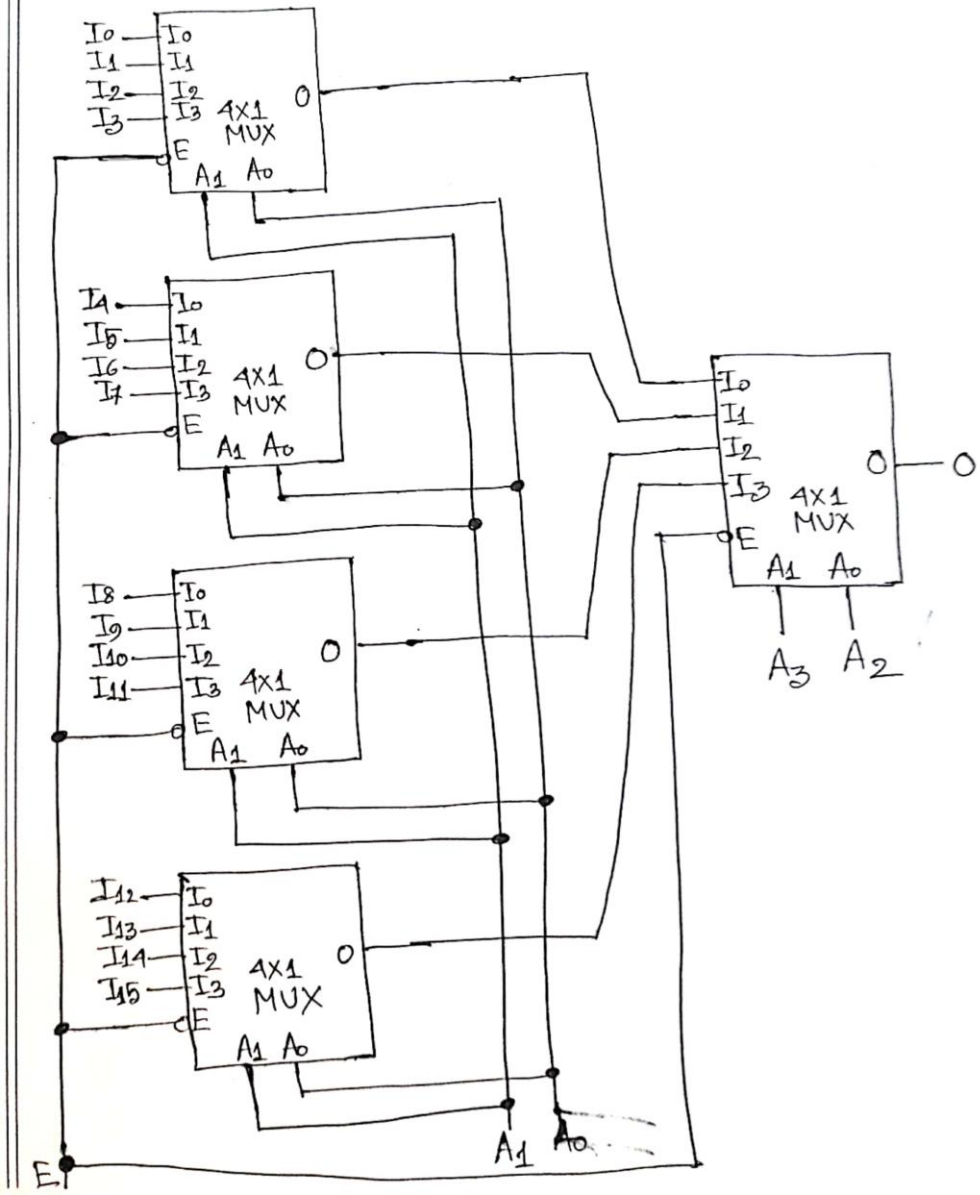


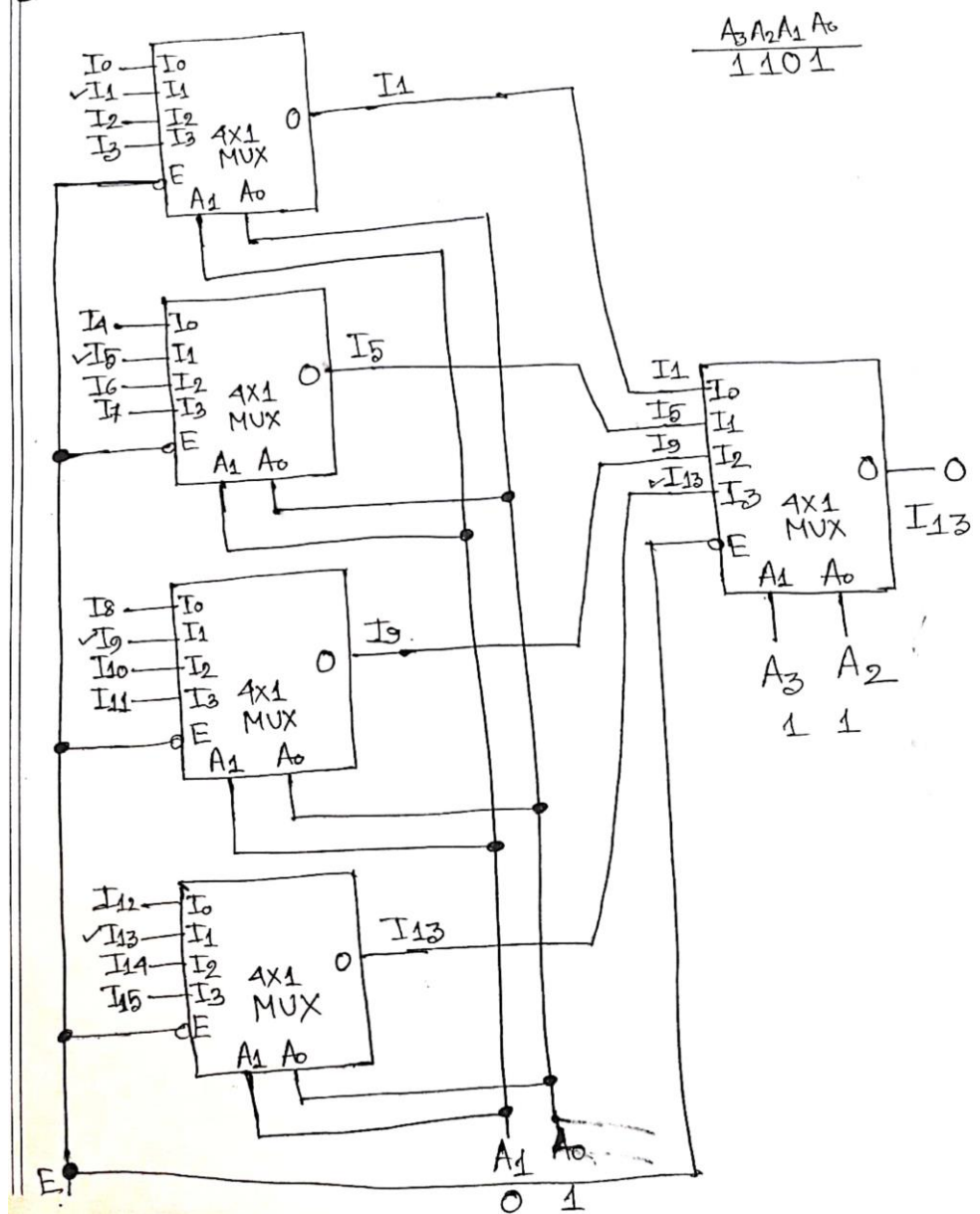
# 8.7.4 Expansion of Multiplexer Implementation of 16X1 MUX with 4X1 MUX




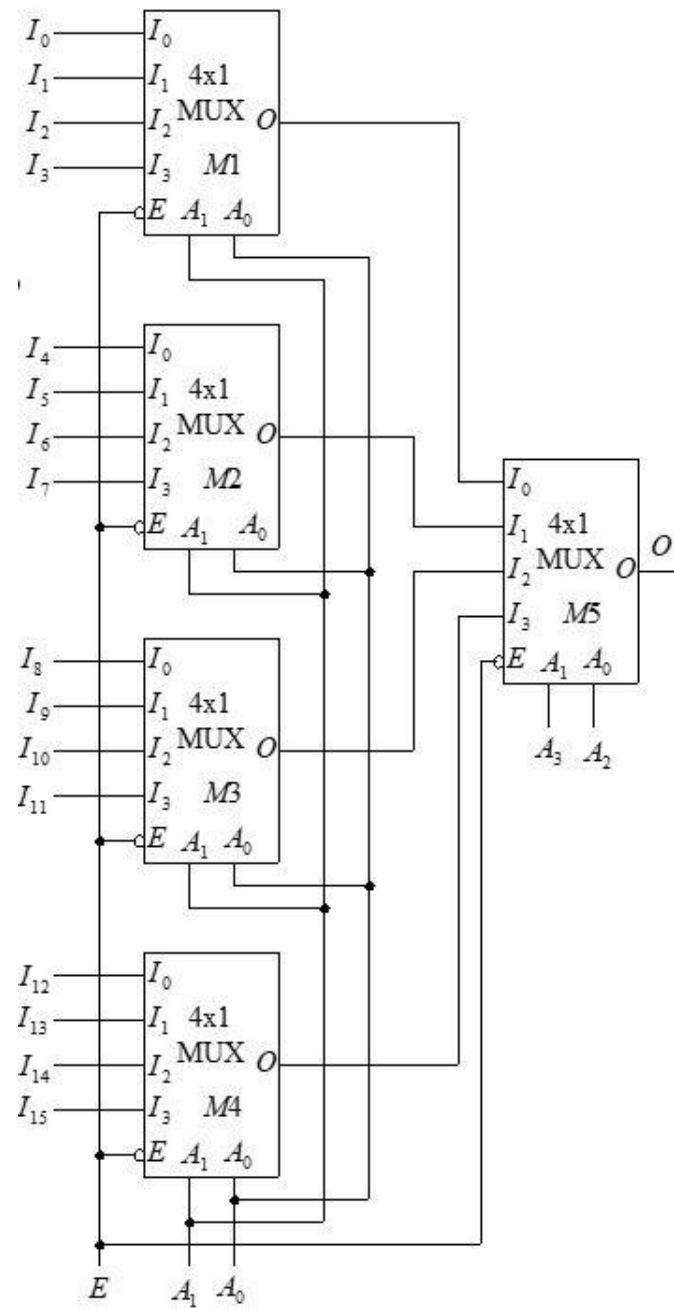



 
### 8.7.5 Combinational Logic Implementation with MUX

$$F(A, B, C, D) = \sum (0, 2, 3, 6, 8, 9, 12, 14)$$


 
### 8.7.5 Combinational Logic Implementation with MUX

$$F(A, B, C, D) = \sum (0, 2, 3, 6, 8, 9, 12, 14)$$



Binary	Minterms
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

Binary	Minterms
0000	0
1000	8

Binary	Minterms
0001	1
1001	9

0,8
1,9
2,10
3,11
4,12
5,13
6,14
7,15

$F(A, B, C, D) = \Sigma(0, 2, 3, 6, 8, 9, 12, 14)$   
Implement the function using  $8 \times 1$  MUX.

Implementation Table:

	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	0	1	2	3	4	5	6	7
$A$	8	9	10	11	12	13	14	15

$F(A, B, C, D) = \Sigma(0, 2, 3, 6, 8, 9, 12, 14)$   
 Implement the function using  $8 \times 1$  MUX.

Implementation Table:

	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	0	1	2	3	4	5	6	7
$A$	8	9	10	11	12	13	14	15
	1				0		1	0

$F(A, B, C, D) = \Sigma(0, 2, 3, 6, 8, 9, 12, 14)$   
 Implement the function using  $8 \times 1$  MUX.

Implementation Table:


	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	0	1	2	3	4	5	6	7
$A$	8	9	10	11	12	13	14	15
	1	A	$A'$	$A'$	A	0	1	0




$F(A,B,C,D) = \Sigma(0, 2, 3, 6, 8, 9, 12, 14)$   
 Implement the function using 8x1 MUX.

Implementation Table:

	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	0	1	2	3	4	5	6	7
$A$	8	9	10	11	12	13	14	15
	1	A	$A'$	$A'$	A	0	1	0

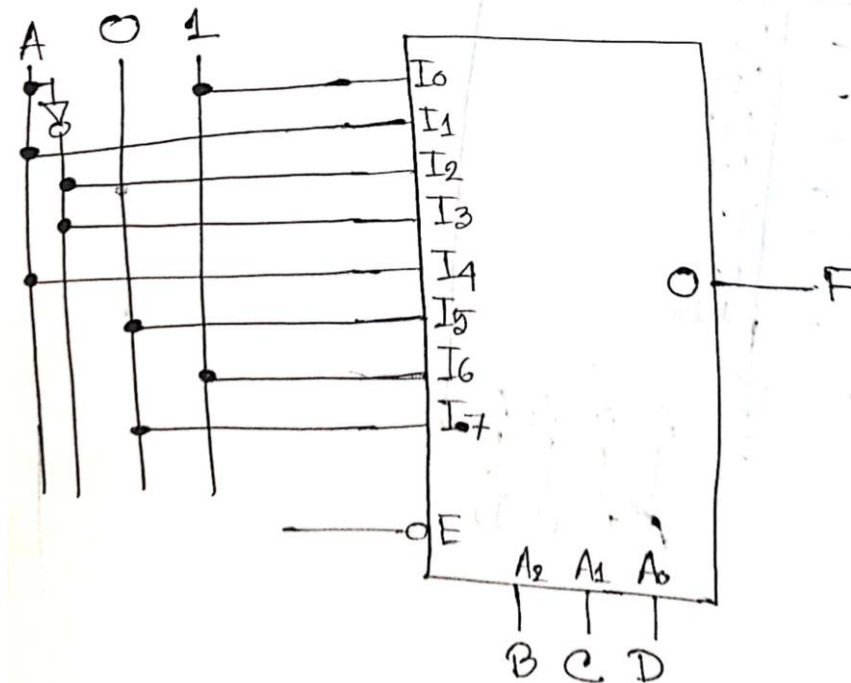

$$F(A, B, C) = \sum (1, 3, 5, 6)$$

 

(a) Implementation with multiplexer

Minterm	$A$	$B$	$C$	$F$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

(b) Truth table


	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	①	2	③
$A$	4	⑤	⑥	7
	0	1	$A$	$A'$

(c) implementation table

$$F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$$

	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	①	②	2	③	④	5	6	7
$A$	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	$A'$	$A'$	0	0	$A$

(a) Implementation table

 

(b) Implementation with multiplexer