



EAST WEST UNIVERSITY

Department of Computer Science and Engineering

B.Sc. in Computer Science and Engineering Program


Mid Term II Examination, Fall 2020 Semester

Course: CSE 345 Digital Logic Design, Section-3
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 40 (20 will be counted for final grading)
Time: 1 Hour and 30 Minutes (Including Submission)

Note: There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Consider that $ABCD$ is a 4-bit input and X is a 1-bit output of a combinational circuit. The output is $X = 1$ if the input contains odd number of 1s; otherwise $X = 0$. **Design** the combinational circuit. [CO3,C3, Mark: 6]

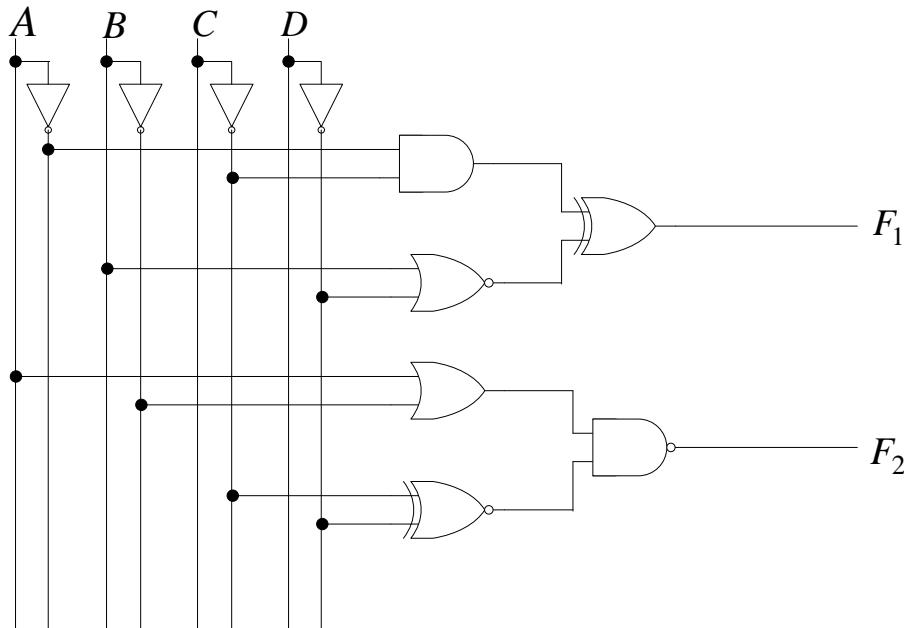2. **Analyze** the following circuit by constructing truth table of the outputs. [CO2,C4, Mark: 8]



3. **Design** a full-adder using only AND, and OR gates. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C3, Mark: 6]
4. **Design** a Binary-to-Hexadecimal Decoder for active-HIGH output. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C6, Mark: 6]

5. Given that 8×1 MUXs are available. Design a 32×1 MUX using necessary number of 8×1 MUXs. [Properly label all inputs and outputs] [CO3,C6, Mark: 6]

6. **Write** a Procedural Verilog description using case statement for implementing a 2×4 Decoder with active-HIGH Enable input and active-LOW outputs. [CO3,C6, Mark: 8]