




EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Final Examination, Fall 2021 Semester

Course: CSE 345 Digital Logic Design, Section-2
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 40 (20 will be counted for final grading)
Time: 1 Hour and 25 Minutes (Including submission)

Note: There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.


1. **Write down** next state and output equations for the following sequential circuit. From these equations **analyze** the sequential circuit and draw the transition diagram.

[CO2,C4,
EP1,
Mark: 8]

 

2. **Design** a sequential circuit represented by the following state diagram using S-R flip-flop.

[CO3,C3,
EP1,EP2,
Mark: 8]

 

3. **Design** a 5-bit serial-in parallel-out bi-directional shift register using D flip-flops. [Draw its block diagram, and logic diagram] [CO3,C6, Mark: 8]
4. **Design** a $\div 4$ synchronous up/down counter using T flip-flops. [Draw its block diagram, transition diagram, excitation table, equation, and logic diagram] [CO3,C6, Mark: 8]
5. **Design** a synchronous sequential circuit represented by the following state diagram using explicit style Verilog code. Assume a negative-edge clock. Also assume that reset will be done when the reset signal will go from 0 to 1. [CO3,C6, EP1,EP2, Mark: 8]

