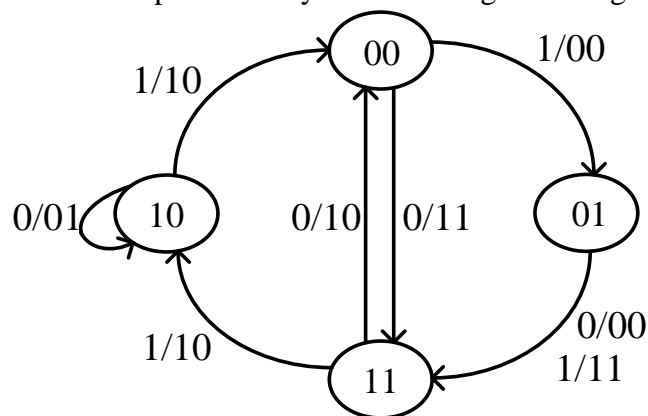


Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Final Examination, Fall 2020 Semester

Note: There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.



3. **Design** a 3-bit serial-in serial-out bi-directional shift register using D flip-flops. [Draw its block diagram, and logic diagram] [CO3,C6, Mark: 8]
4. **Design** a $\div 16$ synchronous up counter using T flip-flops. [Draw its block diagram, transition diagram, excitation table, equation, and logic diagram] [CO3,C6, Mark: 8]
5. **Design** a synchronous sequential circuit represented by the following state diagram using explicit style Verilog code. Assume a positive-edge clock. Also assume that reset will be done when the reset signal will go from 1 to 0. [CO3,C6, Mark: 8]

