



EAST WEST UNIVERSITY

Department of Computer Science and Engineering

B.Sc. in Computer Science and Engineering Program


Mid Term II Examination, Summer 2021 Semester

Course: CSE 345 Digital Logic Design, Section-3
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 40 (20 will be counted for final grading)
Time: 1 Hour and 30 Minutes (Including Submission)

Note: There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Consider that $ABCD$ is a 4-bit input and X is a 1-bit output of a combinational circuit. The output is $X = 1$ if the input contains even number of 1s; otherwise $X = 0$. **Design** the combinational circuit. [CO3,C3, Mark: 6]

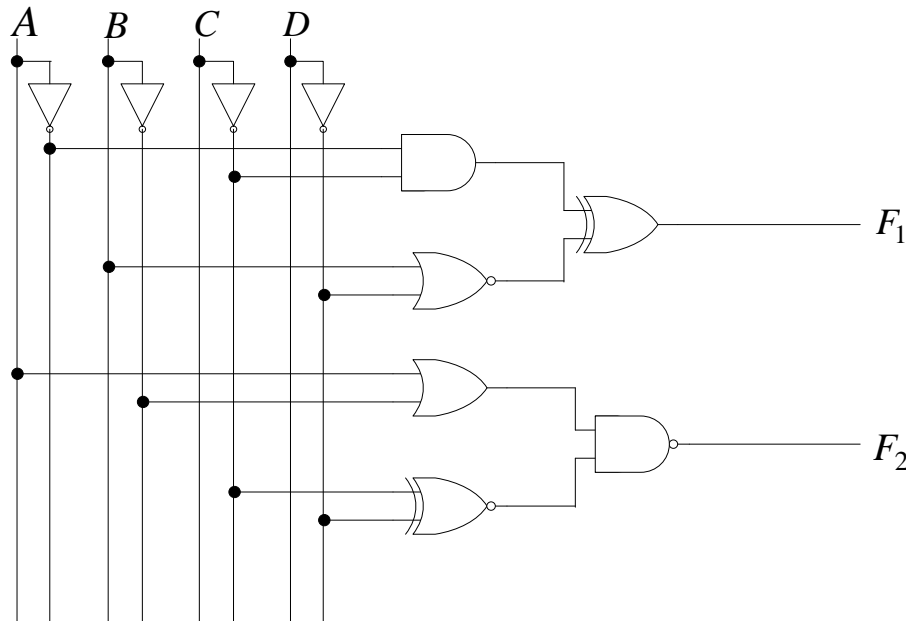2. **Analyze** the following circuit by constructing truth table of the outputs. [CO2,C4, Mark: 8]



3. **Design** a full-adder using only AND, and OR gates. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C3, Mark: 6]
4. **Design** a Binary-to-Hexadecimal Decoder for active-LOW output. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C6, Mark: 6]

5. **Construct** a combinational circuit using an 8×1 MUX for implementing the following Boolean function. [Properly label all the inputs and outputs] [CO3,C6, Mark: 6]

$$F(A, B, C, D) = \prod (0, 3, 6, 9, 12, 13, 15)$$

6. **Write** a Procedural Verilog description using case statement for implementing a 2×4 Decoder with active-LOW Enable input and active-HIGH outputs. [CO3,C6, Mark: 8]