



East West University
Department of Computer Science and Engineering
CSE 109/209 –Electrical Circuits, Section: 05
Semester: Fall 2021

Quiz 1

Name:			Id:
Duration: 25 minutes	Date: 10/11/2021	Total Mark: 10	Mark Obtained:

1. From the following figure, **calculate**

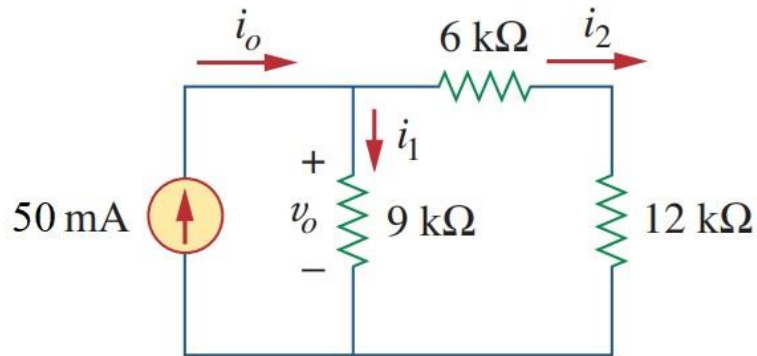


Figure: 01

- (a) the voltage, v_o
- (b) the power supplied by the current source
- (c) the power absorbed by each resistor.