



# East West University

## Department of CSE

### LAB REPORT

**Course Code and Name:**  
CSE 209 ; ELECTRICAL CIRCUIT

**Experiment no: 02**  
**Group no: 01**

**Experiment name:**  
Series-Parallel DC Circuit and Verification of Kirchhoff's Laws

**Name of students & Id:**

1. B M Sharhia Alam	ID: 2021-3-60-016
2. Sidratul Moontaha	ID: 2021-3-60-048
3. Antara Sarkar Rupa	ID: 2021-3-60-056

**Course Instructor information:**  
M Saddam Hossain Khan(SHK)  
Senior Lecturer  
Department of Computer Science and Engineering  
East West University

**Date of Report Submitted:**

## **ABSTRACT:**

This lab experience name is “Series-Parallel DC Circuit and Verification of Kirchhoff’s laws”. For doing this lab simulation firstly we should open our PSpice software and draw a diagram figure-4 and simulate the values of V<sub>1</sub>, V<sub>2</sub>, V<sub>3</sub>, I<sub>1</sub>, I<sub>2</sub>, and I<sub>3</sub>. Then we have to calculate the values V<sub>1</sub>, V<sub>2</sub>, V<sub>3</sub>, I<sub>1</sub>, I<sub>2</sub>, and I<sub>3</sub> and compare the simulated value and calculated value.

## **OBJECTIVE:**

1. Dc series-parallel circuit is analyzed to learn.
2. Kirchhoff’s Voltage Law (KVL) is verified.
3. Kirchhoff’s Current Law (KCL) is verified.

## **THEORY AND EXPERIMENTAL METHODS:**

Kirchhoff’s Voltage Law (KVL) states that the sum of the voltage rises around a closed path is equal to the sum of the voltage drops. The KVL can be written in the following mathematical form:

$$\sum V_{\text{rises}} = \sum V_{\text{drops}}$$


Kirchhoff’s Current Law (KCL) states that the sum of the currents entering a node of a circuit is equal to the sum of the currents leaving the node. The KCL can be written in the following mathematical form:

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

A series-parallel circuit is one that is formed by a combination of series and parallel resistors. For solving series-parallel circuits, parallel combinations of resistors and series combinations of resistors are clearly identified. Then series-

parallel reduction method is used to determine the values of the circuit variables.

### CIRCUIT DIAGRAM:

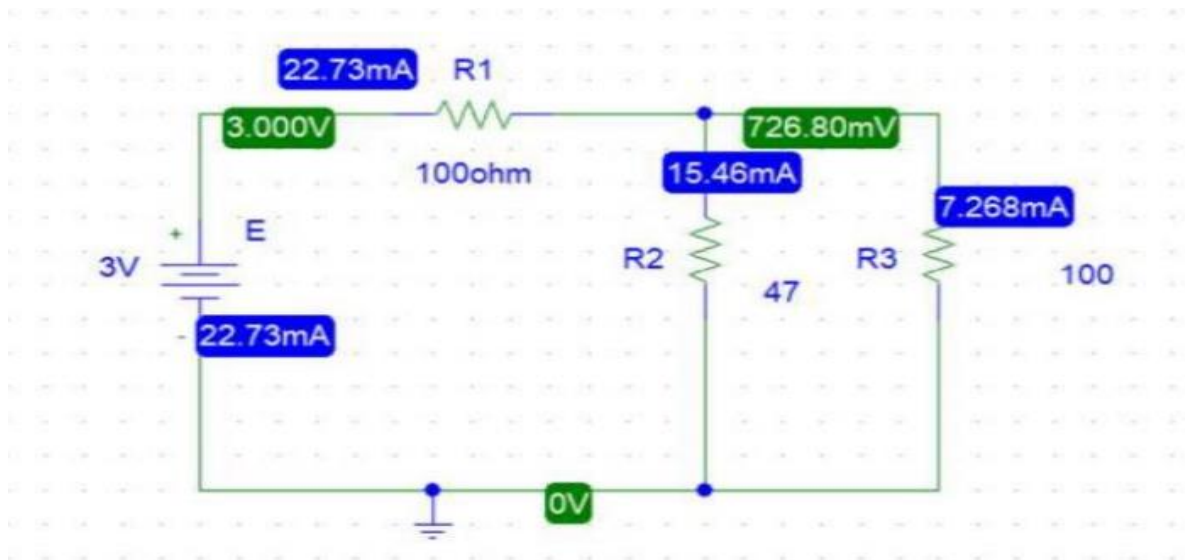

### EQUIPMENTS AND COMPONENTS NEEDED:

1. DC power supply
2. DC voltmeter
3. DC ammeter
4. Multimeter
5. Resistor 100  $\Omega$  (two) and 47  $\Omega$  (one)
6. Breadboard
7. Connecting wires

### LAB PROCEDURE:

From the simulated data,

1.  $V_2 = V_3 = 0.73\text{V}$
2.  $E = V_1 + V_2 = (2.27 + 0.73)\text{V} = 3\text{V}$
3.  $I_1 = I_2 + I_3 = (16 + 8)\text{mA} = 24\text{mA} \approx 23.5\text{mA} = I_1$

**Table 1. Experimental Datasheet**

Group (01)


Table 01 : Experimental Datasheet :

Measured value of $E(V)$	Measured value of $V_1(V)$	Measured value of $V_2(V)$	Measured value of $V_3(V)$	Measured value of $I_1(mA)$	Measured value of $I_2(mA)$	Measured value of $I_3(mA)$	Measured value of Resistance ( $\Omega$ )
3	2.27	0.73	0.73	23.5	16	8	$R_1$ $= 0.09$  $R_2$ $= 0.04$  $R_3$ $= 0.09$

Name : ~~Sha~~ B M Shahrul Atam  
 ID : 2021-3-60-016

Name : Sidratul Moontaha  
 ID : 2021-3-60-048

Name : Antara Sarkan Rupa  
 ID : 2021-3-60-056

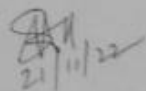  
 21/11/22

① From the Data sheet, we can see

$$V_2 = 0.73V, V_3 = 0.73V$$

~~(i)  $E = 2.27 + 0.73$~~

$$\begin{aligned} \textcircled{ii} E &= V_1 + V_2 \\ &= 2.27 + 0.73 \\ &= 3V \end{aligned}$$

$$\textcircled{iii} I_1 = I_2 + I_3$$

$$\Rightarrow 23.5 = 16 + 8$$

$$\Rightarrow 23.5 \approx 24 \text{ mA}$$

## RESULTS AND DISCUSSIONS:

Here, we can see that the theoretical values and the experimental values are the same. So, we can say there are no discrepancies between the simulated value and the calculated value.

## POST-LAB SOLUTION:

1.

Here,

$$R_1 = 100\Omega,$$

$$R_2 = 47\Omega,$$

$$R_3 = 100\Omega$$

From ohm's law we know that,

$$V = IR$$

$$\text{Or, } I = V/R$$

Here,

$R_1$  and  $R_2$  is in parallel,

$$R_p = 47 * 100 / 47 + 100 = 4700 / 147 = 31.97\Omega$$

Then,  $R_p$  and  $R_1$  is in series,

$$R_{eq} = 100 + 31.97 = 131.97\Omega$$

Here,

$$E = 3V$$

$$\text{and } R_{eq} = 131.97\Omega$$

$$\text{So, } I_1 = 3 / 131.97 = 0.0227A = 22.73mA$$

$$V_1 = I_1 R_1 = 0.0227 * 100 = 2.27V$$

Here, Applying KVL,  $V_2$  and  $V_3$  are parallel so their value will be the same,

$$V_2 = V_3 = I_1 R_{eq} = 0.0227 * 131.97 = 3.00V$$

$$I_2 = V_2 / R_2 = 3.00 / 47 = 0.015A$$

$$I_3 = V_2 / R_3 = 3.00 / 100 = 0.03A$$

So, we can say that there is no discrepancy found because all the value of  $I_1$ ,  $I_2$ ,  $I_3$  and  $V_1$ ,  $V_2$ ,  $V_3$  are the same with measured values by Pspice simulation.

2.

(i) We know that from KVL that two different value of voltage cannot be connect in parallel. If they are connecting in parallel then their value will be same.

$$-V_2 + V_3 = 0$$

$$\text{Or, } V_2 = V_3$$

Calculating  $V_2$  and  $V_3$ ,

$$V_2 = I_2 R_2 = 0.01546 * 47 V = 0.727V$$

$$V_3 = I_3 R_3 = 0.00703 * 100 V = 0.703V$$

$$\text{So, } V_2 = V_3 \text{ (Shown)}$$

(ii) From KVL we can calculate that,

Total sum of rising voltage and dropping voltage = 0

$$\text{Or, } -E + V_1 + V_2 = 0$$

$$\text{Or, } 3 = V_1 + V_2$$

From Question 1, we know,  $V_1 = 2.273\text{V}$  and  $V_2 = 0.7268$

$$V_1 + V_2 = 2.99$$

$$\text{Or, } V_1 + V_2 = 3 \text{ (Showed)}$$

(iii) From KCL we can calculate the Total sum of entering current and leaving current = 0

$$\text{Or, } I_1 = I_2 + I_3$$

From Question 1, we know,

$$I_2 + I_3 = (0.01546 + 0.00703)$$

$$\text{Or, } I_2 + I_3 = 0.022 = I_1$$

$$I_1 = I_2 + I_3 \text{ (Showed)}$$



**Conclusion:** In this experiment, we verified the Kirchhoff's current law (KCL) and Kirchhoff's voltage law (KVL). Here for measuring current, we connected ammeter (Iprobe) in series with the resistors. For measuring voltage, we connected the bubbles across with the resistors. After getting all the voltages and currents then we can easily verify the Kirchhoff's current law and Kirchhoff's voltage law.

## PRE-LAB SOLUTION:

Name : B M Shahrzia Alam  
ID: 2021-23-60-016  
Course: 209 (?)  
Lab: 2
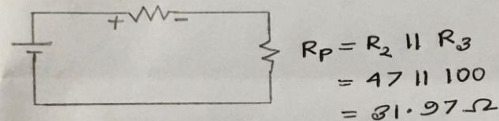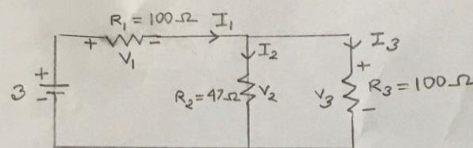
### Lab-2 Pre lab report

- Q. Theoretically calculate the values of  $V_1$ ,  $V_2$ ,  $V_3$ ,  $I_1$ ,  $I_2$  and  $I_3$  for the circuit of figure 4 with  $E = 3V$ .



$$\begin{aligned}\therefore R_{eq} &= R_1 + R_P \\ &= (100 + 31.97) \Omega \\ &= 131.97 \Omega\end{aligned}$$

Here,  $E = 3V$

$$\text{we know, } I_1 = \frac{V}{R_{eq}} = \frac{3}{131.97} = 0.0227 A$$

$$\begin{aligned}\text{Now, } V_1 &= I_1 R_1 \\ &= (0.0227 \times 100) V \\ &= 2.27 V\end{aligned}$$

Applying C.D.R -

$$\begin{aligned}I_2 &= \frac{R_3}{R_2 + R_3} \times I_1 \\ &= \frac{100}{47 + 100} \times 0.0227 \\ &= 0.015 A\end{aligned}$$



$$\begin{aligned}\therefore V_2 &= I_2 R_2 \\ &= 0.015 \times 47 \\ &= 0.703 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Now, } I_3 &= \frac{R_2}{R_2 + R_3} \times I_1 \\ &= \frac{47}{47 + 100} \times 0.0227 \\ &= 0.00703 \text{ A}\end{aligned}$$

$$\begin{aligned}\therefore V_3 &= I_3 R_3 \\ &= 0.00703 \times 100 \\ &= 0.703 \text{ V}\end{aligned}$$

$$\begin{array}{ll}\text{So, } V_1 = 2.27 \text{ V} & I_1 = 0.0227 \text{ A} \\ V_2 = 0.703 \text{ V} & I_2 = 0.015 \text{ A} \\ V_3 = 0.703 \text{ V} & I_3 = 0.00703 \text{ A}\end{array}$$

**Q.2:** From the calculated values, show that (i)  $V_2 = V_3$  ;

(ii) KVL holds, that is  $E = V_1 + V_2$

(iii) KCL holds, that is  $I_1 = I_2 + I_3$

(i) Applying KVL at loop 2 -

$$\begin{aligned}-V_2 + V_3 &= 0 \\ \therefore V_2 &= V_3\end{aligned}$$

Also, from calculated value,

$$V_2 = I_2 R_2 = 0.703$$

$$V_3 = I_3 R_3 = 0.703$$

$$\therefore V_2 = V_3 \quad [\text{Showed}]$$

(ii) Applying KVL at loop 1;

$$-3 + V_1 + V_2 = 0$$

$$\Rightarrow V_1 + V_2 = 3$$

from (i) we get -

$$V_1 = 2.27 \text{ V}$$

$$V_2 = 0.703 \text{ V}$$

$$\therefore V_1 + V_2 = 2.27 + 0.703$$

$$= 2.97$$

$$\approx 3 \text{ V}$$

$$= E$$

[Showed]

(iii) Applying KCL at 1 -

from (i) we get,

$$I_2 = 0.015 \text{ A}$$

$$I_3 = 0.00703 \text{ A}$$

$$\text{So, } I_1 = I_2 + I_3$$

$$= (0.015 + 0.00703) \text{ A}$$

$$= 0.02203 \text{ A}$$

$$= I_1$$

[Showed]





Name:- Sidratul Moontaha

ID:- 2021-3-60-048

Q.11 Theoretically calculate the values of  $V_1, V_2, V_3, I_1, I_2, I_3$  of the circuit of figure 4 with  $E = 3V$ .

Ans:-

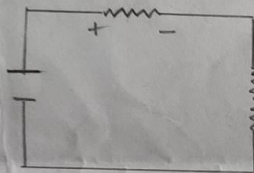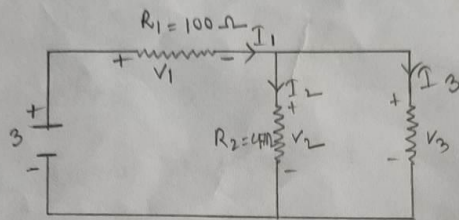

$$R_p = R_2 \parallel R_3 \\ = 47 \parallel 100 = 31.97 \Omega$$

$$R_{eq} = R_1 + R_p \\ = (100 + 31.97) = 131.97 \Omega$$

Here,  $E = 3V$

$$\text{we know, } I_1 = \frac{V}{R_{eq}} = \frac{3}{131.97} = 0.0227A$$

$$\text{Now, } V_1 = I_1 R_1$$

$$= (0.0227 \times 100) = 2.27V$$

$$\text{Applying C.D.R :- } \frac{R_3}{R_2 + R_3} \times I_1$$

$$= \frac{100}{47 + 100} \times 0.0227$$

$$= 0.015A$$

$$V_2 = I_2 R_2$$

$$= 0.015 \times 47 = 0.703V$$

$$I_3 = \frac{R_2}{R_2 + R_3} \times I_1$$

$$= \frac{47}{47 + 100} \times 0.0227 = 0.00703 \text{ A}$$

$$V_3 = I_3 R_3 = 0.00703 \times 100 = 0.703 \text{ V}$$

Q. 21 From the calculated values, show that, i)  $V_2 = V_3$ ,  
ii) KVL holds, that is  $E = V_1 + V_2$ , iii) KCL holds, that is  $I_1 = I_2 + I_3$

i) Applying KVL at loop 2,

$$-V_2 + V_3 = 0$$

$$\Rightarrow V_2 = V_3$$

From calculated values,  $V_2 = 0.703 \text{ V}$ ,  $V_3 = 0.703 \text{ V}$

$$\therefore V_2 = V_3 \text{ (shown)}$$

ii) Applying KVL at loop 1,

$$-3 + V_1 + V_2 = 0$$

$$\Rightarrow V_1 + V_2 = 3$$

$$\Rightarrow 2.27 + 0.703 = 3$$

$$\Rightarrow 2.97 \approx 3 \text{ V} = E \text{ (shown)}$$

iii) Applying KCL at 1 →

$$I_1 = I_2 + I_3$$

$$= (0.015 + 0.00703) \text{ A}$$

$$= 0.02203 \text{ A}$$

$$= I_1$$

$$I_2 + I_3 = 0.015 + 0.00703 = 0.02203 \text{ A}$$

— 0 — (shown)



Name: Antara Sankar Rupa.

ID : 2021-3-60-056

Group no: 01

Ques: (1) Theoretically calculate the values of  $V_1$ ,  $V_2$ ,  $V_3$ ,  $I_1$ ,  $I_2$ , and  $I_3$  of the circuit of figure 4 with  $E = 3V$ .

⇒

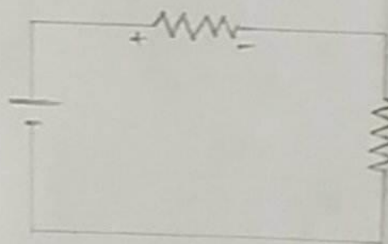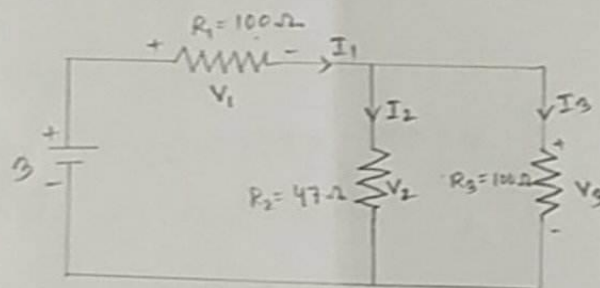

$$\begin{aligned} R_p &= R_2 \parallel R_3 \\ &= 47 \parallel 100 \\ &= 31.97 \, \Omega \end{aligned}$$

$$\begin{aligned} \therefore R_{eq} &= R_1 + R_p \\ &= (100 + 31.97) \\ &= 131.97 \, \Omega \end{aligned}$$



Hence,

$$E = 3\text{ V}$$

We know,

$$I_1 = \frac{V}{R_{eq}}$$

$$= \frac{3}{131.97}$$

$$= 0.0227\text{ A}$$

$$= 22\text{ mA}$$

$$\text{Now, } V_1 = I_1 R_1$$

$$= (0.0227 \times 100)\text{ V}$$

$$= 2.27\text{ V}$$

Applying C.D.R. —

$$I_2 = \frac{R_3}{R_2 + R_3} \times I_1$$

$$= \frac{100}{47 + 100} \times 0.0227$$

$$= 0.015\text{ A}$$

$$\therefore V_2 = I_2 R_2$$

$$= 0.015 \times 47$$

$$= 0.703\text{ V}$$

$$\begin{aligned}\text{Now, } I_3 &= \frac{R_2}{R_2 + R_3} \times I_1 \\ &= \frac{47}{47 + 100} \times 0.0227 \\ &= 0.00703 \text{ A}\end{aligned}$$

$$\begin{aligned}\therefore V_3 &= I_3 R_3 \\ &= 0.00703 \times 100 \\ &= 0.703 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{So, } V_1 &= 2.27 \text{ V} \\ V_2 &= 0.703 \text{ V} \\ V_3 &= 0.703 \text{ V}\end{aligned}$$

$$\begin{aligned}I_1 &= 0.022 \text{ A} \\ I_2 &= 0.015 \text{ A} \\ I_3 &= 0.00703 \text{ A}\end{aligned}$$

② From the calculated values, show that (i)  $V_2 = V_3$ , (ii) KVL holds, that is,  $E = V_1 + V_2$ , and (iii) KCL holds, that is,  $I_1 = I_2 + I_3$ .

$$\begin{aligned}\text{(i) Applying KVL at loop 2 —} \\ -V_2 + V_3 &= 0 \\ \Rightarrow V_2 &= V_3\end{aligned}$$

Also from calculated value,

$$V_2 = I_2 R_2 = 0.703$$

$$V_3 = I_3 R_3 = 0.703$$

$$\therefore V_2 = V_3 \quad [\text{Showed}]$$

(ii) Applying KVL at loop 1,

$$V_1 = 2.27$$

$$-3 + V_1 + V_2 = 0$$

$$\Rightarrow V_1 + V_2 = 3$$

from (i) we get —

$$V_1 = 2.27 \text{ V}$$

$$V_2 = 0.703 \text{ V}$$

$$\therefore V_1 + V_2 = 2.27 + 0.703 \\ = 2.97 \approx 3 \text{ V} = E$$

(iii) Applying KCL at 1 — [Showed]

$$I_1 = I_2 + I_3$$

$$= (0.015 + 0.00703) \text{ A}$$

$$= 0.02203 \text{ A}$$

$$= I_1$$

$$\left\{ \begin{array}{l} \text{from (i) we get-} \\ I_2 = 0.015 \text{ A} \\ I_3 = 0.00703 \text{ A} \end{array} \right.$$

[Showed]