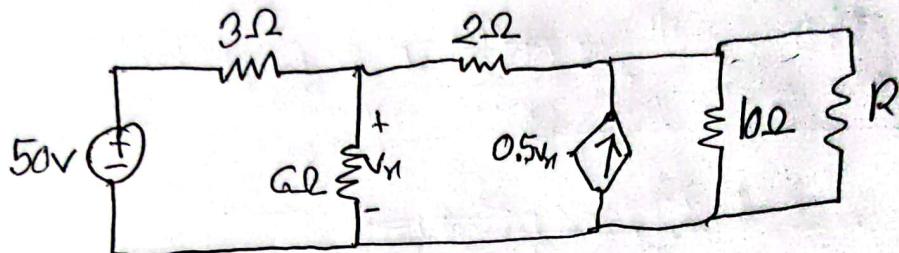


Omar Rafat Adnan

ID: 2020 - 2 - 60 - 037

Answers to the question no: 4



Apply Nodal analysis at the node A.

$$i + 0.5v_n = \left(\frac{1}{10}\right) + \left(\frac{1-v_n}{2}\right)$$

$$i + 0.5v_n = 0.1 + 0.5 - 0.5v_n$$

$$i + 0.5v_n + 0.5v_n = 0.6$$

$$i + v_n = 0.6 \quad \text{--- (1)}$$

Apply Nodal analysis at the node B.

$$\frac{v_n - v_A}{2} + \frac{v_n}{6} + \frac{v_n}{3} = 0$$

(1)

$$\frac{V_n - 1}{2} + \frac{V_n}{6} + \frac{V_n}{3} = 0$$

$$\frac{3(V_n - 1) + V_n + 2V_n}{6} = 0$$

$$\frac{6V_n - 3}{6} = 0$$

$$V_n = \frac{1}{2}V$$

$$V_n = 0.5V$$

Substitute 0.5V for V_n in eq (1)

$$1 + 0.5 = 0.6$$


$$i = 0.1A$$

Thevenin's resistance is the ratio of the test source voltage and the current it is generating. The expression for the Thevenin's resistance is

$$R_{th} = \frac{V_A}{i} = \frac{1}{0.1} = 10\Omega$$

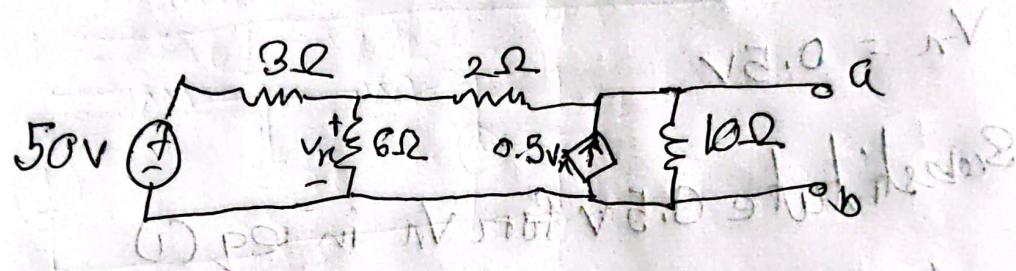(2)

Thus, the Thvenin's resistance is $\boxed{B} 10\Omega$
 The Thvenin's voltage across the a-b terminal
 due to the 50V voltage source. Label the
 nodes and redraw the circuit diagram.



Apply nodal analysis at the node with node
 voltage V_n .

$$\frac{V_n - 50}{3} + \frac{V_n}{6} + \frac{V_n - V_a}{2} = 0$$

$$\frac{2(V_n - 50) + V_n + 3(V_n - V_a)}{6} = 0$$

$$2V_n - 100 + V_n + 3V_n - 3V_a = 0$$

$$6V_n - 3V_a = 100 \quad \text{--- (2)}$$

③

Apply nodal analysis at the node a.

$$\frac{V_a - V_b}{2} + \frac{V_a}{10} = 0.5 V_b$$

$$\frac{6V_a}{10} = V_b$$

$$\frac{3}{5}V_a = V_b \quad \text{--- (3)}$$

Substitute equation (3) in eq (2)

$$6\left(\frac{3V_b}{5}\right) - 3V_b = 100$$

$$\left(\frac{18V_b - 15V_b}{5}\right) = 100$$

$$\frac{18V_b - 15V_b}{5} = 100$$

$$3V_b = 500$$


$$V_b = 166.67 \text{ V}$$

But the node voltage V_a is the voltage across the terminals a-b it is the therenin's voltage


$$V_a = V_{ab} = V_b$$

Thus the therenin's voltage is 166.67 V

Draw The resultant Thvenin circuit

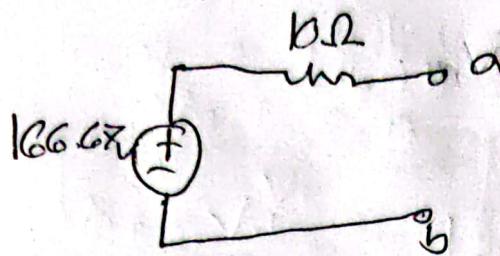


Answer to the question 05

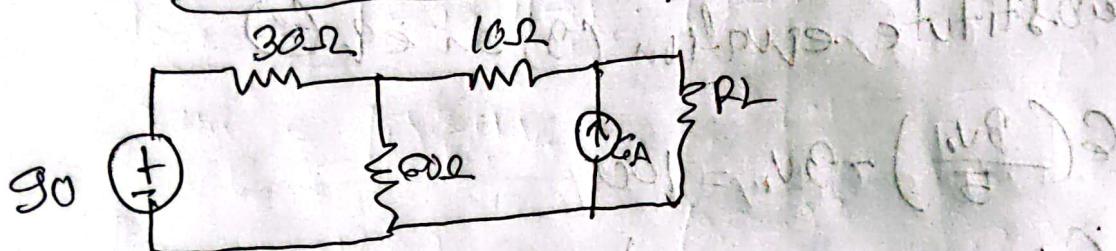

First find the R_{th} - Thvenin Resistance

C.G - Open circuit

Voltage source - Short circuit

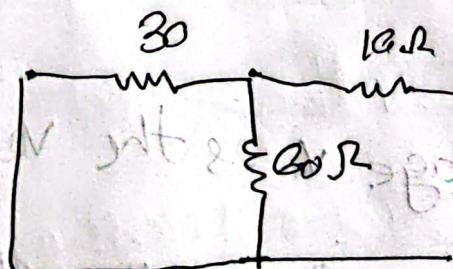

$$R_{th} = 10 + \frac{30 \times 50}{3 + 50}$$

$$R_{th} = 10 + 20$$


$$R_{th} = R_L = 30 \Omega$$

(5)

$$R_L = 30 \Omega$$

Now find the V_{AC} Thuring voltage is open circuit

Voltage

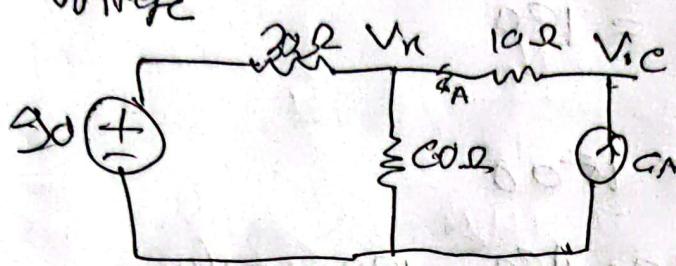

Apply nodal at point A we get to

$$\frac{V_A - 30}{30} + \frac{V_A - 0}{C_0} - \frac{V_{AC}}{G_A} = 0$$

$$2V_A - 180 + V_A = G_A \times 20$$

$$3V_A = 360 + 100 = 560$$

$$\frac{V_{AC} - V_A}{10} = 0$$

$$V_{AC} - C_0 = 30$$

$$V_{AC} = 120V$$

(a)

$$3V_R = 590$$

$$V_R = \frac{590}{3} = 180 \text{ V}$$

$$\frac{V_{OC} - V_R}{10} = 120$$

$$V_{OC} - 180 = 120$$

$$V_{OC} = 180 + 120 = 1920 \text{ V}_TH$$

$$V_{TH} = 1920 \text{ V}$$


$$R_{max} = \frac{V_{TH}^2}{4 \cdot R_m} = \frac{(1920)^2}{4 \cdot 30} = 32640$$

$$P_{max} = 32.64 \text{ kW}$$

$$S_{max} = 32.64 + 32.64 = 65.28$$

(7)

Ans to the question no: 3

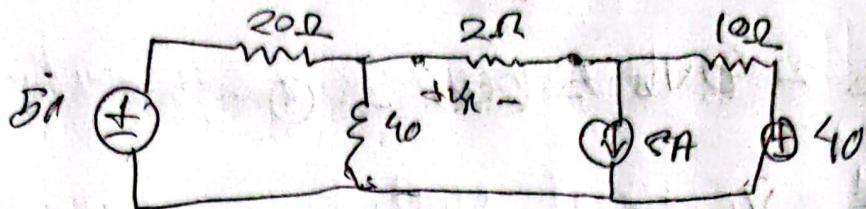


$$V_{oc} = V_a - V_b$$

40V Voltage source $\approx 10\Omega$ resistor is in series we can transform to current source

40V voltage source $\approx 10\Omega$ eni las ke

thons formed

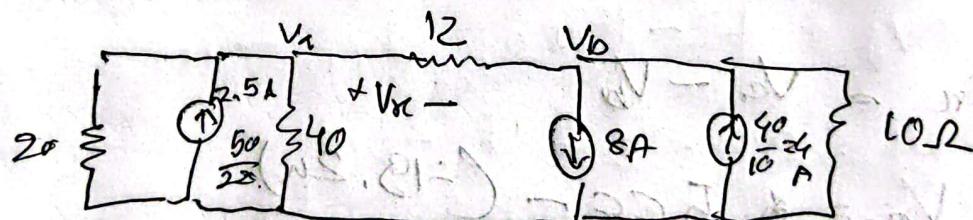

KCL At V_a

$$\frac{V_a}{20} + \frac{V_a}{40} + \frac{(V_a - V_b)}{12} = 2.5$$

$$V_a \left(\frac{1}{20} + \frac{1}{40} + \frac{1}{12} \right) - \frac{V_b}{12} = 2.5$$

$$V_a \left(\frac{3.6 + 10}{48 \times 12} \right) - \frac{V_b}{12} = 2.5$$

(8)

$$V_a \left(\frac{70}{90 \times 12} \right) - \frac{40V_b}{90 \times 12} = 2.5$$

$$70V_a - 40V_b = 1200 \quad \textcircled{1}$$

Let at V_a

$$\frac{V_b - V_a}{18} + \frac{N_o}{10} \cdot 24 \text{ V} = 0$$

$$V_b \left(\frac{10 + 12}{120} \right) - \frac{V_a}{12} = -4.0$$

$$22V_b - 10V_a = -480 \quad \textcircled{2}$$

Solve $\textcircled{1} \& \textcircled{2}$

$$V_a = 5.00 \text{ V}, V_b = -19.2 \text{ V}$$

$$V_R = V_a - V_b$$

$$V_R = 5.00 - (-19.2)$$

$$V_R = 24.2 \text{ V}$$

$$4\Omega = \frac{dV}{dI} = \frac{V_R}{10} + \frac{V_R}{10}$$


$$4\Omega = \frac{dV}{dI} = \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{10} \right)$$

$$3.0 = \frac{dV}{dI} = \left(\frac{3}{10} \right)$$

Answer to question no. 2

Case-1: When only 12V source is active and
3A current source is deactivated and replaced

by internal impedance

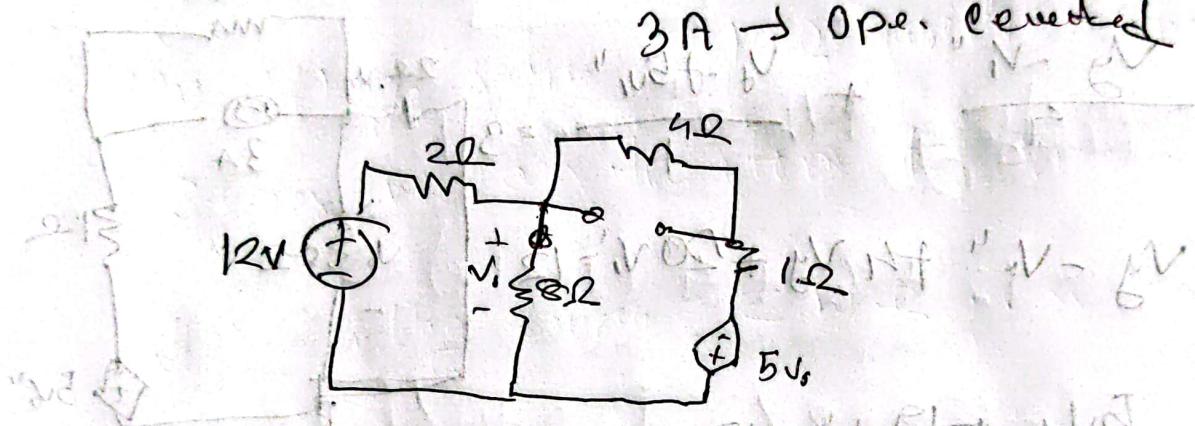

Apply KCL at node C

$$\frac{V_o' - 12}{2} + \frac{V_o' + 5V_o'}{4+1} + \frac{V_o' - 0}{8} = 0$$

$$V_o' \left(\frac{1}{2} + \frac{1}{5} + \frac{1}{8} \right) = \frac{12}{2}$$

$$V_o' \left(\frac{73}{40} \right) = \frac{12}{2}$$

$$V_o' = \frac{12}{2} \times \frac{40}{73}$$

$$V_o' = 3.28 \text{ V} \quad \text{--- (1)}$$

(1)


Case 2: When only 3A current source is
deactivated and RV source is deactivated.

i.e. $RV \rightarrow$ short circuit

Apply KCL node A:

$$\frac{V_y - V_x}{1} + \frac{V_y + 5V_x}{1} = 3$$

$$V_y - V_x + V_y + 5V_x = 12$$

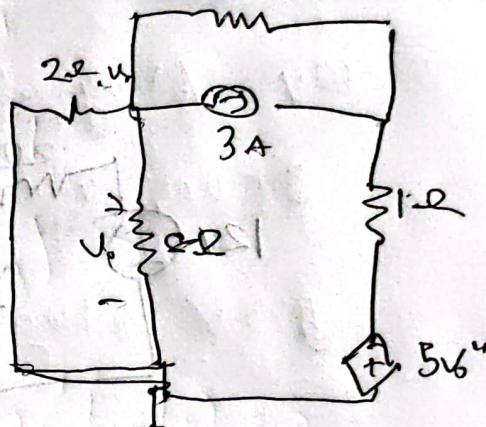

$$2V_y + 12V_x = 12$$

$$2V_y = 12 - 12V_x$$

$$V_y = 2 - 6V_x \quad \text{or} \quad V_x = \frac{2 - V_y}{6}$$

Apply KCL at node A:

$$\frac{V_o - V_y}{1} + \frac{V_o - 0}{2} + \frac{V_o - 0}{2} = -3$$

$$V_o \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{2} \right) = -3$$

put eqn ① in above equation

$$V_R'' \left(\frac{Z}{S} \right) - \frac{1}{4} (2.4 - 3.8 V_R'') = -3$$

$$V_R' \left(\frac{Z}{S} + \frac{3.8}{5} \right) = -3 + \frac{2.4}{5}$$

$$1.825 V_R' = -2.4$$

$$V_R'' = \frac{-2.4}{1.825}$$

$$V_R'' = -1.28 V_R$$

by superposition theorem

$$V_R = V_R' + V_R''$$

$$V_R = 3.2875 - 1.28$$

$$\therefore V_R = 2.0075 \text{ v. } \& V_R = 2V$$

neglect to just


$$V_R = (1 - 0.1)^2 + 0.8 \times 0.8 + (1 - 0.1) \times 0$$

$$= 0.81 + 0.64 + 0.18 = 1.63$$

or $(1 - 0.1)^2$

R

Ans for the question no. 01

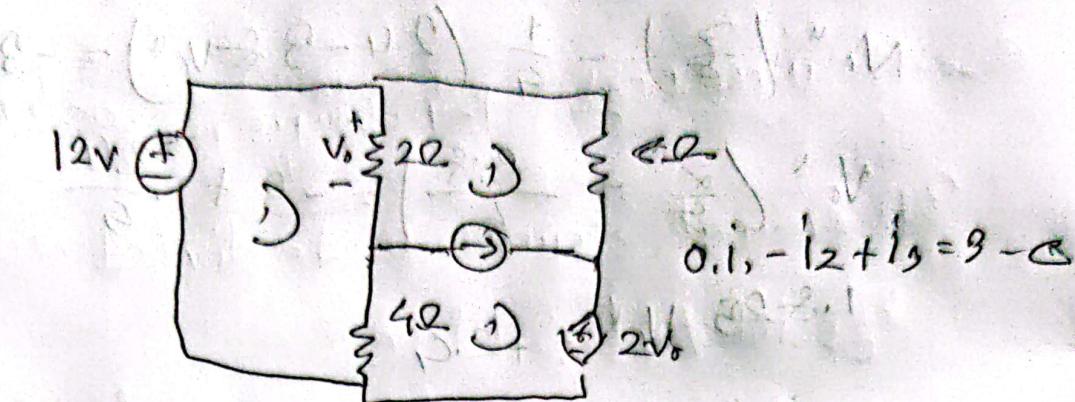

Analogy KVL at node 1.

$$-12 + V_0 + 4(i_1 - i_3) = 0$$

$$\Rightarrow -12 + 2(i_1 - i_2) + 4(i_1 - i_3) = 0$$

$$\Rightarrow -12 + 2i_1 - 2i_2 + 4i_1 - 4i_3 = 0$$

$$\Rightarrow 6i_1 - 2i_2 - 4i_3 - 12 = 0 \quad \text{--- (1)}$$

KVL at Supernode

$$2(i_2 - i_1) + 8i_2 - 2i_1 + 4(i_2 - i_1) = 0$$

$$\Rightarrow 2(i_2 - i_1) + 2.2(i_2 - i_1) + 8i_2 = 0$$

$$4(i_2 - i_1) = 0$$

(13)

$$\Rightarrow -2i_1 + 6i_2 + 4i_3 = 0 \quad \text{--- (3)}$$

Applying Cramer's rule,

$$i_1 = \frac{\begin{vmatrix} 3 & -1 & 1 \\ 12 & 2 & -4 \\ 0 & 6 & 9 \end{vmatrix}}{\begin{vmatrix} 0 & -1 & 1 \\ 6 & -2 & -4 \\ -2 & 6 & 9 \end{vmatrix}} = \frac{R_{\delta_1}}{48} = 3.5A$$

$$i_2 = \frac{\begin{vmatrix} 0 & 3 & 1 \\ 0 & 12 & -4 \\ -2 & 6 & 9 \end{vmatrix}}{\begin{vmatrix} 0 & -1 & 1 \\ 6 & -2 & -4 \\ -2 & 6 & 9 \end{vmatrix}} = \frac{-24}{48} = -0.5A$$

$$i_3 = \frac{\begin{vmatrix} 0 & -1 & 3 \\ 12 & 2 & 12 \\ 0 & 6 & 0 \end{vmatrix}}{\begin{vmatrix} 0 & -1 & 1 \\ 6 & -2 & -4 \\ -2 & 6 & 9 \end{vmatrix}} = \frac{120}{48} = 2.5A$$

(iv)