



East West University

LAB REPORT

Course Code and Name: CSE 209 ; ELECTRICAL CIRCUIT	
Experiment no: 07 Group no: Individual	
Experiment name: DC Circuit Analysis in PSpice using Source and Resistance Sweep	
Name of student & Id:	
B M Sharhia Alam	ID: 2021-3-60-016
Course Instructor information: M Saddam Hossain Khan(SHK) Senior Lecturer Department of Computer Science and Engineering East West University	
Date of Report Submitted: 26 December ,2022	

OBJECTIVE:

1. To analyze DC circuit in PSpice by sweeping source and resistance.
2. To verify maximum power transfer theorem.

INTRODUCTION:

In PSpice, DC analysis may be performed by varying the value of a DC voltage source or by varying a resistance. The results of such sweeps may be graphically viewed using the Probe tool of PSpice.

THEORY AND EXPERIMENTAL METHODS:

METHODS:

The open circuit voltage between the terminals and R_{th} is the ratio of the open circuit voltage to the short circuit current through the terminals.

CIRCUIT DIAGRAM:



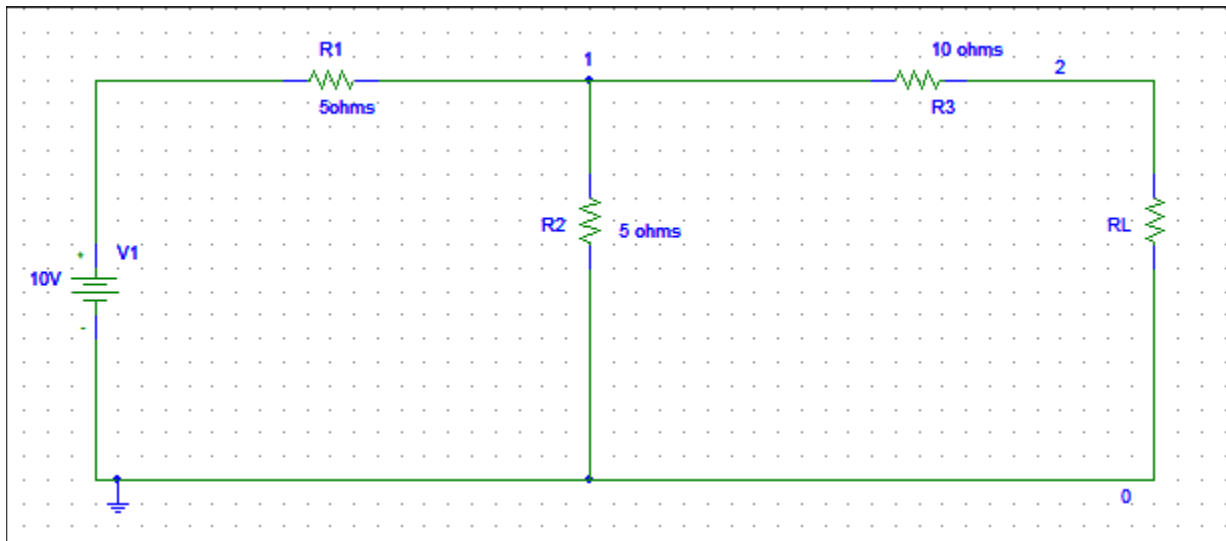


Figure 1: Example circuit.

Step: 1

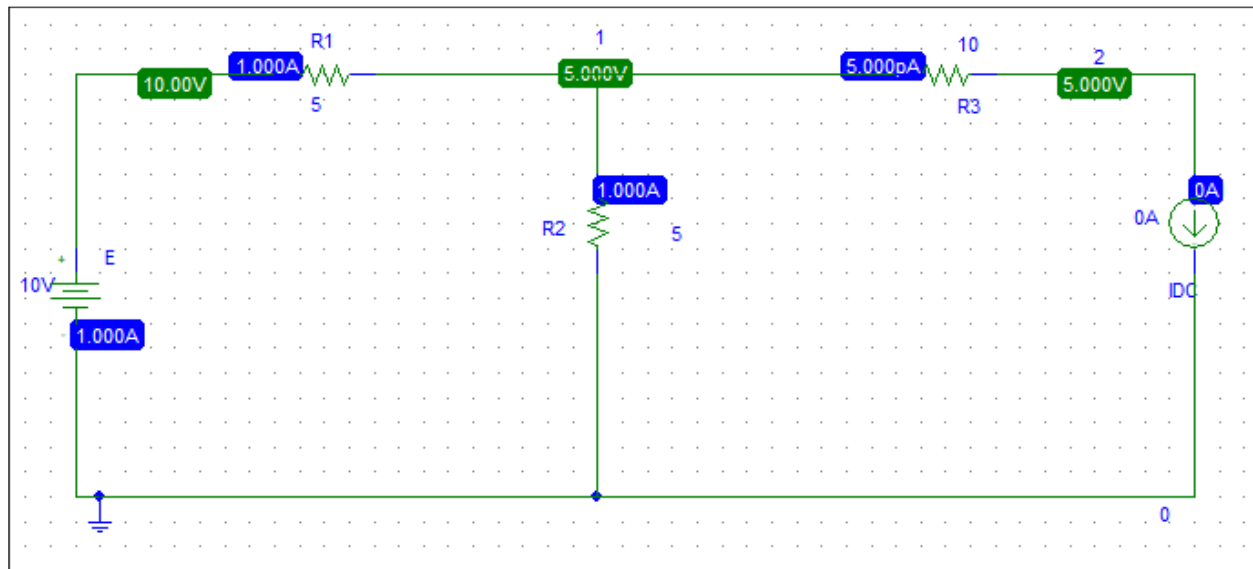

Step: 2

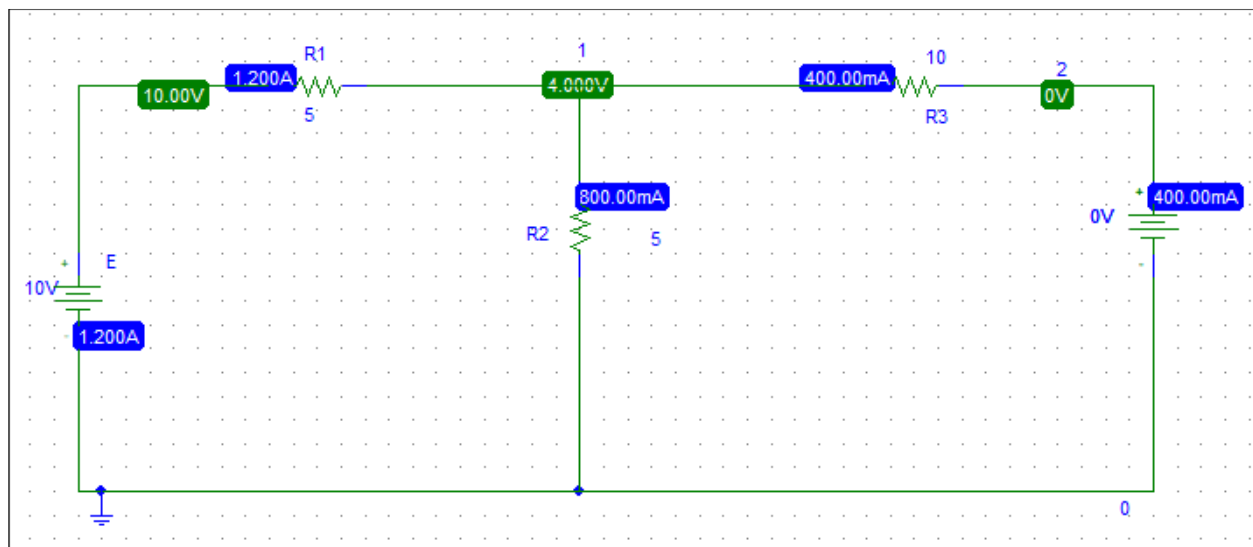


Step: 3

$$E_{th} = V_{oc} = 5V$$


$$R_{th} = V_{oc} / I_{sc} = 5 / 400 = 0.0125k = 12.5\Omega$$

$$R_L = R_{th} = 12.5\Omega$$

Step: 4

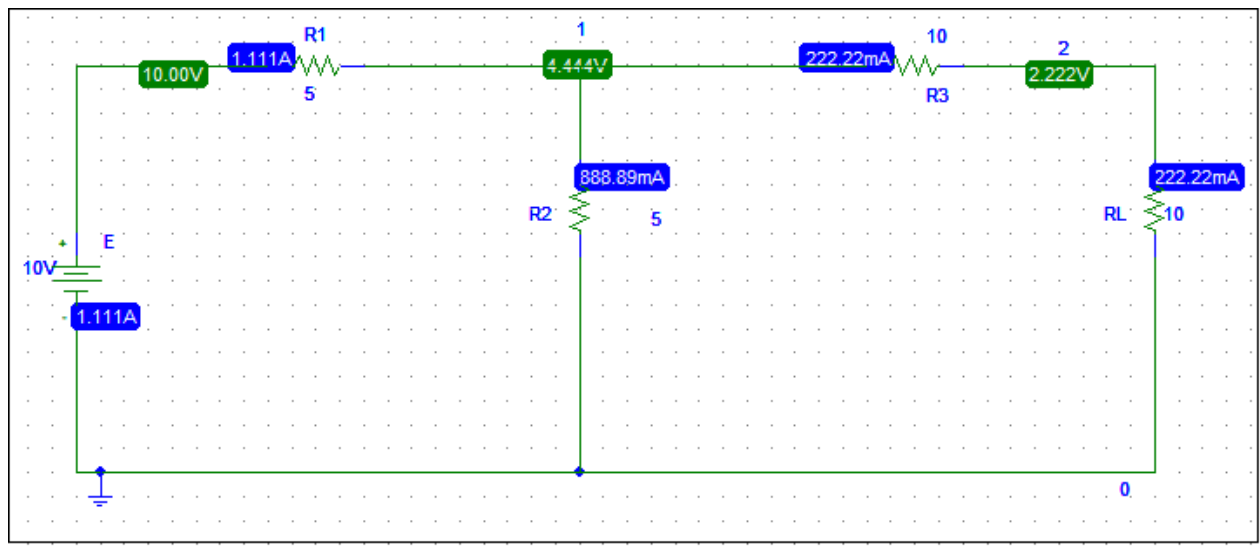


To determine V(1), V(2) and I(R3):

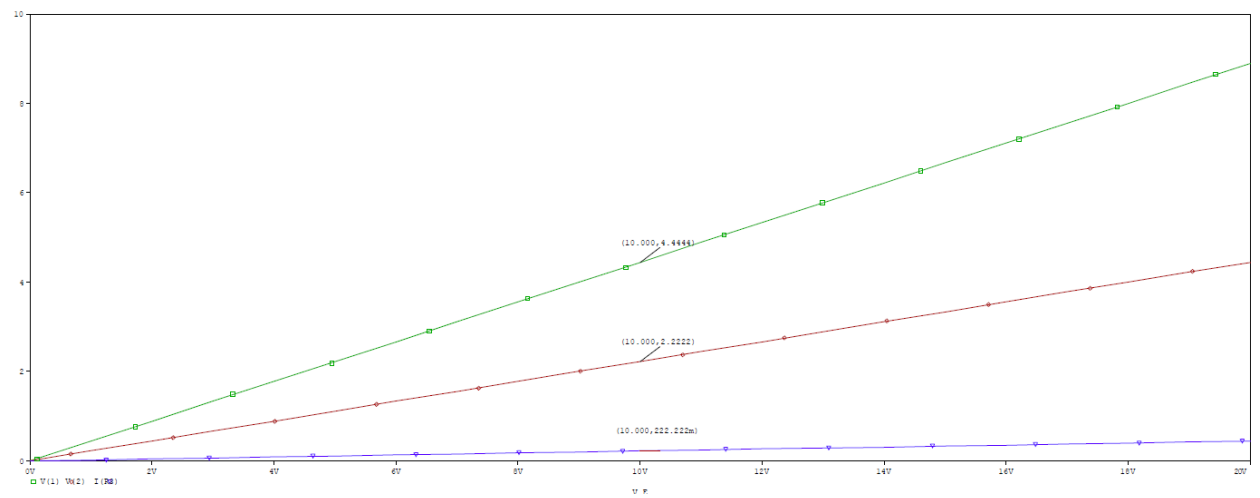


$V(1) = 4.444V$, $V(2) = 2.222V$ and $I(R3) = 222.22mA$

Step 5:

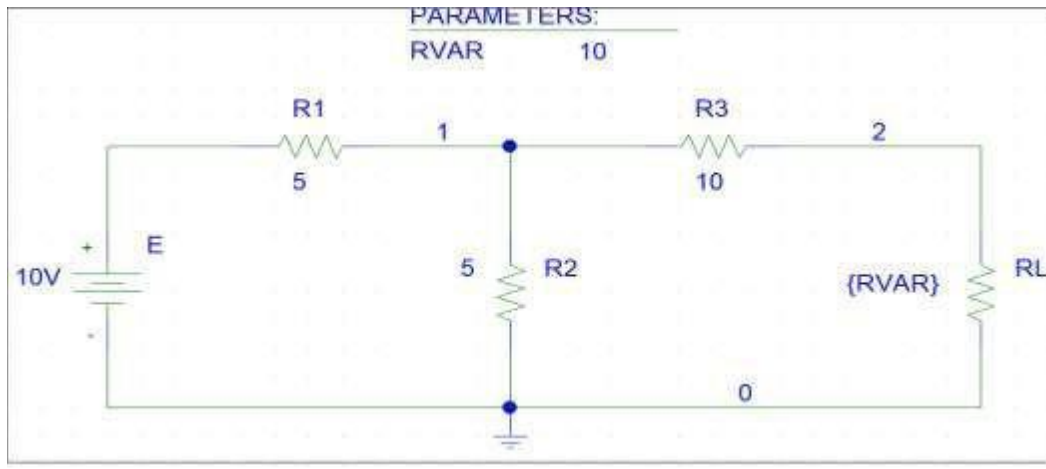


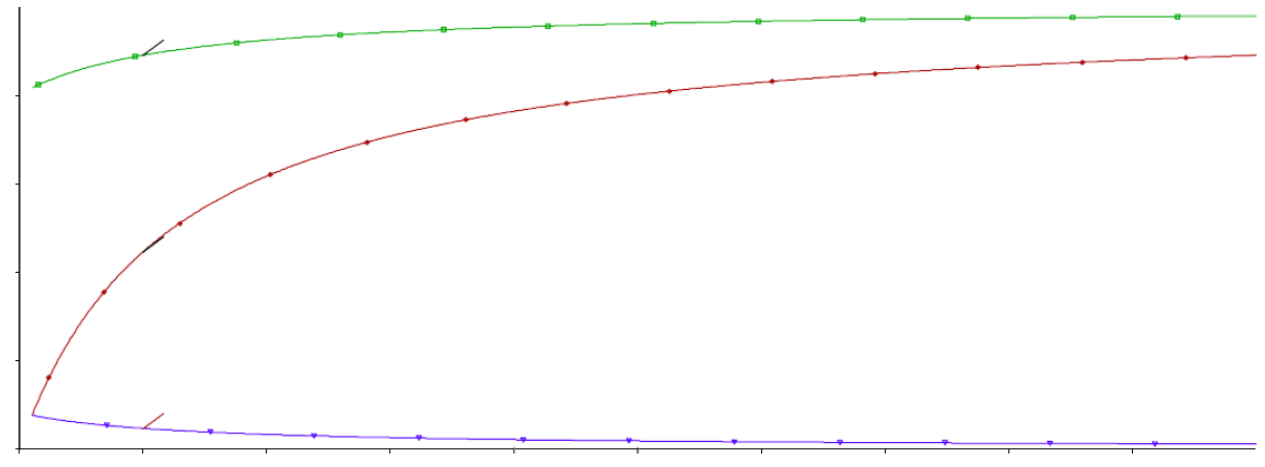Step 5(d): To determine $V(1)$, $V(2)$ and $I(R3)$ for $R = 10$ ohm:



$$V(1) = 4.444\text{V}, V(2) = 2.222\text{V} \text{ and } I(R3) = 222.22\text{mA}$$

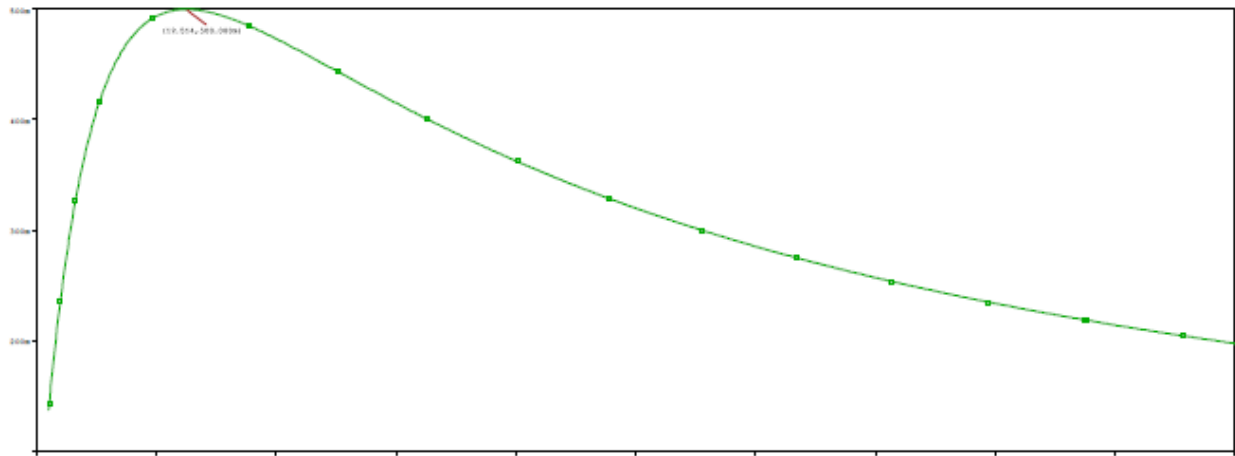Step 5(e): Graph to determine the maximum value of the load power and the value of $R_L = 12.5$ Maximum value of the load power, $P_{L\max} = 5\text{W}$



Post-Lab Report Answers:

Answers to the questions no: 01

Comparing the values of V(1), V(2) and I(R3) obtained in steps 4 and 5(d):

	Step-4	Step-5(d)
V(1)	4.444V	4.444V
V(2)	2.222V	2.222V
I(R3)	222.22mA	222.22mA

So, here is no difference between the step 4 and step 5(d) values.

Answers to the questions no: 02

From step 2,

Load resistance = 12.5

From step 5(e),

Load resistance = 12.5

Comparing the load resistance for maximum power transfer obtained in steps 2 and 5(e):

Step2:

Load resistance = 12.5


Step 5(e):

Load resistance = 12.5

So, here is no differences between the step 2 and step 5(e) value.

Answers to the questions no: 03

Theoretical solution:

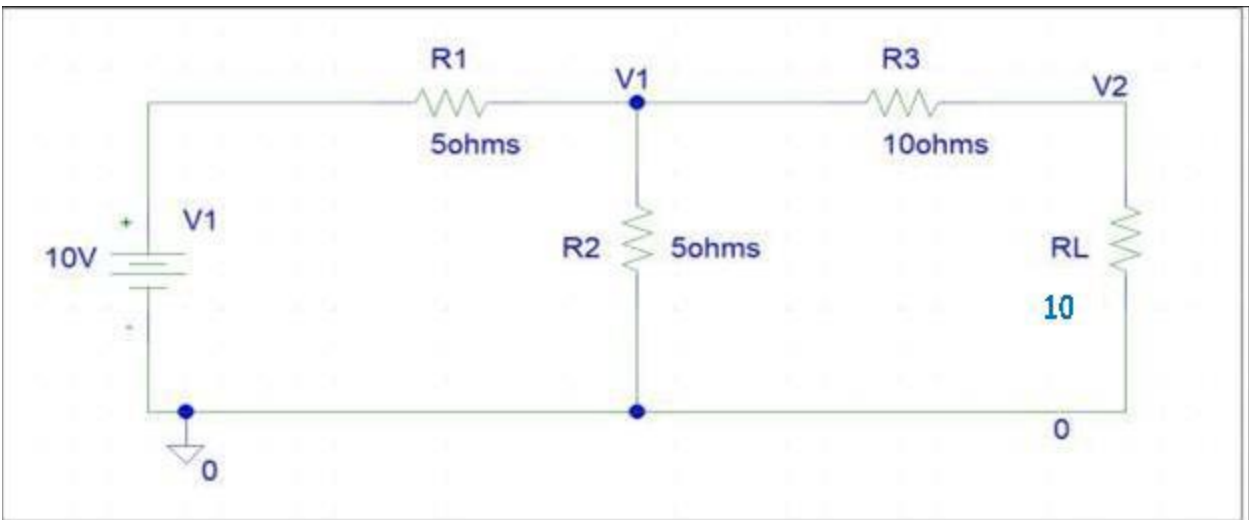

Kcl at node 1,

$$\frac{V1-10}{5} + \frac{V1}{5} + \frac{V1}{20} = 0$$


$$\Rightarrow V1=4.44V$$

Now,

$$I(R3) = V1/20 = 4.44/20 = 0.22A$$

$$\text{So, } V2 = R_L \times I(R3) = 10 \times 0.22 = 2.22V$$

PSpice Simulation:

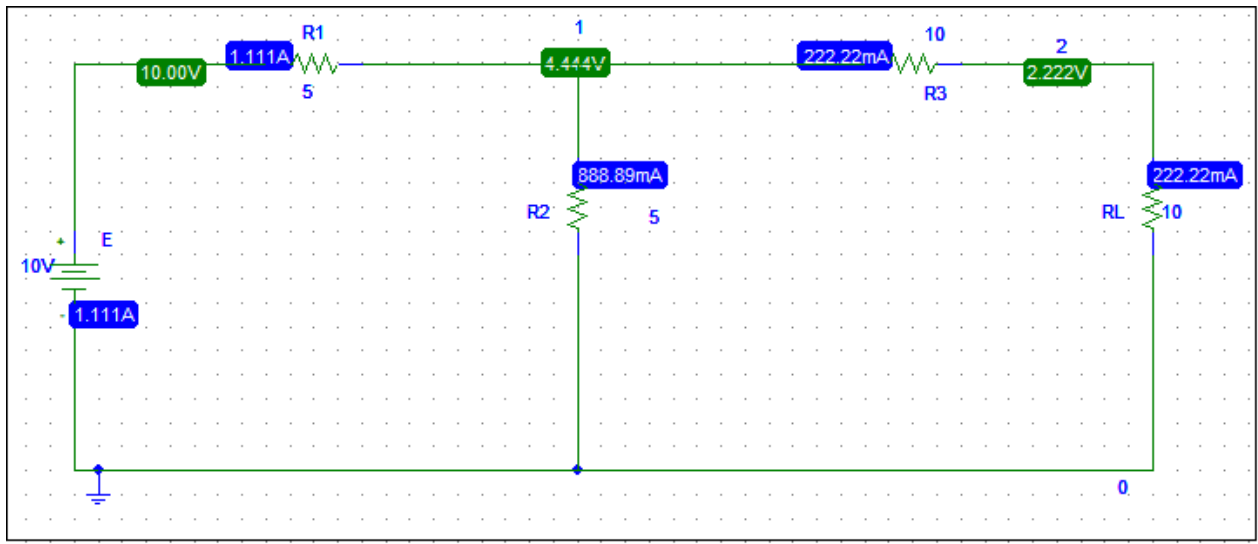

$I(R3) = 222.22\text{mA}$ $V(1) = 4.444\text{V}$ $V(2) = 2.222\text{V}$ and Comparing the theoretical and PSpice solution:

PSpice solutions:

$V(1) = 4.444\text{V}$, $V(2) = 2.222\text{V}$ and $I(R3) = 222.22\text{mA}$

Theoretical solutions:

$V(1) = 4.444\text{V}$, $V(2) = 2.222\text{V}$ and $I(R3) = 222.22\text{mA}$

So, here is no differences between the theoretical solutions and PSpice solutions.

Result & Discussion:

PSpice data:

Measured values are $= 12.5\Omega$, $V(1) = 4.444\text{V}$, $V(2) = 2.222\text{V}$ and $I(R3) = 222.22\text{mA}$. There are some a little differences between the theoretical values and the experimental measured values. Pre-Lab data and experimental data are also almost same. From this experiment, we slightly broaden our knowledge we gained from the previous experiment. By doing this experiment we have been able to simulate our

circuits via PSpice and test the results. After doing this experiment we gain knowledge about maximum power transfer theorem.

Theoretical data:

Theoretically calculated values = 12.5Ω , $V(1) = 4.444V$, $() = 2.222V$ and $I(R3) = 222.22mA$

Conclusion:

While doing the experiments, the readings were taken very carefully. Though there is no slightly difference between calculated value and PSpice value, at the end of the experiment we finally gained practical knowledge about Superposition theorem.

Pre lab:


Name: B M Shahria Alam

ID: 2021-3-60-016

Grp: 01


Exp no: 7

Pre lab report

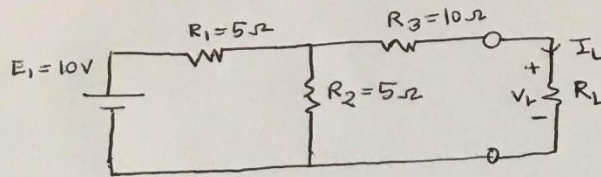

We have to calculate the value of R_L when $R_L = R_{th}$. The R_L will draw the maximum power.

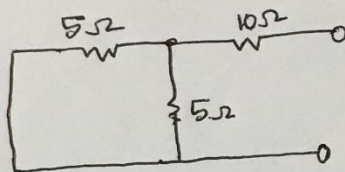
$$P_{max} = I_L \times V_L = \frac{V_{th}^2}{4R_{th}}$$



$$R_{eq} = 10 + [5 \parallel 5] \\ = 12.5 \Omega$$

$$\therefore R_{eq} = R_{th} = 12.5 \Omega \\ = R_L$$


Now we have to calculate V_{th} .

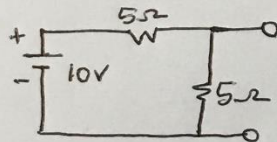

$$V_{th} = V_1$$

Using VDR,

$$V_1 = \frac{5}{10} \times 10 = 5V$$

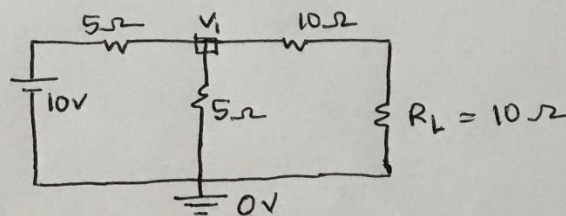

KCL at node 1,

$$\frac{V_1 - 10}{5} + \frac{V_1}{5} + \frac{V_1}{20} = 0$$

$$\therefore V_1 = 4.44V$$

$$\therefore I(R_3) = \frac{V_1}{20} \\ = \frac{4.44}{20} = 0.22A$$

$$\begin{aligned}\therefore V_L &= R_L \times I(R_3) \\ &= 10 \times 0.22 \\ &= 2.22 \text{ V}\end{aligned}$$
