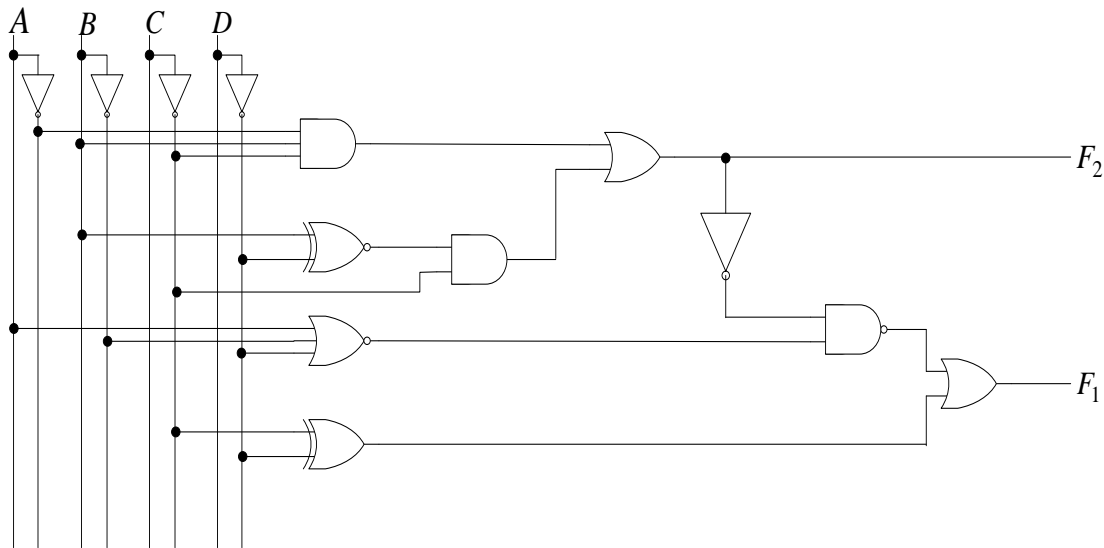


Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Term II Examination, Fall 2021 Semester

Note: There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

2. **Analyze** the following circuit by writing the Boolean expression of the outputs. [CO2,C4, EP1, Mark: 8]



- Page 1 of 2

5. **Construct** a combinational circuit using an 8×1 MUX for implementing the following Boolean function. [Properly label all the inputs and outputs]

[CO3,C6,
EP1,EP2,
Mark: 6]

$$F(A, B, C, D) = \prod (1, 2, 6, 7, 11, 12, 15)$$

6. **Write** a behavioral Verilog code to design the following Boolean function using Procedural technique using case statement.

[CO3,C6,
EP1,EP2,
Mark: 8]

$$F(A, B, C, D) = (B + D')C' + (A' + C)$$