



EAST WEST UNIVERSITY

Course Title: CSE209

Section: 02

Semester: Fall 22

Assignment- 02

SUBMITTED TO

M. Saddam Hossain Khan

Senior Lecturer

Department of Computer Science & Engineering

East West University


SUBMITTED BY

Name: B M Shahria Alam

Student ID: 2021-3-60-016

Date of submission: 03 November 2022.

Assignment - 2

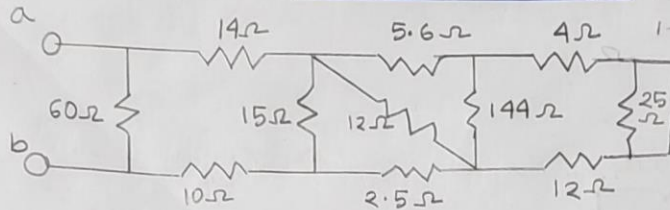


Here, a wire connected over 25Ω . So the 25Ω resistor won't work here. So this is a short circuit.

So, 4Ω and 12Ω are in series;

$$R_{S1} = (4 + 12)\Omega$$

$$= 16\Omega$$

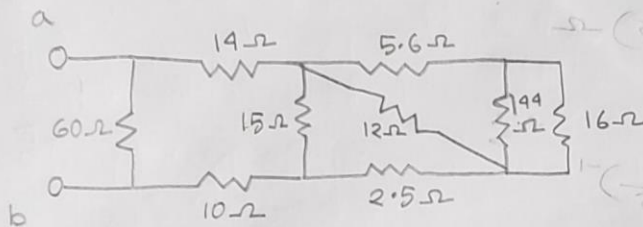


Here,

14Ω and 16Ω are in parallel,

$$\frac{1}{R_{P1}} = \left(\frac{1}{14} + \frac{1}{16} \right)$$

$$\therefore R_{P1} = 14.4\Omega$$

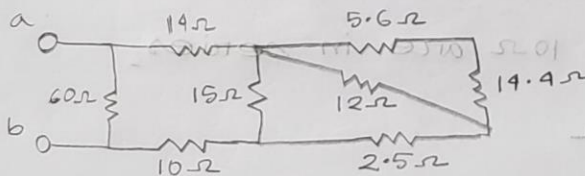

Here,

5.6Ω and 14.4Ω are in series,


$$R_{S2} = (5.6 + 14.4)\Omega$$

$$= 20\Omega$$

and the 20Ω and 12Ω are in parallel]

$$R_{P2} = \left(\frac{1}{20} + \frac{1}{12} \right)^{-1} \Omega$$

$$= 7.5\Omega$$

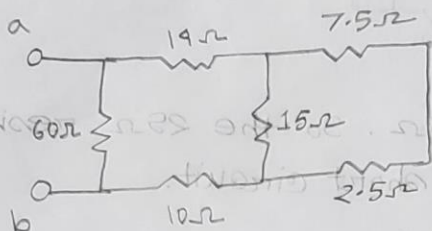

Here 7.5Ω and 2.5Ω are in series, and with 15Ω


they are parallel,

$$R_{S3} = (7.5 + 2.5) \Omega$$

$$= 10\Omega$$

$$\therefore R_{P3} = \left(\frac{1}{10} + \frac{1}{15} \right)^{-1}$$


$$= 6\Omega$$

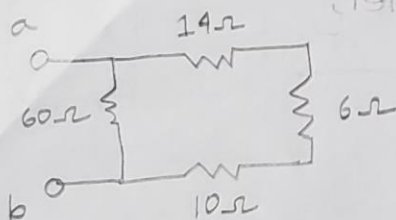

Here, 14Ω , 6Ω and 10Ω are in series,

$$R_{S4} = (14 + 6 + 10) \Omega$$


$$= 30\Omega$$

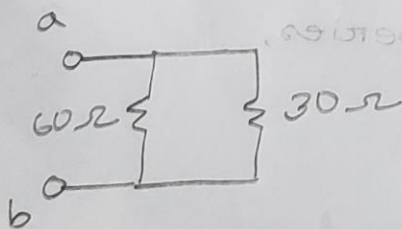

Here,

30Ω and 60Ω are in parallel,
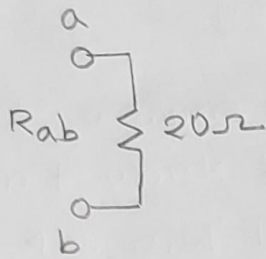
$$R_{PA} = \left(\frac{1}{30} + \frac{1}{60} \right)^{-1}$$
$$= 20\Omega$$



$$\therefore R_{ab} = 20\Omega$$