



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
Summer 2021 Semester
CSE345 Digital Logic Design, Section-3, Class Test-2
Marks:10
Time: 25 minutes

1. Design an OR-AND circuit for the Boolean function (5)

$$F(A, B, C, D) = \sum (1, 3, 4, 5, 9, 12, 13) + \sum_{d.c.} (2, 7, 8, 11, 14)$$

2. Analyze the following circuit by constructing the truth table of the output. (5)

