




EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
In Course Assessment - 2, Spring 2021

Course: CSE 209 – Electrical Circuits, Section-4
Instructor: SHK, Senior Lecturer, CSE Department
Full Marks: 19
Time: 1 Hour and 30 Minutes [Including submission time]

Note: There are FOUR questions, answer ALL of them. Course outcomes (CO), cognitive levels and marks of each question are mentioned at the right margin.


- 1a. Apply nodal analysis to determine i_0 from the circuit given below.

[CO2,
Mark:4]

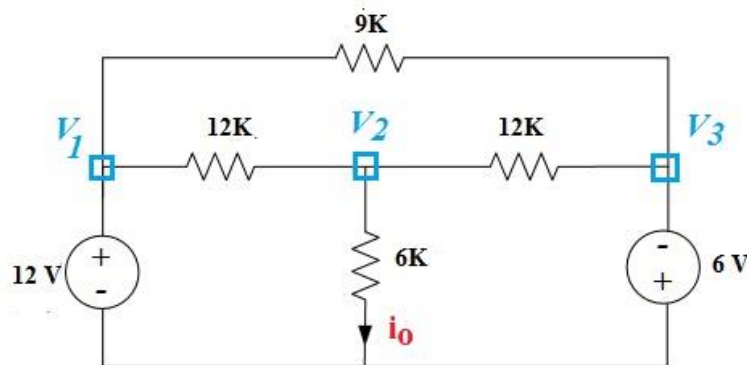


- 1b. Using nodal analysis, determine V_x from the circuit given below.

[CO2,
Mark:2]

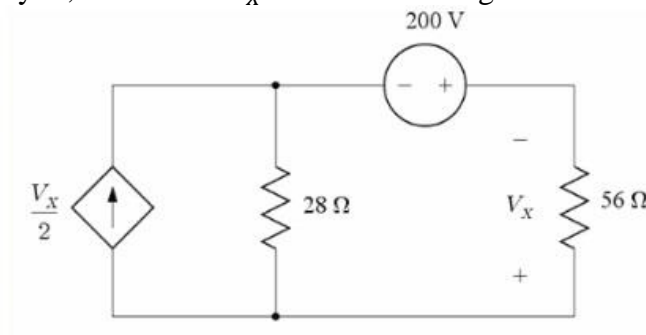


2. Using mesh currents indicated in the circuit, determine v_0 in the following circuit.

[CO2,
Mark:6]

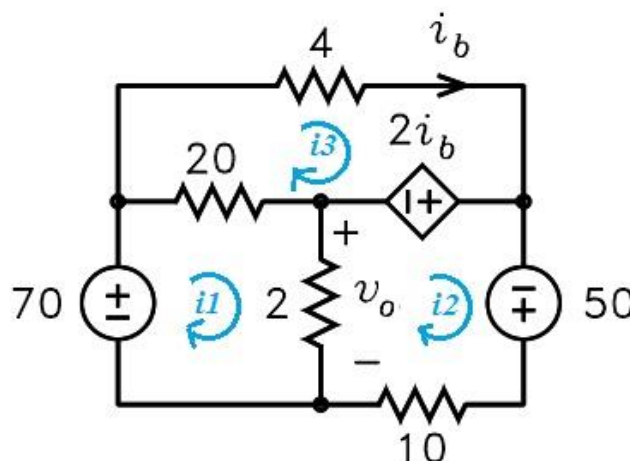

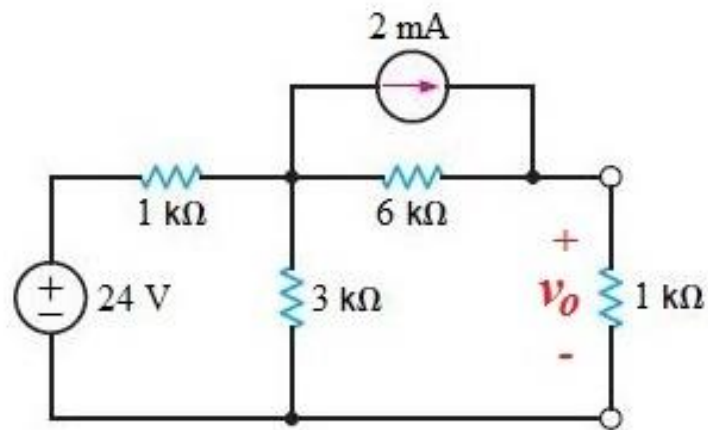3. Use most effective source transformation to determine v_o in the following circuit. [CO2, Mark: 3]



4. Use superposition technique to determine i in the following circuit. [CO2, Mark: 4]

