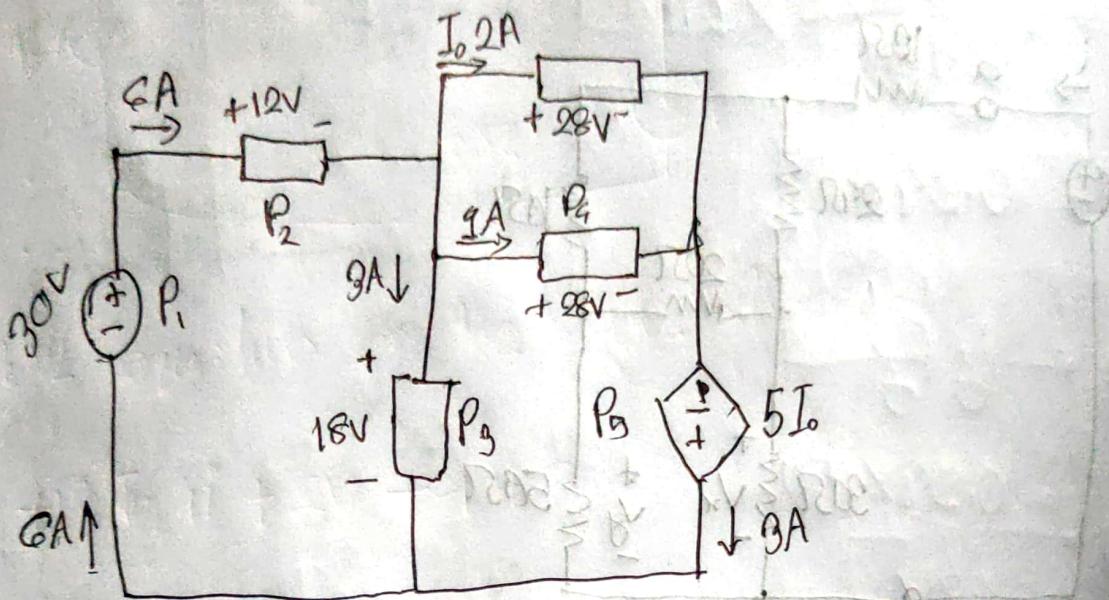


Omar Rabet Adnan
Id: 2020-2-20-037

Answer to the question number 1



$$P_1 = -VI = -(30 \times 6) = -180 \text{ watt (S)}$$

$$P_2 = +VI = (6 \times 12) = 72 \text{ watt (A)}$$

$$P_3 = +VI = (18 \times 3) = 54 \text{ watt (A)}$$

$$P_4 = +VI = (1 \times 28) = 28 \text{ watt (A)}$$


$$P_5 = -VI = -(5I_o \times 10) = -15I_o \text{ (S)}$$

$$= -(15 \times 2)$$


$$= -30 \text{ watt (S)}$$

Answer to the question NO 104

(b)

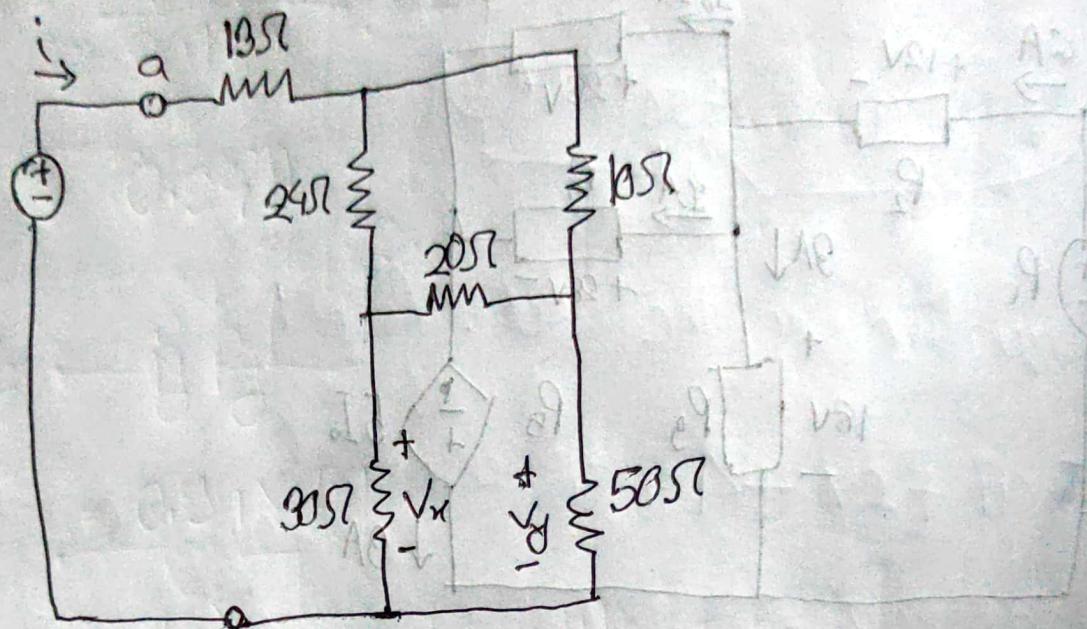

Applying Why-delta transformation.




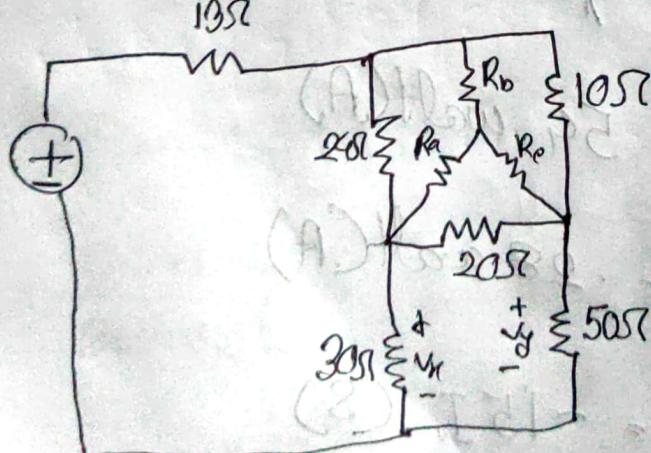


$$R_a = \frac{24 \times 20}{24 + 20 + 10} = 8.89 \Omega$$

②

$$R_b = \frac{24 \times 10}{24+20+10} = 4.44 \Omega$$
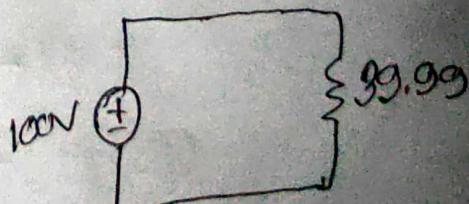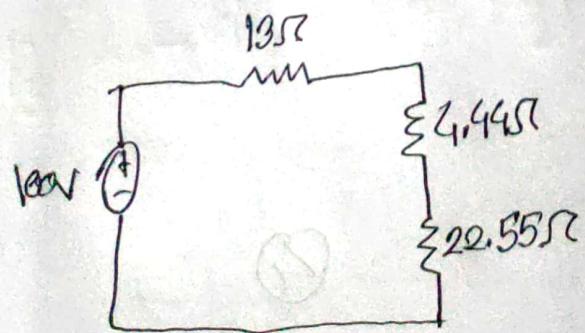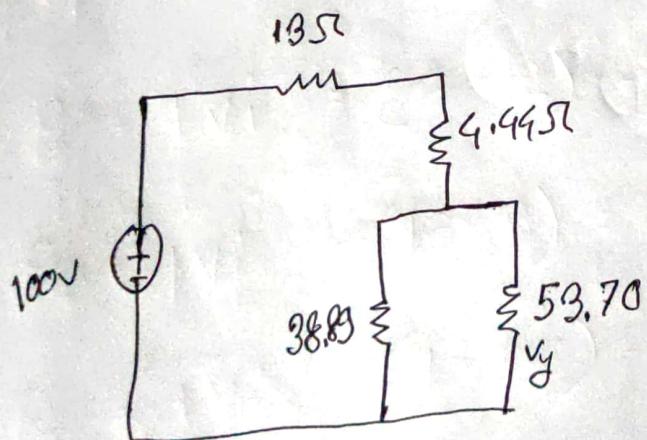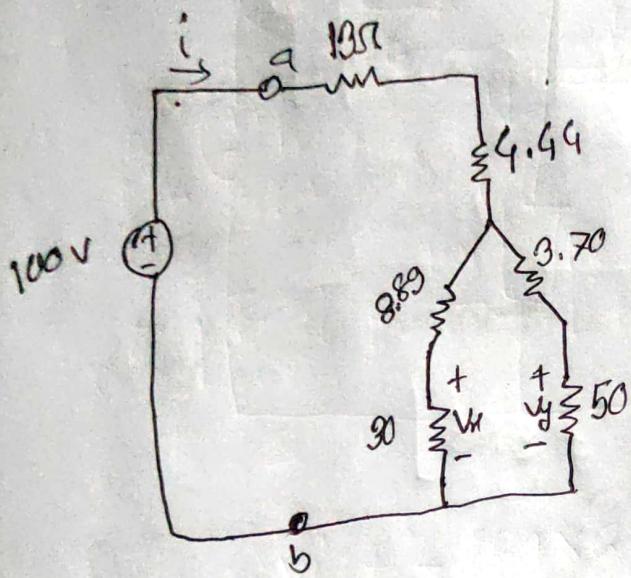
$$R_c = \frac{20 \times 10}{24+20+10} = 3.70 \Omega$$



$$i = \frac{100}{39.99} = 2.50A$$

$$i_y = \frac{30}{30+50} \times 2.50 \\ = 0.94A$$


$$V_y = i_y R_y \\ = 0.94 \times 50 \\ = 47V$$

$$\therefore i = 2.50A, V_y = 47V$$




(2)



Answer to the question No 03

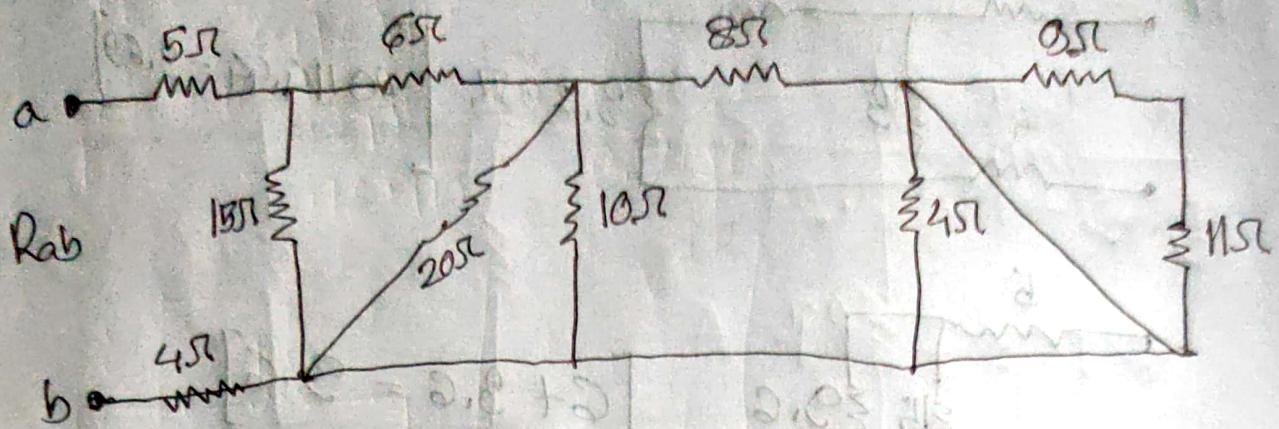

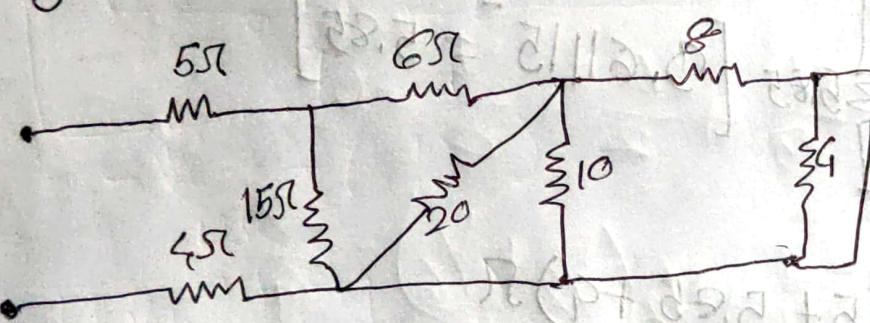Hence 9Ω and 11Ω are connected in series and they are connected with a short circuit.






4Ω is connected with a short circuit

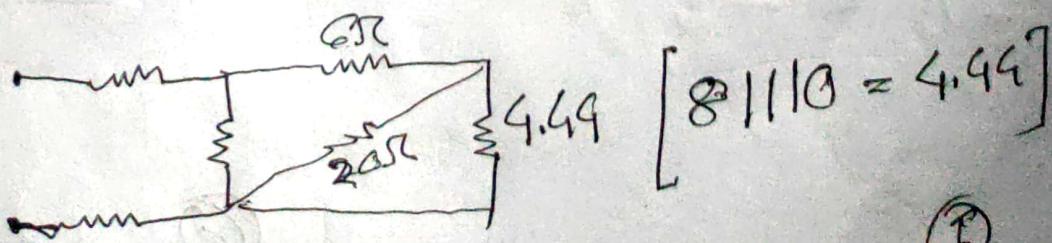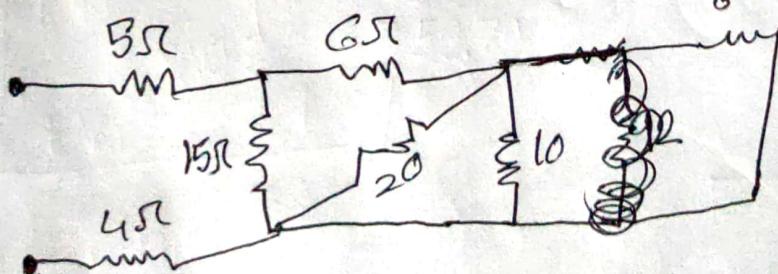

$$[8 // 10 = 4.49]$$

(3)

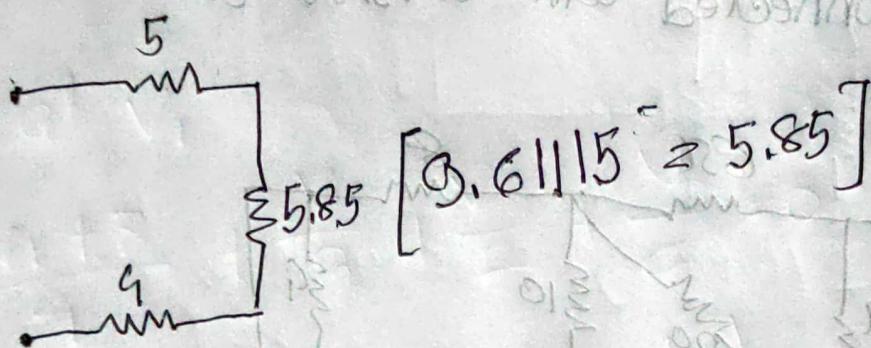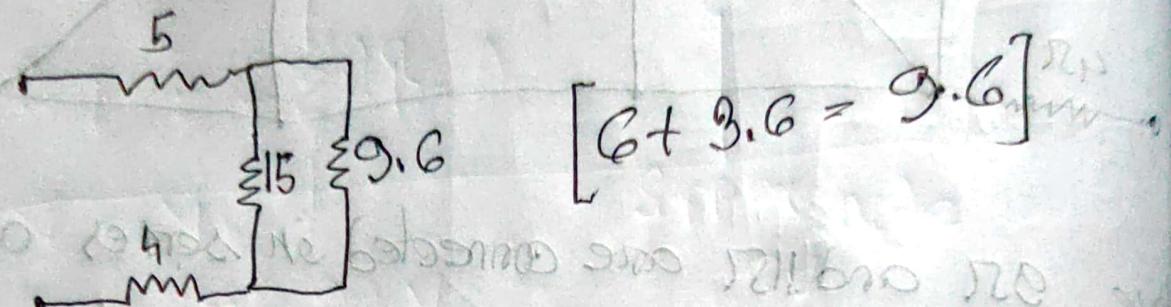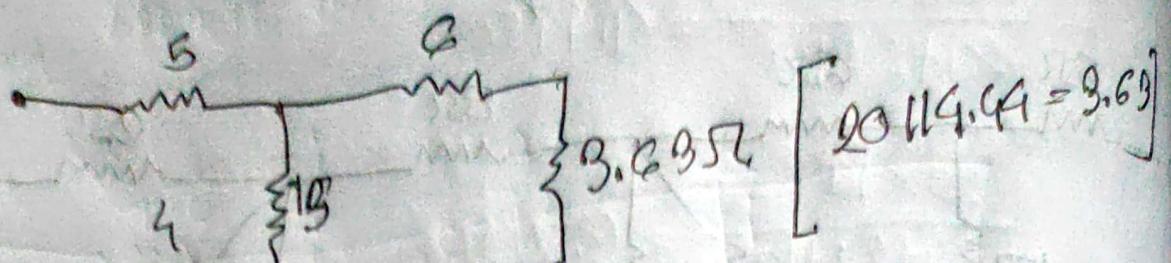


$$\therefore R_{ab} = (5 + 5.85 + 4) \Omega$$

$$= \cancel{14.85} \Omega$$



$$[R.P.P = 0.1118]$$

Answer to the question number (5)

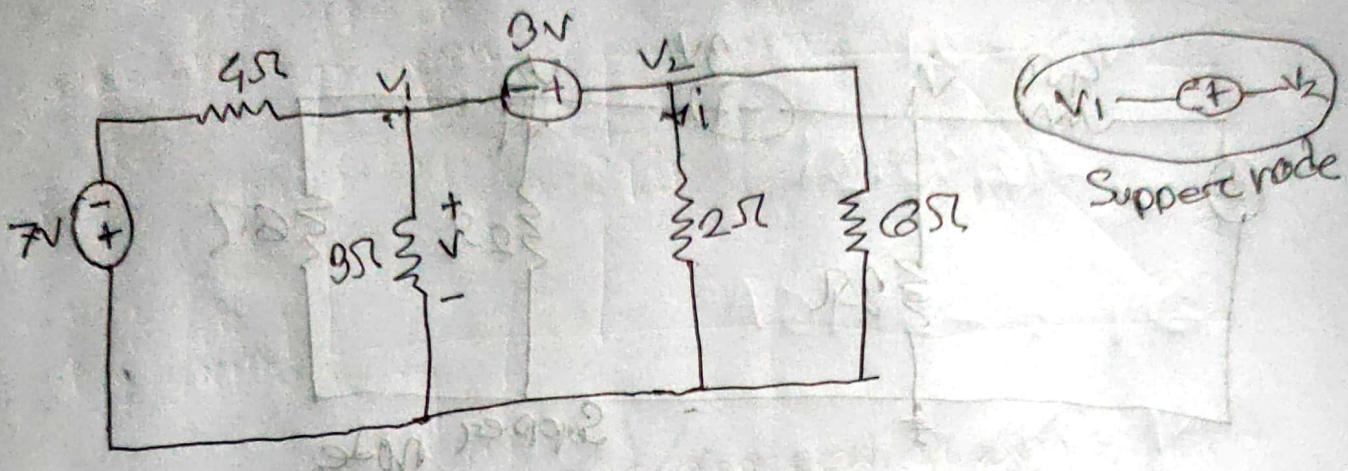

apply node analysis at V_1

$$\frac{V_1 + 7}{4} + \frac{V_1}{3} + \frac{V_2}{2} + \frac{V_2}{C} = 0$$

$$V_1 \left[\frac{1}{4} + \frac{1}{3} \right] + V_2 \left[\frac{1}{2} + \frac{1}{C} \right] = -\frac{7}{4} + \frac{8 + 1V}{C}$$



$$V_1 [0.5833] + 0.666V_2 = -1.75 + \frac{8 + 1V}{C}$$

$$D = \begin{vmatrix} 0.5833 & 0.666 \\ 1 & -1 \end{vmatrix}$$

$$= -0.5833 - 0.666$$

$$D = -1.2499$$

Answer to the question number 5

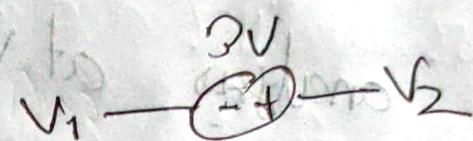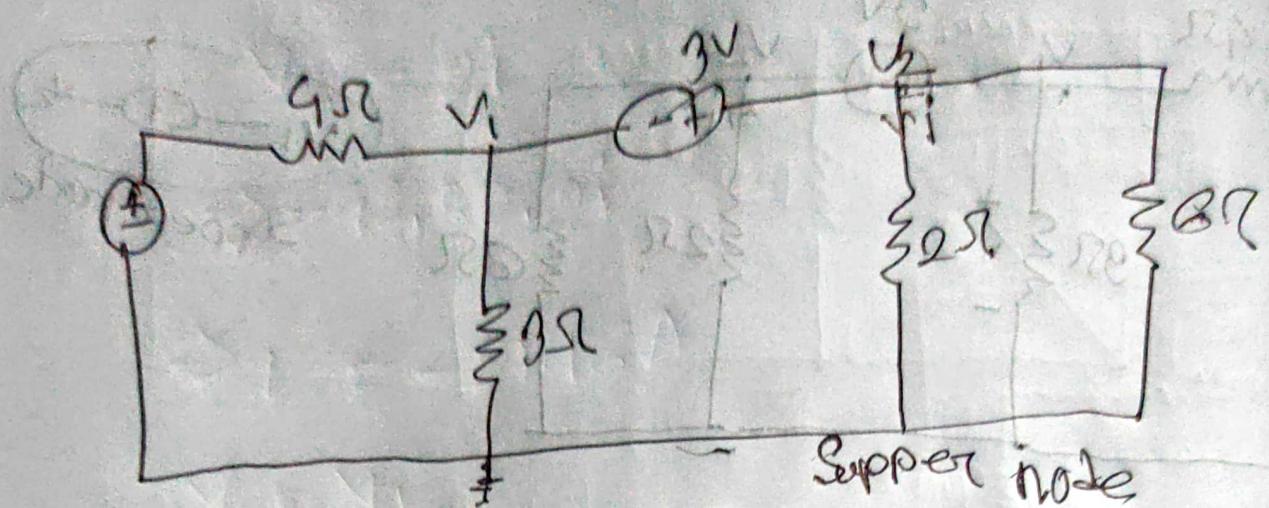

KCL at V_1

$$0 = \frac{V}{3} + \frac{V}{2} + \frac{V}{6} + \frac{V}{12}$$

$$\frac{V_1 + 7}{4} + \frac{V_1}{3} + \frac{V_2}{2} + \frac{V_2}{6} = 0$$

$$\Rightarrow V_1 \left[\frac{1}{4} + \frac{1}{3} \right] + V_2 \left(\frac{1}{2} + \frac{1}{6} \right) = -\frac{7}{4}$$

$$\Rightarrow V_1 (0.5833) + 0.66666 V_2 = -1.75$$

KCL at V_2

$$V_1 - V_2 = -3 \rightarrow \text{Eqn } (1)$$

By Cramer's rule:

$$V_1 = \frac{\begin{vmatrix} -1.75 & 0.666 \\ -3 & -1 \end{vmatrix}}{\begin{vmatrix} 0.5833 & 0.666 \\ 1 & -1 \end{vmatrix}}$$

$$= (1.75 - 1.998) / (-0.5833 + 0.666)$$

$$= -2.99 V$$

$$V_2 = \frac{\begin{vmatrix} 0.5833 & -1.75 \\ 1 & -3 \end{vmatrix}}{\begin{vmatrix} 0.5833 & 0.666 \\ 1 & -1 \end{vmatrix}}$$

$$= \frac{-1.7499 - 1.75}{-0.5833 + 0.666}$$

$$= -42.32 V$$



Hence,

$$V_2 = 2i$$

$$\Rightarrow -42.32 \cdot 2i$$

$$\Rightarrow I = -21.16 A$$

$$V = V_1 \\ = -2.99 V$$

Aus

$$V_{EE.C} =$$

$$25.1 - 228.0 \\ | 0 - h |$$

$$222.0 \quad 228.0 \\ | - |$$

$$25.1 - 228.0 \\ | - |$$


$$222.0 + 228.0 \\ | - |$$

$$V_{EE.CP} =$$

(10)

Answer to the question No. 02

Given

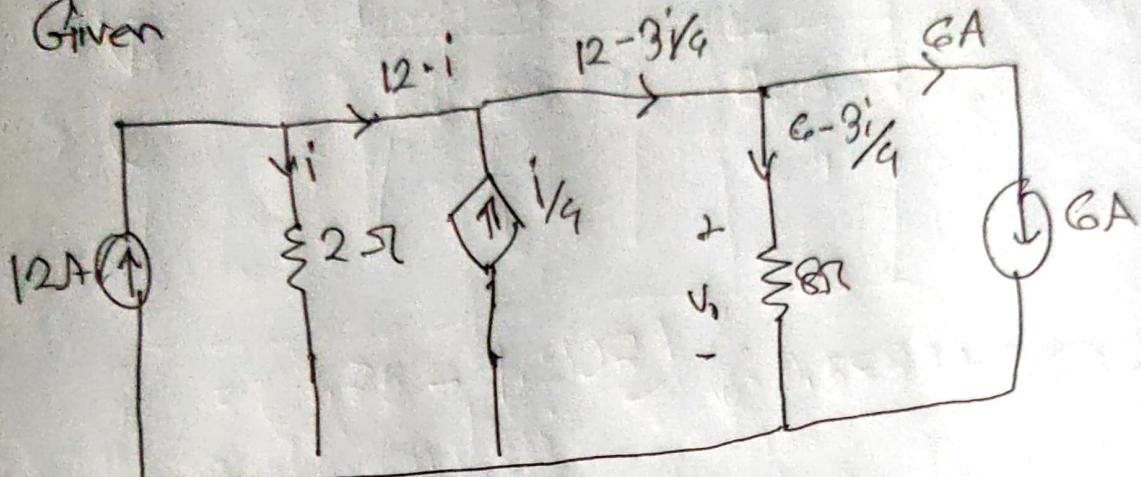

from loop ① we can write

$$2i - \epsilon \left(G - \frac{3i}{a} \right) = 0$$

$$2i - 4\epsilon + 6i = 0$$

$$i = 6 \text{ Amp}$$

$$V_o = \left(G - \frac{3i}{a} \right) \times 8$$

$$= \left(G - \frac{3 \times 6}{4} \right) \times 8$$

$$= 12 \text{ Volt}$$

Ans

(w)