


**Department of Computer Science and Engineering**  
**B.Sc. in Computer Science and Engineering Program**  
**Mid Term II Examination, Fall 2021 Semester**


**Course:** CSE 345 Digital Logic Design, Section-3  
**Instructor:** Musharrat Khan, Senior Lecturer, CSE Department  
**Full Marks:** 40 (20 will be counted for final grading)  
**Time:** 1 Hour and 25 Minutes (Including Submission)

**Note:** There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Consider that  $ABCD$  is a 4-bit input and  $F$  is a 1-bit output of a combinational circuit. [CO3,C3,  
The output is  $F = 1$  for both case 1 and case 2: EP1,EP2,  
Case 1: When only A and C are 1 Mark: 6]  
Case 2: When only B and D are 1  
**Design** the combinational circuit.

 2. **Analyze** the following circuit by constructing truth table of the outputs. [CO2,C4, EP1, Mark: 8]
- $A$       $B$       $C$       $D$





3. **Design** a full-adder using only AND, and OR gates. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C3, Mark: 6]
4. **Design** a  $10 \times 4$  Encoder for active-LOW inputs. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C6, Mark: 6]

5. Given that only  $8 \times 1$  MUXs are available. Design a  $24 \times 1$  MUX using necessary number of  $8 \times 1$  MUXs. [Properly label all inputs and outputs] [CO3,C6, EP1,EP2, Mark: 6]
  
6. **Write** a Procedural Verilog description using case statement for implementing a  $4 \times 1$  MUX with active-LOW Enable input. [CO3,C6, EP1,EP2, Mark: 8]