

Chapter 14

Design of Combinational Circuits using Verilog HDL

- Verilog Codes

- Structural Verilog Code

- Behavioral Verilog Code

- ❖ Procedural Model

- ❖ Continuous assign statement

Structural Verilog Code of S output of FA

 


Fig: S output of FA circuit

Structural Verilog Code:

```
module sumofFAstructural (input A,B,Cin,output S);
    wire w1,w2,w3,w4;
    and g1(w1,~A,~B,Cin),
        g2(w2,~A,B,~Cin),
        g3(w3,A,~B,~Cin),
        g4(w4,A,B,Cin);
    or g5(S,w1,w2,w3,w4);
endmodule
```

Behavioral Verilog Code of S output of FA

Procedural Model:

```
module sumofFABehavioral(input A, B, Cin, output reg S);  
always@(A, B, Cin) begin  
S=0;  
if (~A & ~B & Cin) S=1;  
if (~A & B & ~Cin) S=1;  
if (A & ~B & ~Cin) S=1;  
if (A & B & Cin) S=1;  
end  
endmodule
```

A	B	Cin	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

```

module sumofFABehavioral(input A, B, Cin, output reg S);
always@(A, B, Cin) begin
S=1;
if (~A&~B&~Cin) S=0;
if (~A&B&Cin) S=0;
if (A&~B&Cin) S=0;
if (A&B&~Cin) S=0;
end
endmodule

```

A	B	Cin	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


Continuous assign statement:

```
module sumofFAAssign(input A, B, Cin, output S);  
assign S=(~A & ~B & Cin)|(~A & B & ~Cin)|(A & ~B & ~Cin)|(A & B & Cin);  
endmodule
```

Continuous assign statement:

```
module sumofFAAssign(input A, B, Cin, output S);  
assign S=(A|B|Cin)&(A|~B|~Cin)&(~A|B|~Cin)&(~A|~B|Cin);  
endmodule
```

 Procedural description of a 2x1 MUX
using if statement



A	F
0	I ₀
1	I ₁

$$F = I_0 A' + I_1 A$$

A	I ₀	I ₁	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Procedural Model:

```
module twoByOneMux(input A, I0, I1, output reg F);  
  always@(A, I0, I1)  
    if (A==0)  
      F=I0;  
    else F=I1;  
endmodule
```

Continuous assign statement:

```
module twoByOneMuxAssign(input A, I0, I1, output F);  
assign F=(~A&I0)|(A&I1);  
endmodule
```

Procedural Description of sum of FA using case statement

```
module sumofFACase(input A, B, Cin, output reg S);  
always@(A, B, Cin)  
    case({A, B, Cin})  
        3'b000: S=0;  
        3'b001: S=1;  
        3'b010: S=1;  
        3'b011: S=0;  
        3'b100: S=1;  
        3'b101: S=0;  
        3'b110: S=0;  
        3'b111: S=1;  
    endcase  
endmodule
```

Procedural Description of sum of FA using case statement with Default

```
module sumofFACaseWithDefault(input A, B, Cin, output reg S);  
always@(A, B, Cin)  
    case({A, B, Cin})  
        3'b000: S=0;  
        3'b011: S=0;  
        3'b101: S=0;  
        3'b110: S=0;  
        default: S=1;  
    endcase  
endmodule
```