



**EAST WEST UNIVERSITY**  
**Department of Computer Science and Engineering**  
**Fall 2021 Semester**  
**CSE345 Digital Logic Design, Section-3, Class Test-2**  
**Marks:10**  
**Time: 25 minutes**

1. Design an OR-AND circuit for the Boolean function (5)

$$F(A, B, C, D) = \sum (1, 3, 4, 5, 9, 13) + \sum_{d.c.} (2, 7, 8, 11, 14)$$

2. Analyze the following circuit by writing the Boolean expression of the output. (5)

