



# EAST WEST UNIVERSITY

Department of Computer Science and Engineering

B.Sc. in Computer Science and Engineering Program


Mid Term II Examination, Fall 2020 Semester

**Course:** CSE 345 Digital Logic Design, Section-3  
**Instructor:** Musharrat Khan, Senior Lecturer, CSE Department  
**Full Marks:** 40 (20 will be counted for final grading)  
**Time:** 1 Hour and 30 Minutes (Including Submission)

**Note:** There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Consider that  $ABCD$  is a 4-bit input and  $X$  is a 1-bit output of a combinational circuit. The output is  $X = 1$  if the input contains odd number of 1s; otherwise  $X = 0$ . **Design** the combinational circuit. [CO3,C3, Mark: 6]

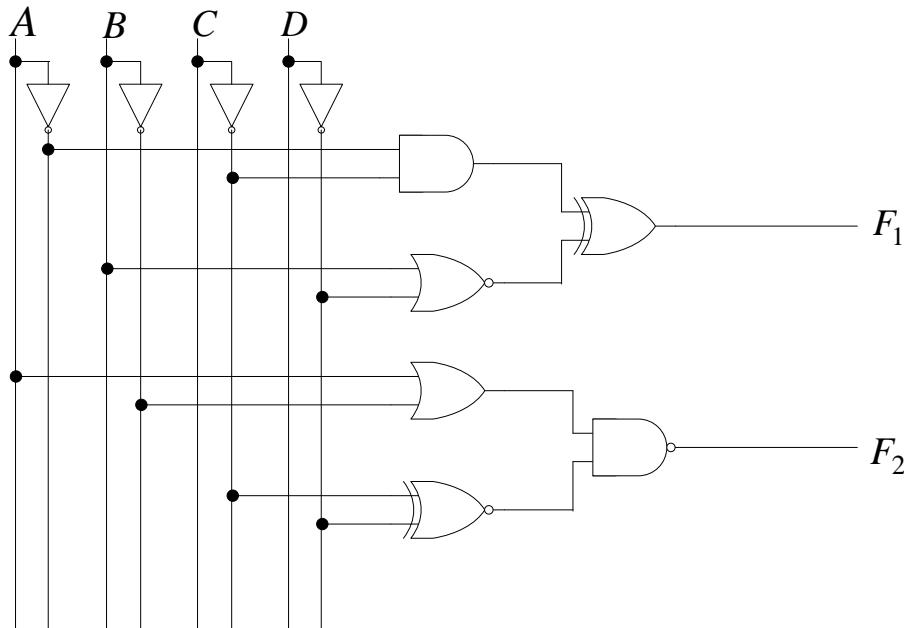2. **Analyze** the following circuit by constructing truth table of the outputs. [CO2,C4, Mark: 8]



3. **Design** a full-adder using only AND, and OR gates. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C3, Mark: 6]
4. **Design** a Binary-to-Hexadecimal Decoder for active-HIGH output. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C6, Mark: 6]

5. Given that  $8 \times 1$  MUXs are available. Design a  $32 \times 1$  MUX using necessary number of  $8 \times 1$  MUXs. [Properly label all inputs and outputs] [CO3,C6, Mark: 6]
  
6. **Write** a Procedural Verilog description using case statement for implementing a  $2 \times 4$  Decoder with active-HIGH Enable input and active-LOW outputs. [CO3,C6, Mark: 8]