
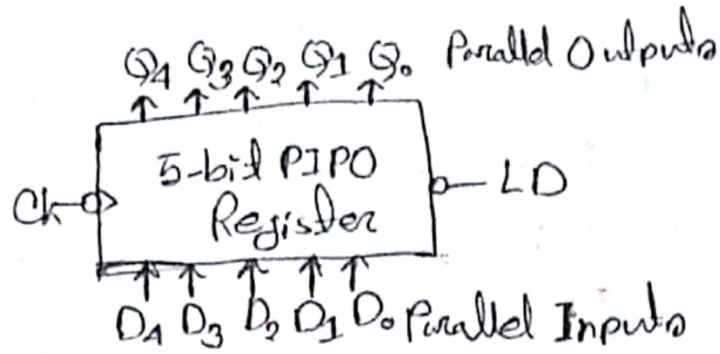


Parallel-in, Parallel-out (PIPO):

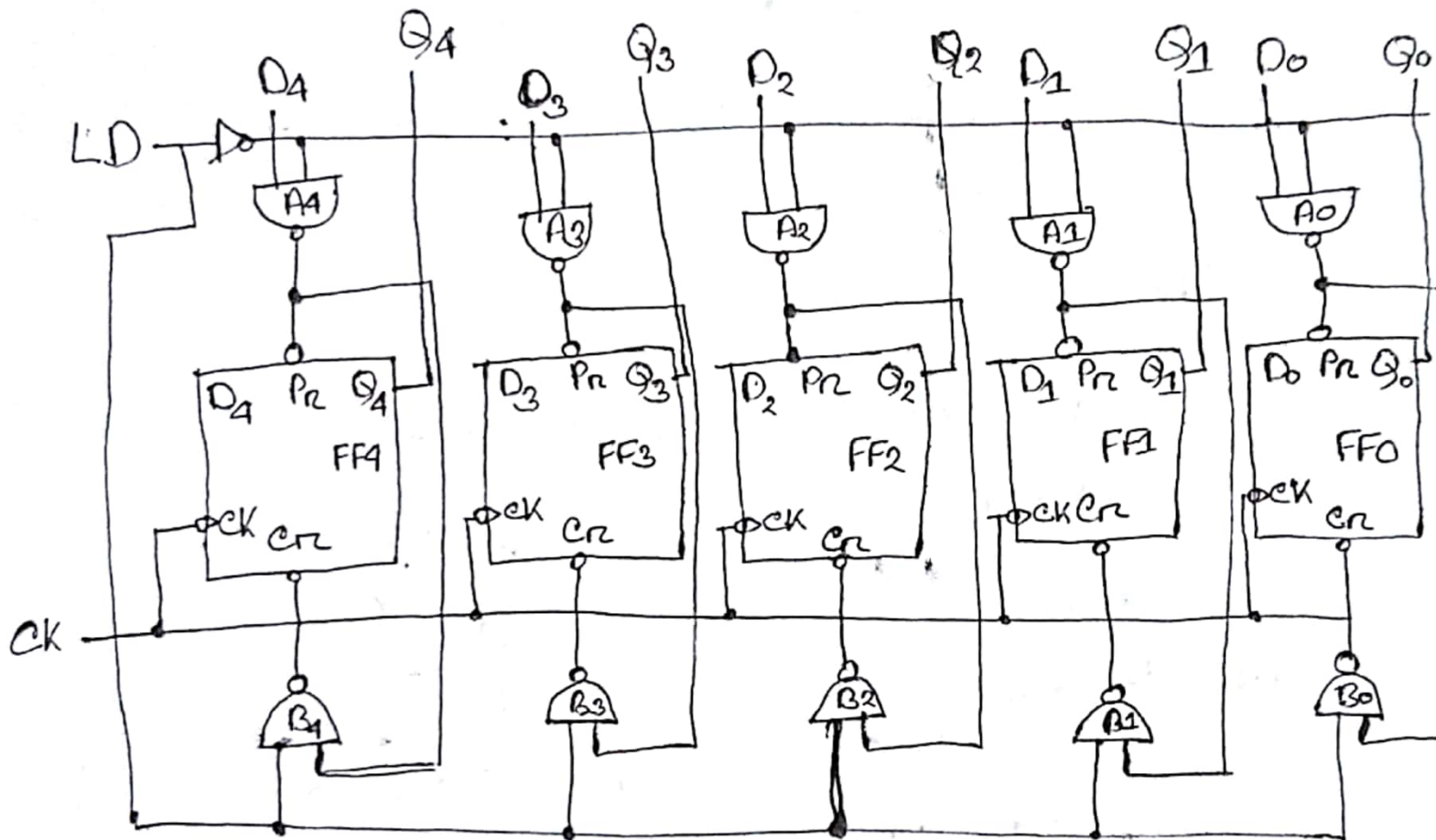


(a) Block diagram



(b) Logic Diagram

Parallel-In Parallel-out Register

$LD=0, Ck=0$

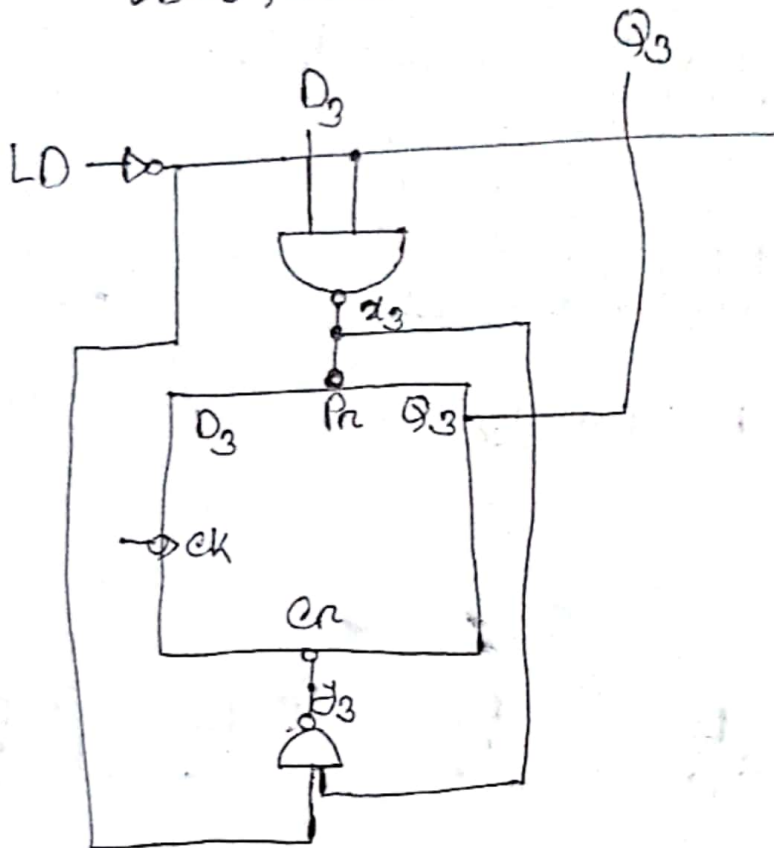

$LD=0$

$$x_3 = (D_3 \cdot LD)'$$

$$= (D_3 \cdot 1)'$$

$$x_3 = D_3'$$

$$P_n = x_3 = D_3'$$

$$y_3 = (x_3 \cdot LD)'$$

$$= (x_3 \cdot 1)'$$

$$= (D_3')'$$


$$y_3 = D_3$$

$$C_n = y_3 = D_3$$


| D_3 | P_n | C_n | Q_3 |
|-------|-------|-------|-------|
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |

Answer to the Question No. 4

a. $\div 16$ Synchronous up Counter:

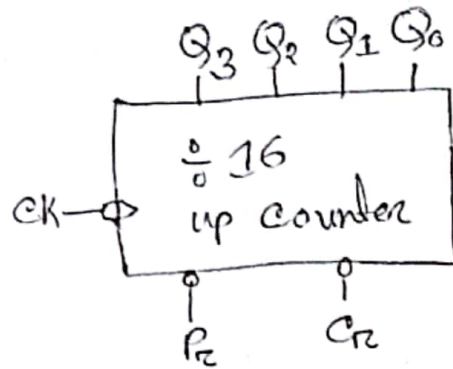

(a) Block diagram

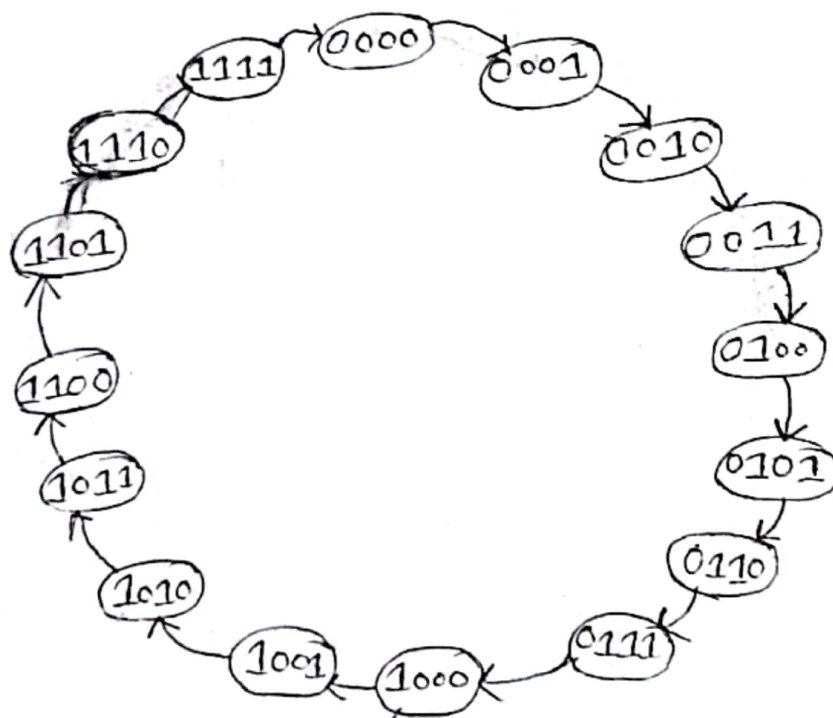

(b) Transition Diagram

Excitation Table:

| Present state | | | | Next state | | | | Flip-Flop Inputs | | | |
|---------------|----------|----------|----------|------------|------------|------------|------------|------------------|-------|-------|-------|
| Q_{2n} | Q_{2n} | Q_{1n} | Q_{0n} | Q_{2n+1} | Q_{2n+1} | Q_{1n+1} | Q_{0n+1} | T_3 | T_2 | T_1 | T_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

| $Q_3 Q_2$ \ $Q_1 Q_0$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | 1 | |
| 11 | | | 1 | |
| 10 | | | | |

$$T_3 = Q_2 Q_1 Q_0$$

| $Q_3 Q_2$ \ $Q_1 Q_0$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00 | | | 1 | |
| 01 | | 1 | 1 | |
| 11 | | | 1 | |
| 10 | | | 1 | |

$$T_2 = Q_1 Q_0$$


| $Q_3 Q_2$ \ $Q_1 Q_0$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00 | | 1 | 1 | |
| 01 | | 1 | 1 | |
| 11 | | 1 | 1 | |
| 10 | | 1 | 1 | |

$$T_2 = Q_0$$


| $Q_3 Q_2$ \ $Q_1 Q_0$ | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |

$$T_0 = 1$$

Date :

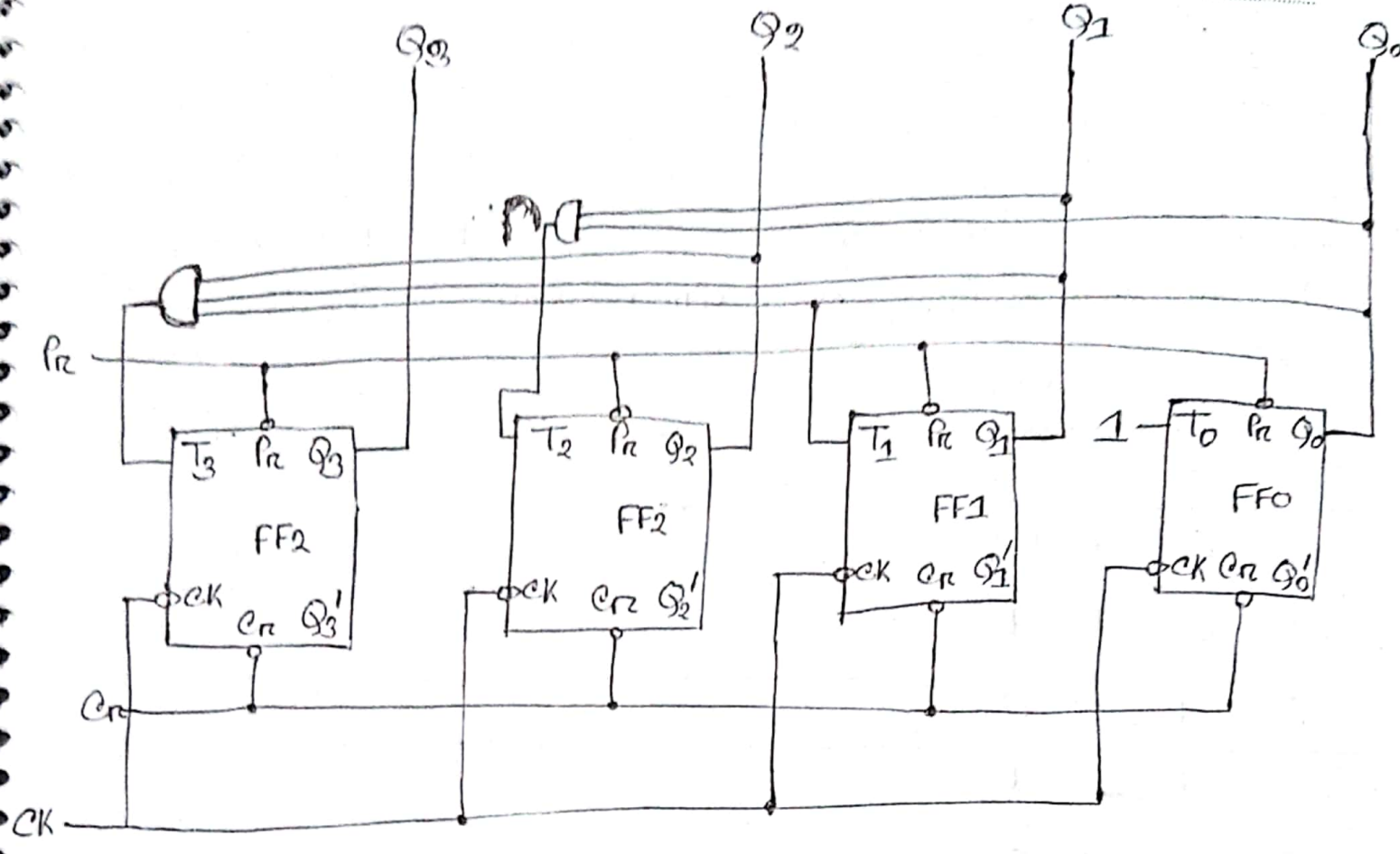

Answer to the Question No: 5

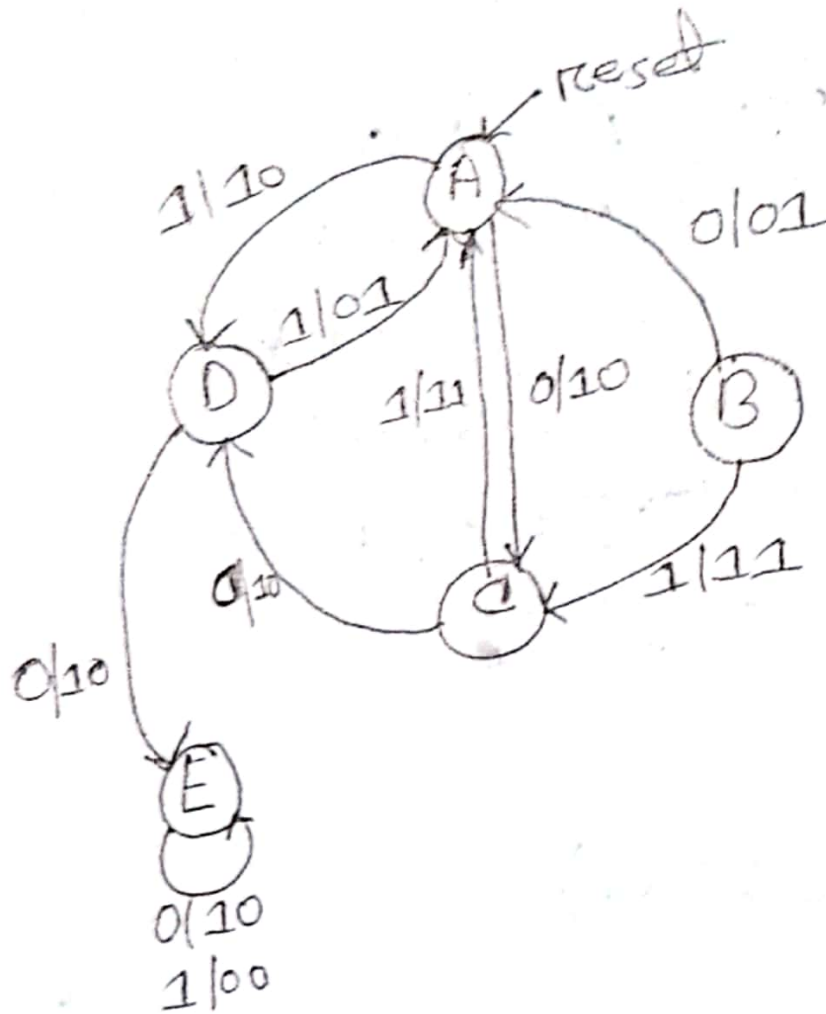

```

module syn_s_circuit(input i, clock, reset,
                    output reg[1:0] out);

```

```

    reg [2:0] currentState, next
              nextState;

```

~~localparam [2:0]~~

localparam [2:0] A = 3'b000,
B = 3'b001,
C = 3'b010,
D = 3'b011,
E = 3'b100;

always @ (*)

case (currentState)

A: begin

nextState = (i == 0) ? C : D;

~~out~~ out = (i == 0) ? 2'b10 : 2'b10;

end

B: begin

nextState = (i == 0) ? A : C

out = (i == 0) ? 2'b01 : 2'b11;

end

C: begin

nextstate = (i == 0) ? D : A;

out = (i == 0) ? 2'b10 : 2'b11;

end

D: begin

nextstate = (i == 0) ? E : A;

out = (i == 0) ? 2'b10 : 2'b01;

end

E: begin

nextstate = (i == 0) ? E : E;

out = (i == 0) ? 2'b10 : 2'b00;

end

default: begin

nextstate = A;

out = 3'bxxx;

end

endcase

always @ (posedge clock, negedge reset)

if (~reset)

currentState <= A;

else

currentState <= nextState;

endmodule

Answer to the Question No: 1

Output Equation:

$$\begin{aligned} Z &= (x + Q_{1n}) x Q_{2n} \\ &= x \cdot x Q_{2n} + x Q_{1n} Q_{2n} \\ &= \underset{1}{x} \underset{1}{Q_{2n}} + \underset{1}{x} \underset{1}{Q_{1n}} \underset{1}{Q_{2n}} \end{aligned}$$

Excitation Equations:

$$\begin{aligned} J_{1n} &= (x' \oplus Q_{2n}') \\ &= x' Q_{2n}' + x' Q_{2n}' \end{aligned}$$

$$K_{1n} = x$$

$$\begin{aligned} J_{2n} &= (x Q_{1n})' \\ &= x' + Q_{1n}' \end{aligned}$$

$$K_{2n} = Q_{1n}'$$


Next state equations:

$$\begin{aligned}
 Q_{1n+1} &= J_{1n} Q_{1n}' + K_{1n}' Q_{1n} \\
 &= (x Q_{2n}' + x' Q_{2n}') Q_{1n}' + x' Q_{1n} \\
 &= \underset{1}{x} \underset{0}{Q_{1n}'} \underset{0}{Q_{2n}'} + \underset{0}{x'} \underset{0}{Q_{1n}'} \underset{0}{Q_{2n}'} + \underset{0}{x'} \underset{1}{Q_{1n}}
 \end{aligned}$$


$$\begin{aligned}
 Q_{2n+1} &= J_{2n} Q_{2n}' + K_{2n}' Q_{2n} \\
 &= (x' + Q_{1n}') Q_{2n}' + Q_{1n}' Q_{2n} \\
 &= \underset{0}{x'} \underset{0}{Q_{2n}'} + \underset{0}{Q_{1n}'} \underset{0}{Q_{2n}'} + \underset{1}{Q_{1n}} \underset{1}{Q_{2n}}
 \end{aligned}$$

| Present state $Q_{1n} Q_{2n}$ | Next State $Q_{1n+1} \times Q_{2n+1}$ Input x | | Output z Input x | |
|----------------------------------|--|-----|-------------------------|---|
| | 0 | 1 | 0 | 1 |
| 0 0 | 1 1 | 1 1 | 0 | 0 |
| 0 1 | 0 0 | 0 0 | 0 | 1 |
| 1 1 | 1 1 | 0 1 | 0 | 1 |
| 1 0 | 1 1 | 0 0 | 0 | 0 |

Transition diagram

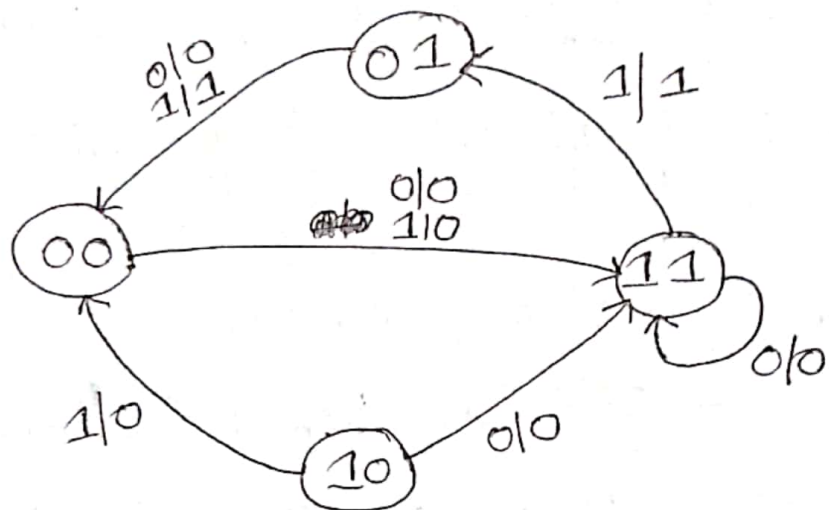

Answer to the Question No: 2

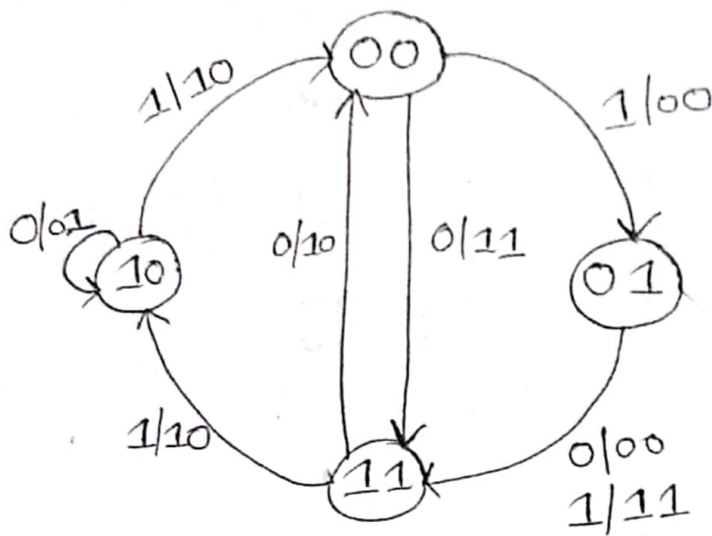

Excitation Table:

| Q_n | Q_{n+1} | S_n | R_n |
|-------|-----------|-------|-------|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | 0 |

| Present State $Q_{1n} Q_{2n}$ | Next State $Q_{1n+1} Q_{2n+1}$ | | Flip-Flop Inputs | | | | Output Z_1, Z_2 Input X | |
|----------------------------------|-----------------------------------|-------|-----------------------|---------------------------|-----------------|-----------------|--------------------------------|----|
| | | | | | | | | |
| | $X=0$ | $X=1$ | $X=0$ | | $X=1$ | | 0 | 1 |
| | | | $S_{1n} R_{1n}$ | $S_{2n} R_{2n}$ | $S_{1n} R_{1n}$ | $S_{2n} R_{2n}$ | | |
| 0 0 | 11 | 01 | 10 | 00 10 | 0X | 10 | 11 | 00 |
| 0 1 | 11 | 11 | 10 | X0 00 | 10 | X0 | 00 | 11 |
| 1 1 | 00 | 10 | 01 | 01 | X0 | 01 | 10 | 10 |
| 1 0 | 0 10 | 00 | 0 1X X0 | 0X 10 X0 | 01 | 0X | 01 | 10 |

S_{1n}

| $Q_{1n} Q_{2n} \backslash X$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 1 | 0 |
| 01 | 1 | 1 |
| 11 | 0 | X |
| 10 | 0 | 0 |

| $Q_{1n} Q_{2n} \backslash X$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 1 | 0 |
| 01 | 1 | 1 |
| 11 | 0 | X |
| 10 | X | 0 |

$$S_{1n} = Q_{1n}' Q_{2n} + Q_{2n}' X'$$

R_{1n}

| $Q_{1n} Q_{2n} \backslash X$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 0 | X |
| 01 | 0 | 0 |
| 11 | 1 | 0 |
| 10 | 0 | 1 |

$$R_{1n} = Q_{1n} Q_{2n} X' + Q_{2n}' X$$

S_{2n}

| $Q_{1n} Q_{2n} \backslash x$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 1 | 1 |
| 01 | X | X |
| 11 | 0 | 0 |
| 10 | 1 | 0 |

$S_{2n} = Q_{1n}'$

R_{2n}

| $Q_{1n} Q_{2n} \backslash x$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 0 | 0 |
| 01 | 0 | 0 |
| 11 | 1 | 1 |
| 10 | X | X |

$R_{2n} = Q_{1n}$

Z₁

| $Q_{1n} Q_{2n} \backslash x$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 1 | 0 |
| 01 | 0 | 1 |
| 11 | 1 | 1 |
| 10 | 0 | 1 |

$$Z_1 = Q_{1n} Q_{2n} + Q_{1n} x + Q_{2n} x + Q_{1n}' Q_{2n}' x'$$

Z₂

| $Q_{1n} Q_{2n} \backslash x$ | 0 | 1 |
|------------------------------|---|---|
| 00 | 1 | 0 |
| 01 | 0 | 1 |
| 11 | 0 | 0 |
| 10 | 1 | 0 |

$$Z_2 = Q_{2n}' x' + Q_{2n}' Q_{1n}$$

