



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
Fall 2021 Semester
CSE345 Digital Logic Design, Section-3, Class Test-3
Marks:10
Time: 25 minutes

1. Analyze the following sequential circuit and draw the transition diagram.

