



# East West University

## LAB REPORT

<b>Course Code and Name:</b> CSE 209 ; ELECTRICAL CIRCUIT	
<b>Experiment no: 05</b> <b>Group no: Individual</b>	
<b>Experiment name:</b> Bias Point Detail Analysis of DC Circuit With Dependent Sources Using PSpice Schematics	
<b>Name of student &amp; Id:</b>	
B M Sharhia Alam	<b>ID:</b> 2021-3-60-016
<b>Course Instructor information:</b> M Saddam Hossain Khan(SHK) Senior Lecturer Department of Computer Science and Engineering East West University	
<b>Date of Report Submitted:</b> 11 December ,2022	

## **OBJECTIVE:**

1. To analyze Bias Point Detail of DC circuit with dependent source using PSpice Schematics.

## **THEORY AND EXPERIMENTAL METHODS:**

In electric circuit there are two types of sources:

1. Independent source
2. Dependent source.

Dependent source contains two elements such as the controlling element and the controlled element which either can be current or voltage.


There are also four types of dependent source. They are:

1. Voltage-controlled voltage source (VCVS)
2. Voltage-controlled current source (VCCS)
3. Current-controlled voltage source (CCVS)
4. Current-controlled current source (CCCS)

But in PSpice they are described with different symbols or alphabets. Which are:

1. Voltage-controlled voltage source (VCVS) as E1.
2. Voltage-controlled current source (VCCS) as G1.
3. Current-controlled voltage source (CCVS) as H1.
4. Current-controlled current source (CCCS) as F1.

## CIRCUIT DIAGRAM:

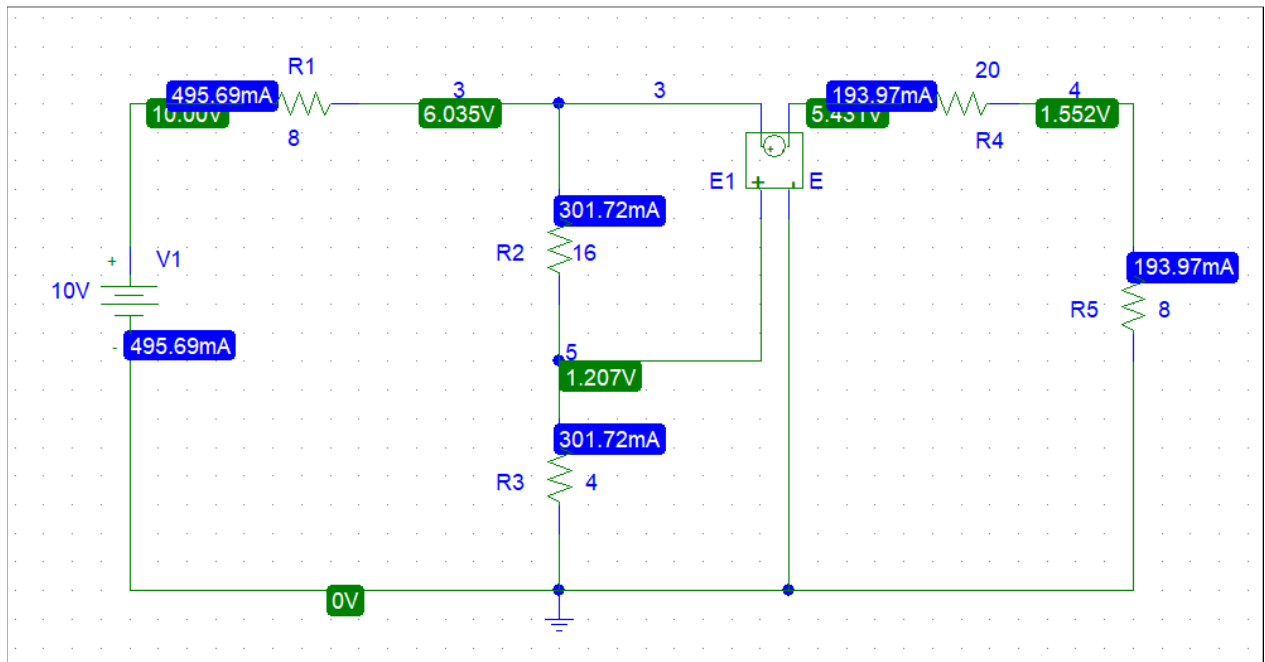

**Figure 2**

**\* Schematics Netlist \***

**V\_V1 1 0 10V**

**R\_R1 1 3 8**


**R\_R2 5 3 16**

**R\_R3 0 5 4**

**R\_R4 4 \$N\_0001 20**

**R\_R5 0 4 8**

**E\_E1 3 \$N\_0001 5 0 0.5**

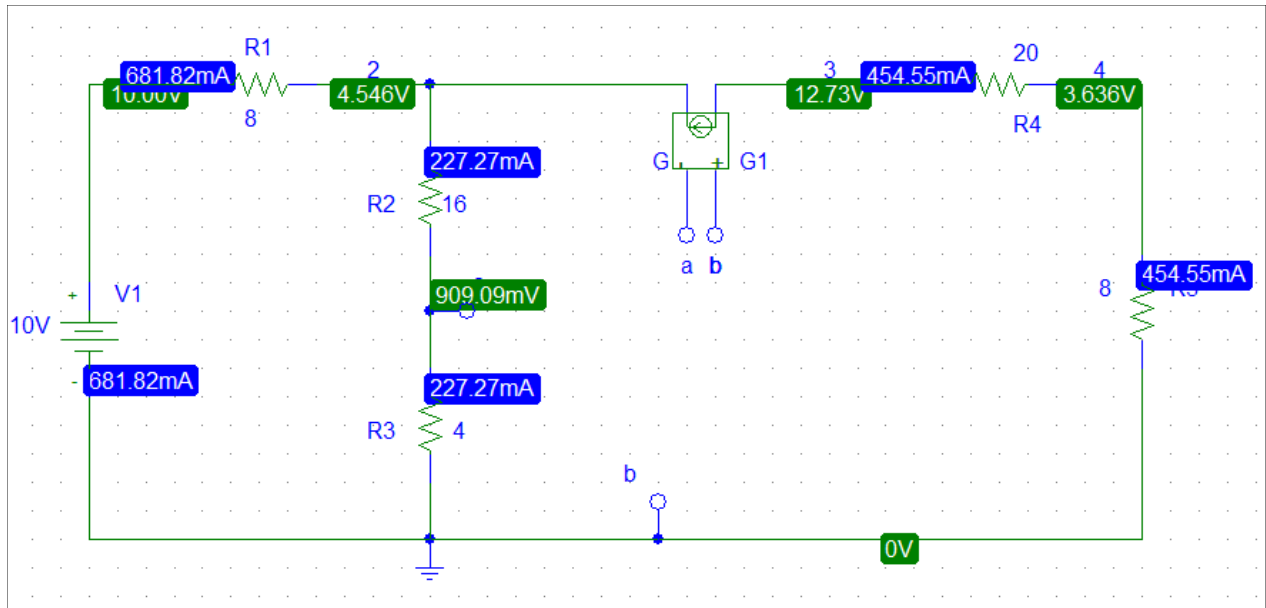


**Figure 5**

**\* Schematics Netlist \***

```

R_R4 4 3 20
R_R1 1 2 8
R_R2 a 2 16
R_R3 0 a 4
R_R5 4 0 8
V_V1 1 0 10V
G_G1 3 2 0 a 0.5

```

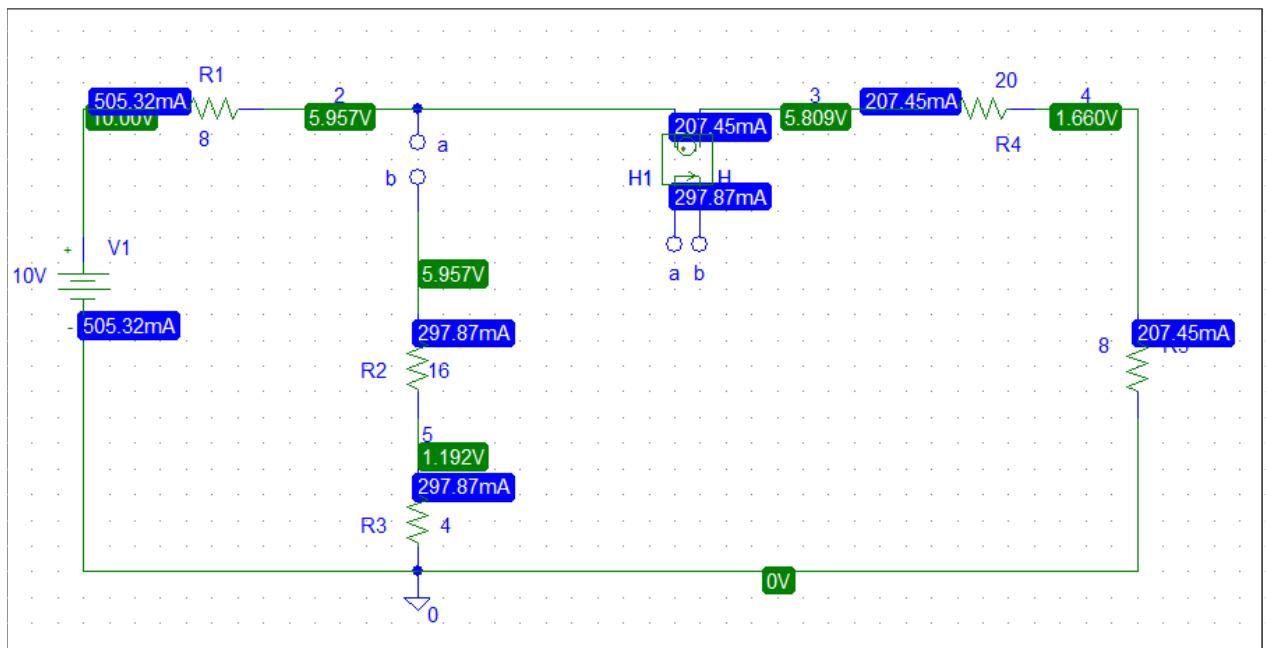

**Figure 7**

**\* Schematics Netlist \***

**V\_V1 1 0 10V**

**R\_R1 1 a 8**

**R\_R2 5 b 16**


**R\_R4 4 3 20**

**R\_R5 4 0 8**

**R\_R3 0 5 4**

**H\_H1 a 3 VH\_H1 0.5**

**VH\_H1 a b 0V**

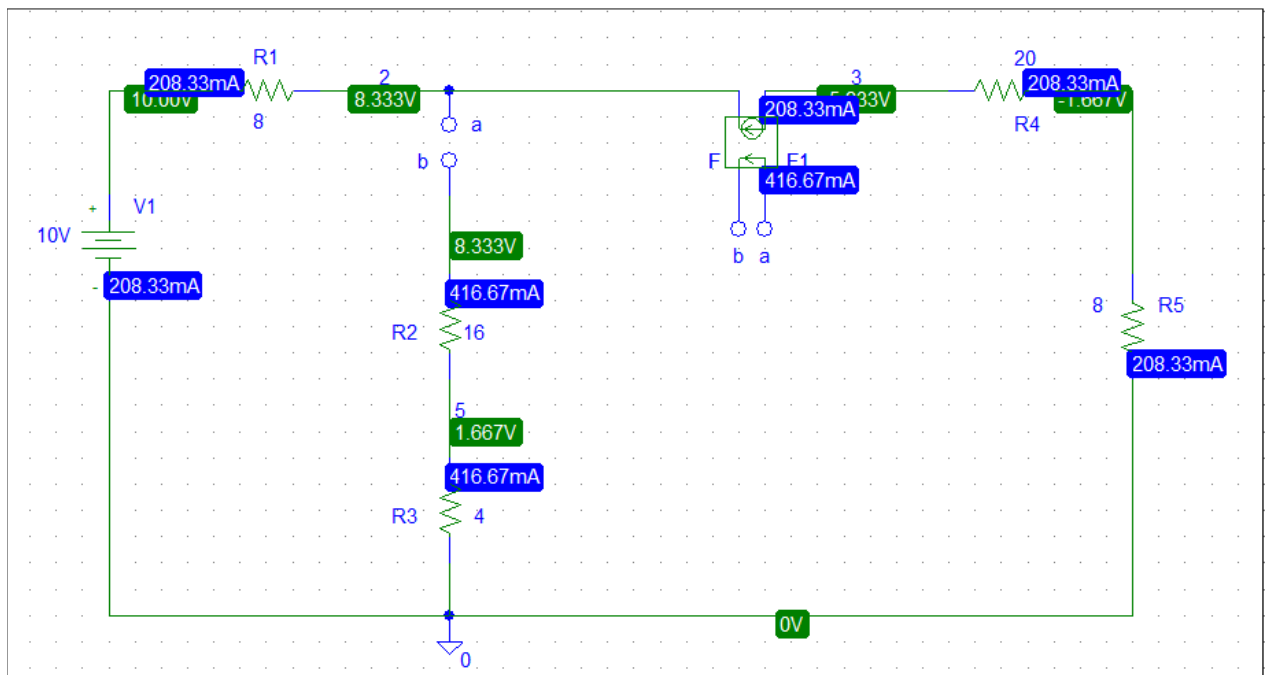

**Figure 9**

**\* Schematics Netlist \***

**V\_V1 1 0 10V**

**R\_R1 1 a 8**

**R\_R2 5 b 16**


**R\_R3 0 5 4**

**R\_R4 4 3 20**

**R\_R5 4 0 8**

**F\_F1 3 a VF\_F1 0.5**

**VF\_F1 a b 0V**

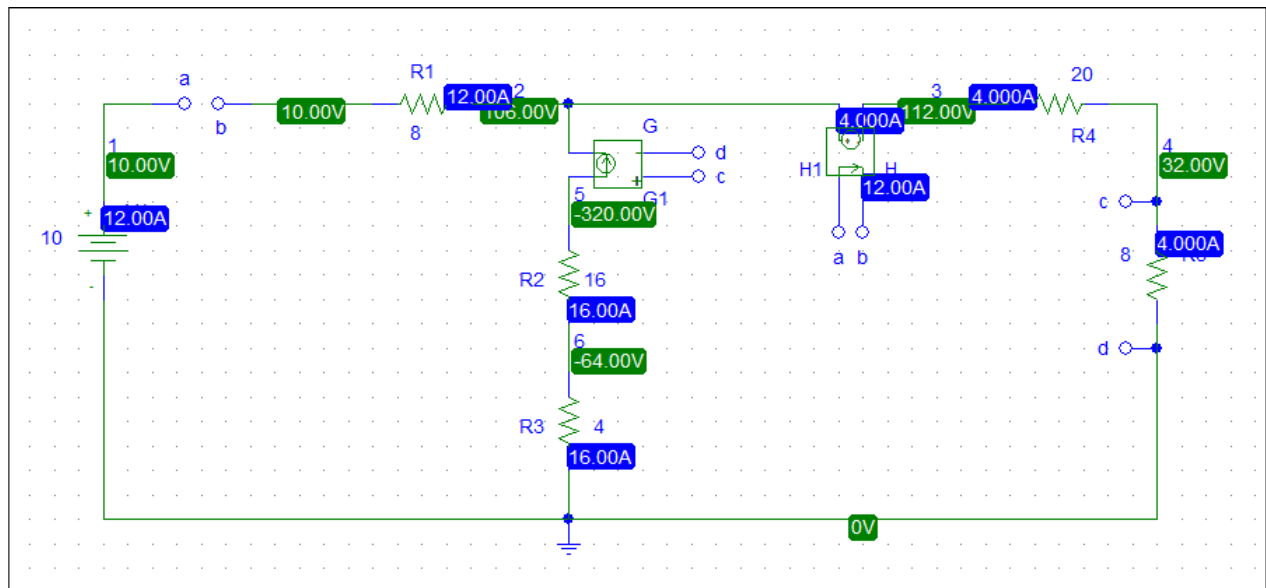

**Figure 11**

**\* Schematics Netlist \***

**G\_G1 5 2 c 0 0.5**

**H\_H1 2 3 VH\_H1 0.5**

**VH\_H1 a b 0V**

**V\_V1 a 0 10**

**R\_R3 0 6 4**


**R\_R5 c 0 8**

**R\_R4 c 3 20**

**R\_R2 6 5 16**

**R\_R1 b 2 8**

## Post-Lab Report Answers:

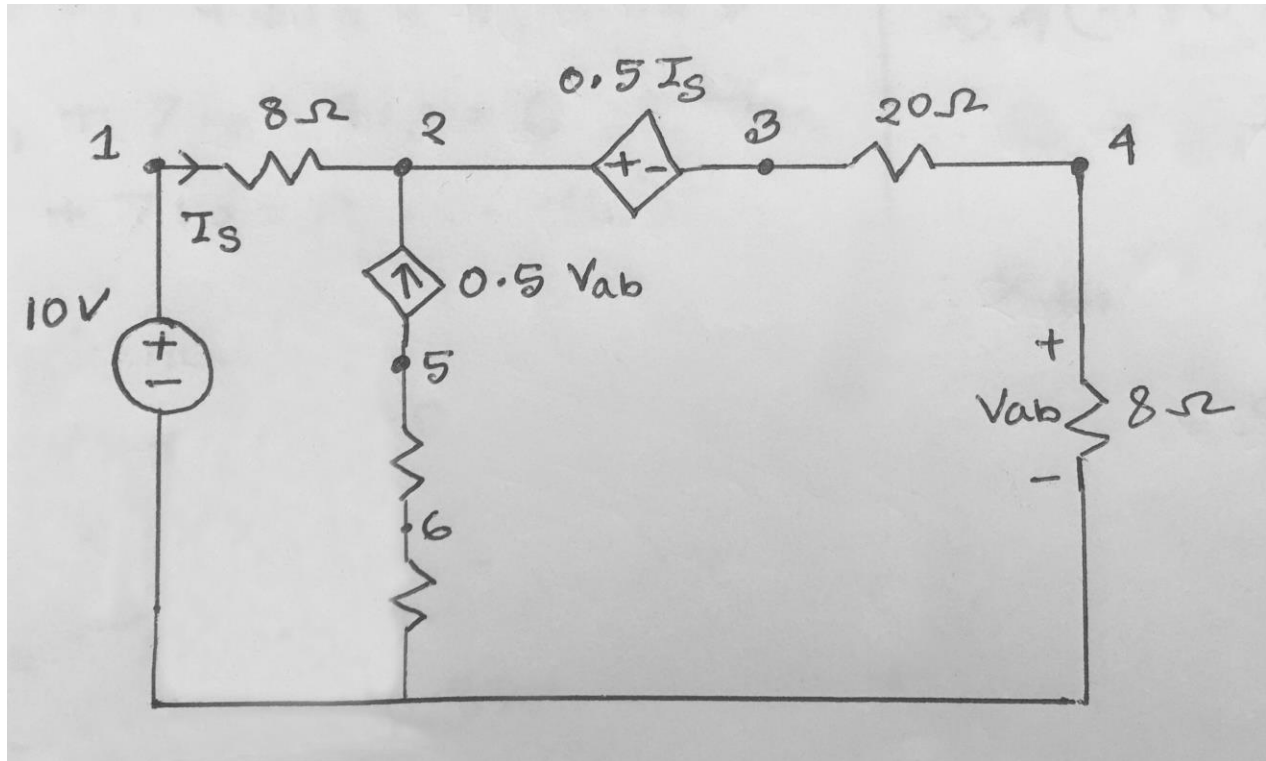

### Answers to the questions no: 01

From the figure,

$$I_s = i_1$$

$$V_{ab} = 8i_2$$

KVL at Super-mesh,

$$-10 + 8i_1 + 0.5I_s + 20i_2 + 8i_2 = 0$$

$$\Rightarrow -10 + 8i_1 + 0.5i_1 + 20i_2 + 8i_2 = 0 \quad [\because I_s = i_1]$$

$$\Rightarrow 8.5i_1 + 28i_2 = 10 \dots\dots\dots(i)$$

Then,

$$i_2 - i_1 - 0.5V_{ab} = 0$$

$$\Rightarrow i_2 - i_1 - 0.5 \times 8i_2 = 0 \quad [\because V_{ab} = 8i_2]$$

$$\Rightarrow i_1 + 3i_2 = 0 \dots\dots\dots(ii)$$

From equation (i) and (ii) we get,

$$i_1 = -12A$$

$$i_2 = 4\text{A}$$

So,

$$\begin{aligned} i_o &= i_2 - i_1 \\ &= 4 - (-12) \\ &= 16\text{A} \end{aligned}$$

Now, Voltage at Node 1,

$$V_1 = 10\text{V}$$

**Voltage at Node 2,**

Applying KCL at Node 2,

$$\begin{aligned} V_2 - 10 &- V_2 - 0.5I_s 28 = 16 \\ \Rightarrow V_2 - 10 - V_2 - 0.5 \times (-12) 28 &= 16 \\ \Rightarrow 9V_2 - 56 &= 47728 \\ \Rightarrow V_2 &= 106\text{V} \end{aligned}$$

Voltage at Node 3,

$$\begin{aligned} i_2 &= 4\text{A} \\ R &= 20 + 8 \\ &= 28\Omega \\ V_3 &= (4 \times 28) \\ &= 112\text{V} \end{aligned}$$

Voltage at Node 4,

$$\begin{aligned} i_2 &= 4\text{A} \\ R &= 8\Omega \\ V_4 &= (4 \times 8) \\ &= 32\text{V} \end{aligned}$$

Voltage at Node 5,

$$\begin{aligned} i_o &= 16\text{A} \\ R &= 16 + 4 \\ &= 20\Omega \\ V_5 &= - (16 \times 20) \\ &= -320\text{V} \end{aligned}$$

Voltage at Node 6,

$$\begin{aligned} i_o &= 16\text{A} \\ R &= 4\Omega \\ V_6 &= - (16 \times 4) \\ &= -64\text{V} \end{aligned}$$



So,  
 $V_1 = 10V$   
 $V_2 = 106V$   
 $V_3 = 112V$   
 $V_4 = 32V$   
 $V_5 = -320V$   
 $V_6 = -64V$   
 $i_1 = -12A$   
 $i_2 = 4A$   
 $i_o = 16A$

### Answers to the questions no: 02

Compare the theoretical solution of the circuit with the solutions obtained from PSpice simulation:

		Theoretical solution	PSpice solution
<b>Current</b>	$i_1$	-12A	12A
	$i_2$	4A	4A
	$i_o$	16A	16A
<b>Voltages</b>	$V_1$	10V	10V
	$V_2$	106V	106V
	$V_3$	112V	112V
	$V_4$	32V	32V
	$V_5$	-320V	-320V
	$V_6$	-64V	-64V

**Result:**

By doing this experiment we are able to simulate our circuits using PSpice and test the results. Previously we had tested our circuits practically, but this is more efficient.

**Conclusion:**

While doing this experiments, the readings were taken very carefully. Though there is some difference between calculated value and PSpice value, at the end of the experiment we finally gained practical knowledge that how to work with PSpice Schematic and independent source.