




**EAST WEST UNIVERSITY**  
**Department of Computer Science and Engineering**  
**B.Sc. in Computer Science and Engineering Program**  
**Mid Term 1, Summer 2021**


**Course:** CSE 109/209 – Electrical Circuits, Section-5  
**Instructor:** SHK, Senior Lecturer, CSE Department  
**Full Marks:** 20  
**Time:** 1 Hour and 30 Minutes [Including submission time]

**Note:** There are FIVE questions, answer ALL of them. Course outcomes (CO) and marks of each question are mentioned at the right margin.

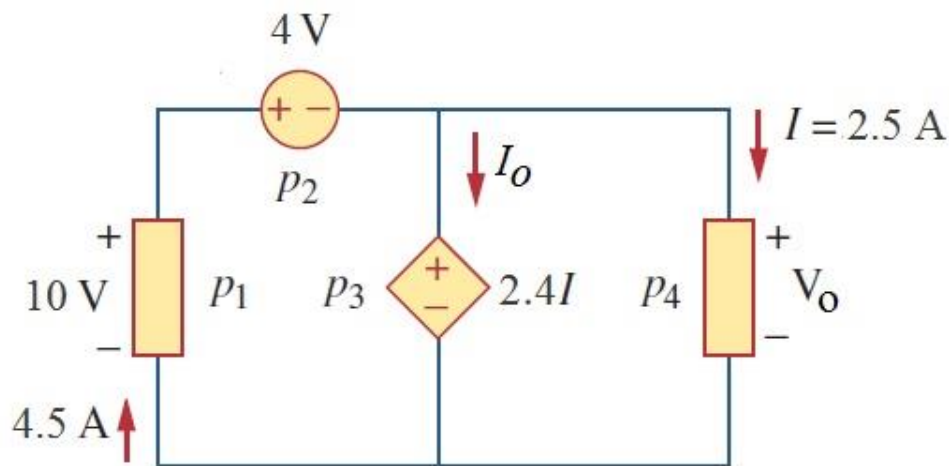1. **Estimate** the power absorbed or supplied by all the circuit elements from the figure given below, [CO1, Mark: 3]



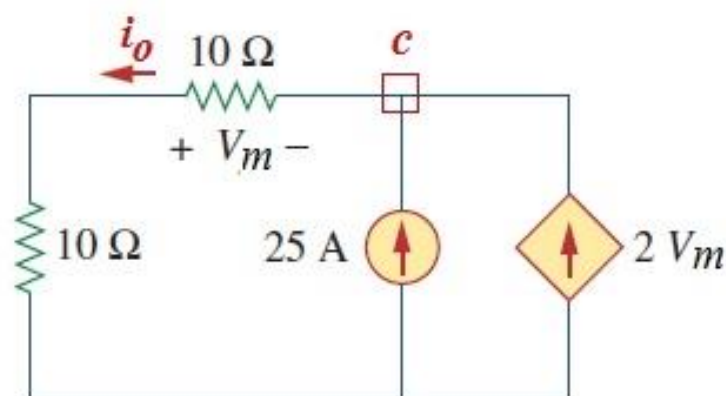2. From the figure given below, [CO1, Mark: 4]




- a) Find  $V_m$  and  $i_o$  .  
 b) Also, **verify** Kirchhoff's Current Law (KCL) at node c.

[Note that, to solve this circuit **you cannot use** advance analysis techniques like Nodal Analysis. You have to use the **Basic Laws** for analysis!]

3. Determine  $R_{ab}$  from the circuit given below.


[CO1,  
Mark: 4]

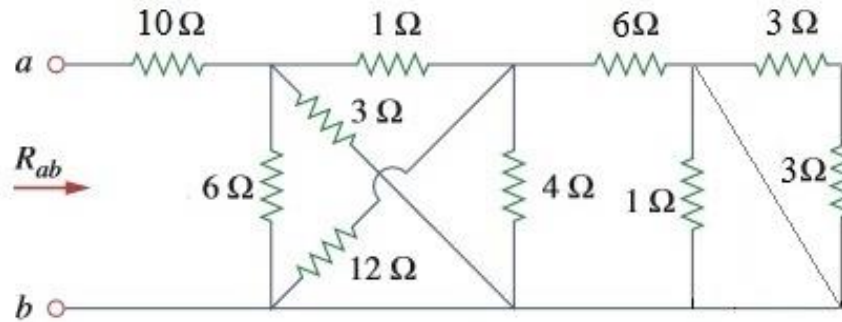

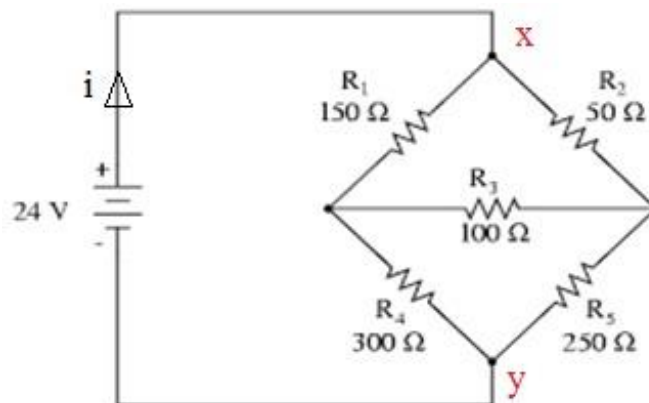4. Analyze the bridge network circuit given below using **wye-delta** transformation technique and find the followings:
- Find the total current  $i$  and the voltage  $V_{R4}$  (voltage across  $300\Omega$  resistor).
  - Find the total current  $i$  and the voltage  $V_{R5}$  (voltage across  $250\Omega$  resistor).

[CO1,  
Mark: 4]

[Note that, if the last digit of your student ID is even, then solve a, otherwise solve b].



5. Determine the labeled node voltages  $v_1$ ,  $v_2$  and  $v_3$  using nodal analysis from the following circuit [Use Cramer's rule to analyze].

[CO2,  
Mark: 5]

